

Device Delay (2F)


Copyright (c) 2011-2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".



Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.





Input Switching H → L

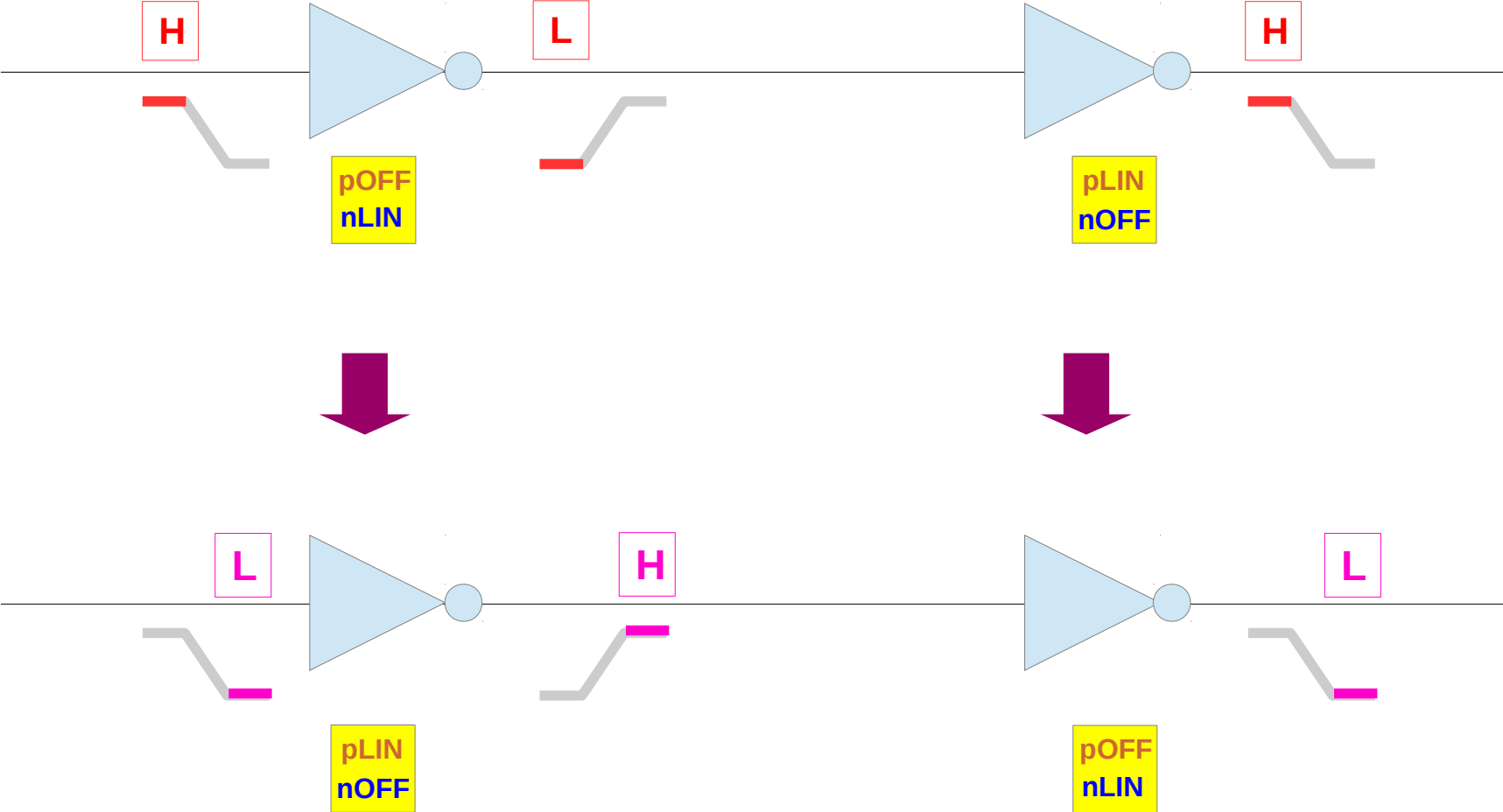



Charge (-) and (+)

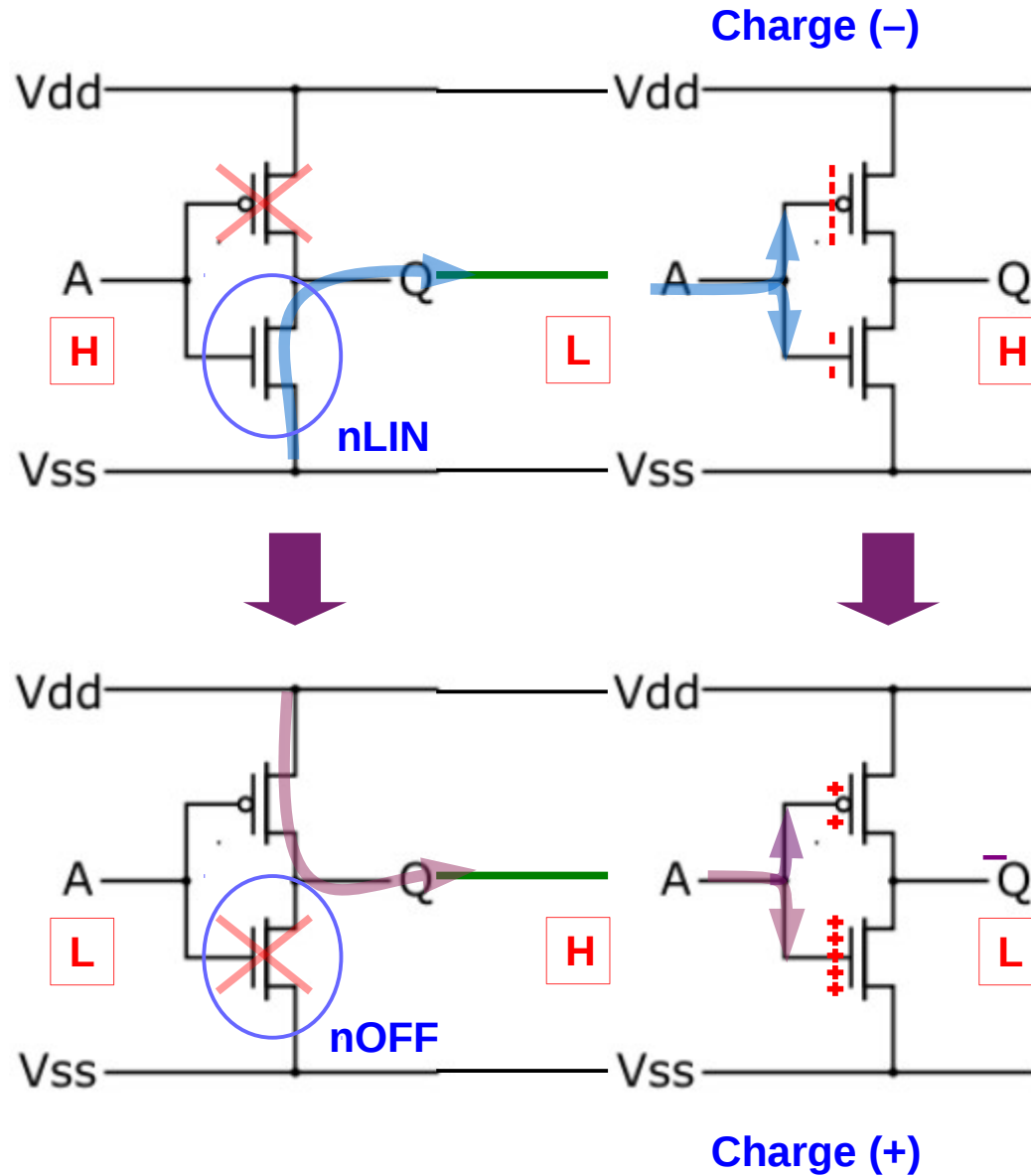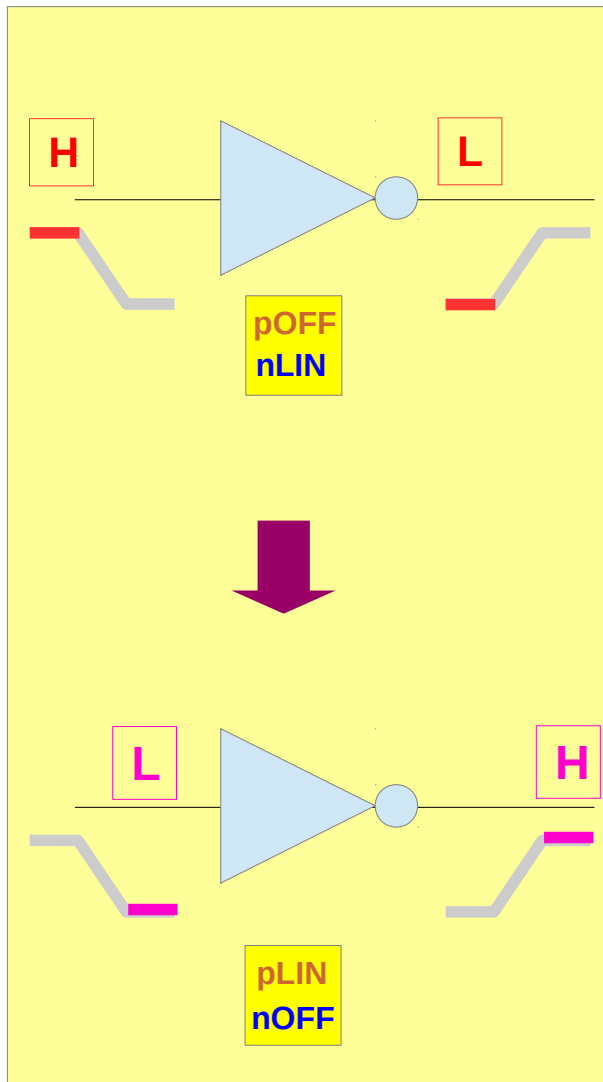


Gate Capacitances

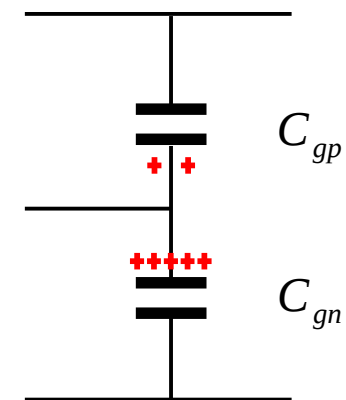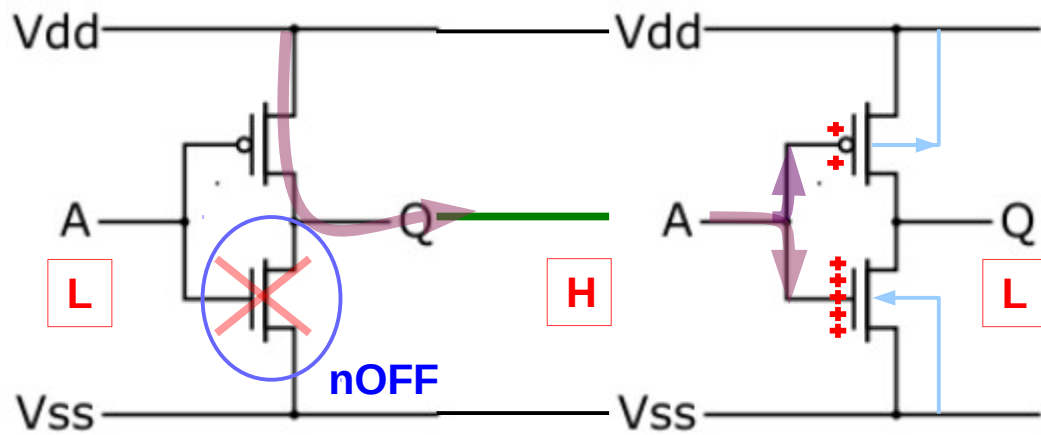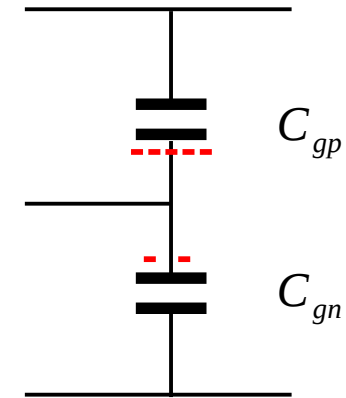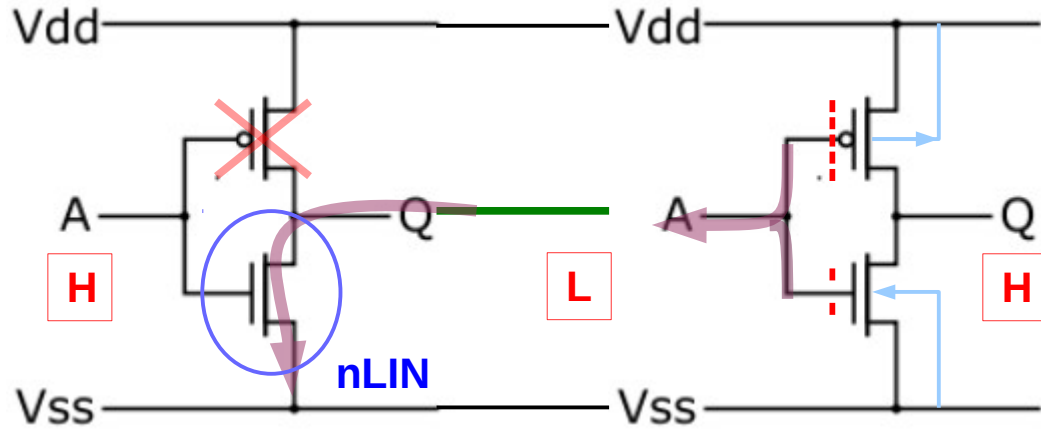


Load Capacitance Model

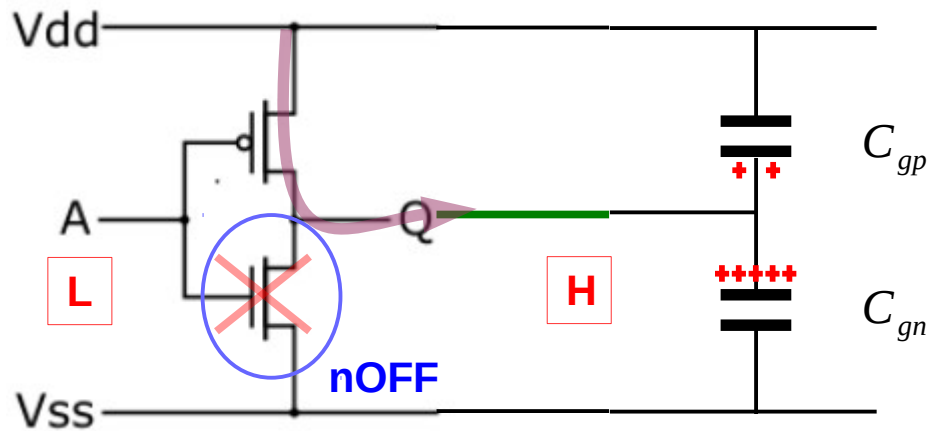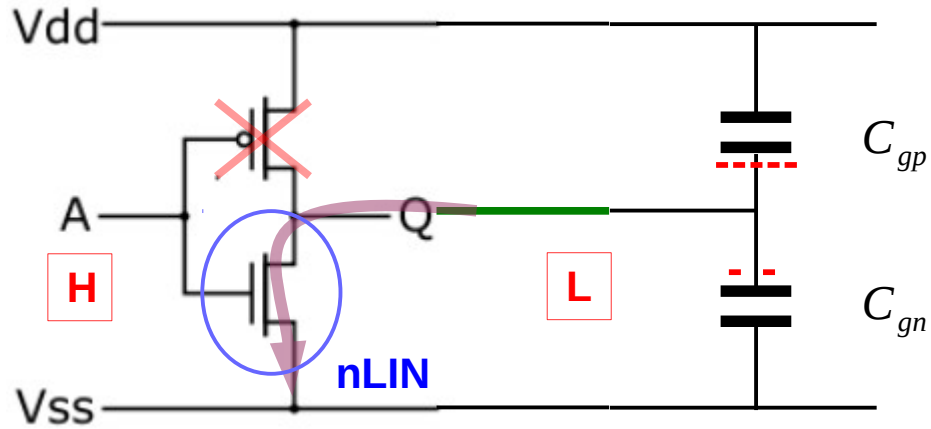


Charge (-) ↔ Discharge (+)

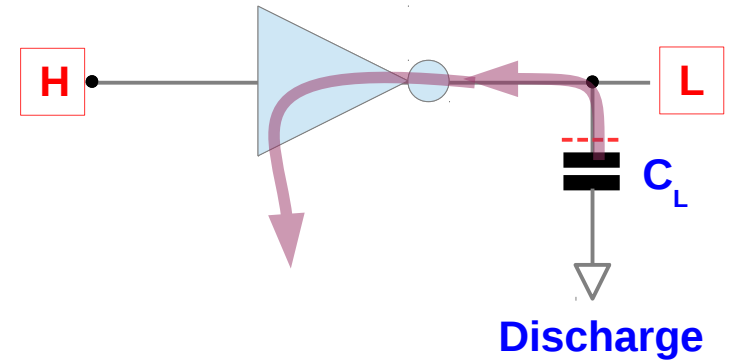

$$C_L = C_{pn} + C_{gn}$$

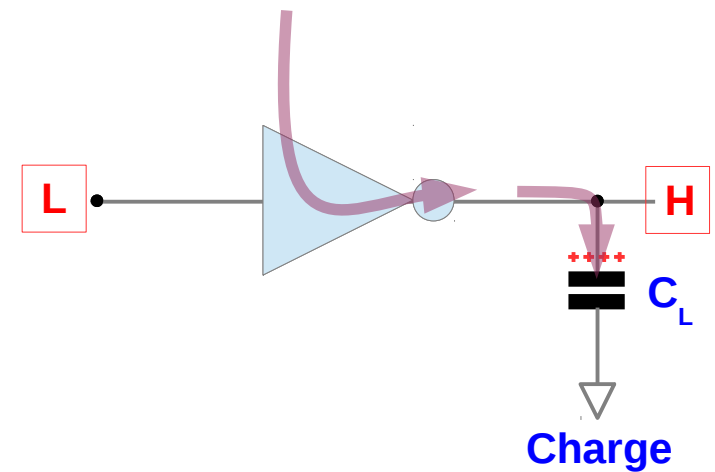

Load Capacitance


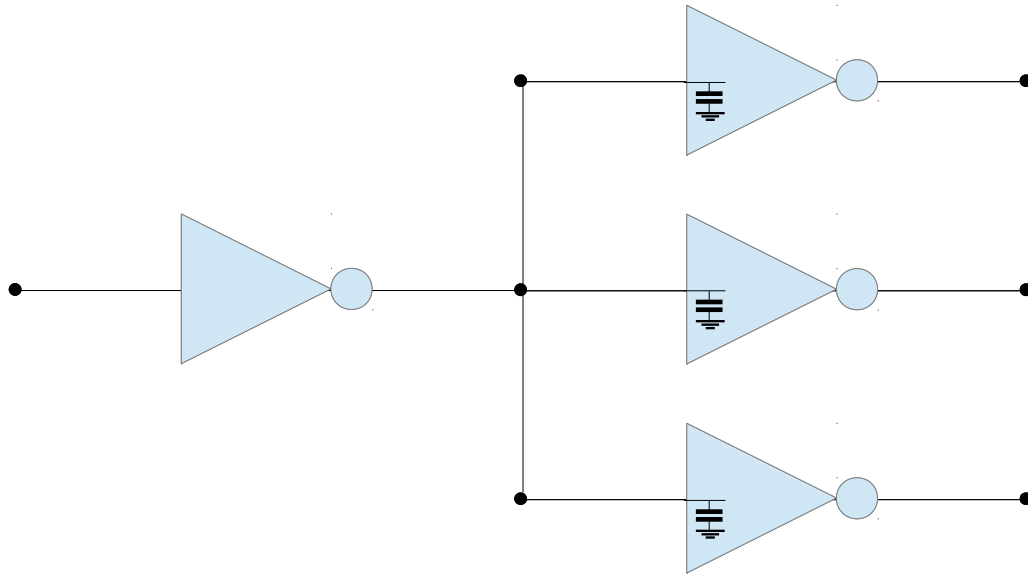


$$C_L = 3C_g$$



Big Capacitance

- A signal connected off-chip
- A signal with very long wire
- A clock signal driving many flip-flops




Fall Time

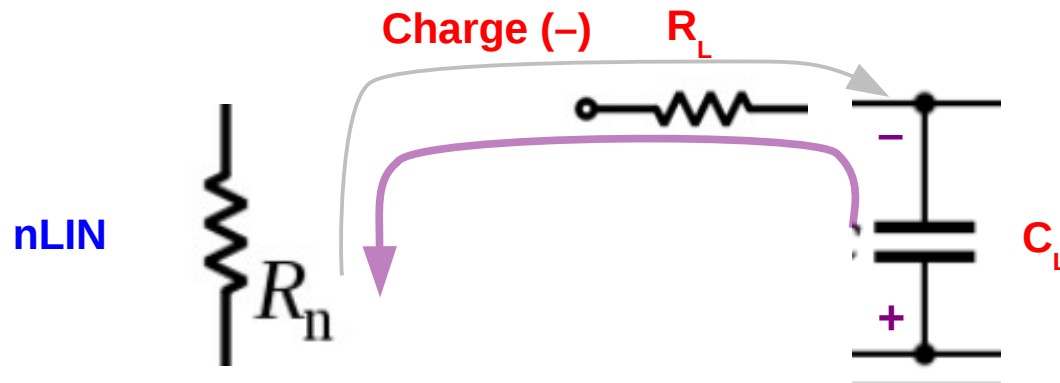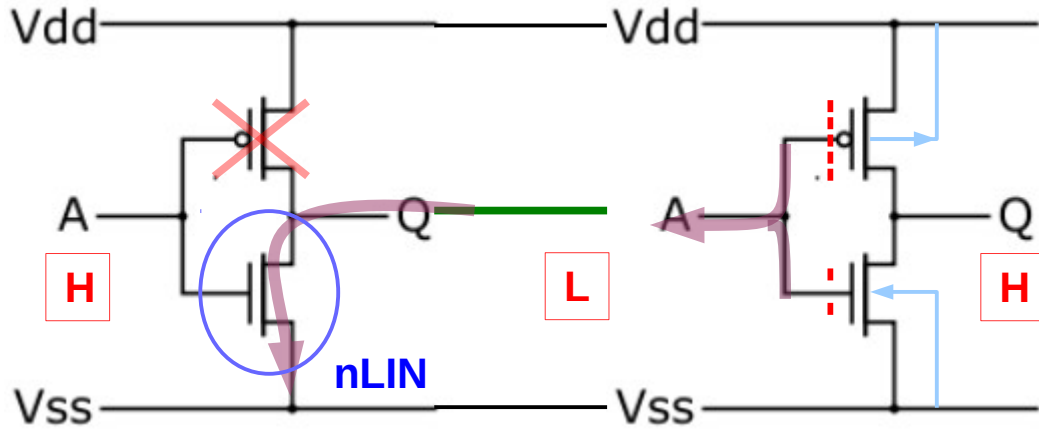

Rise Time

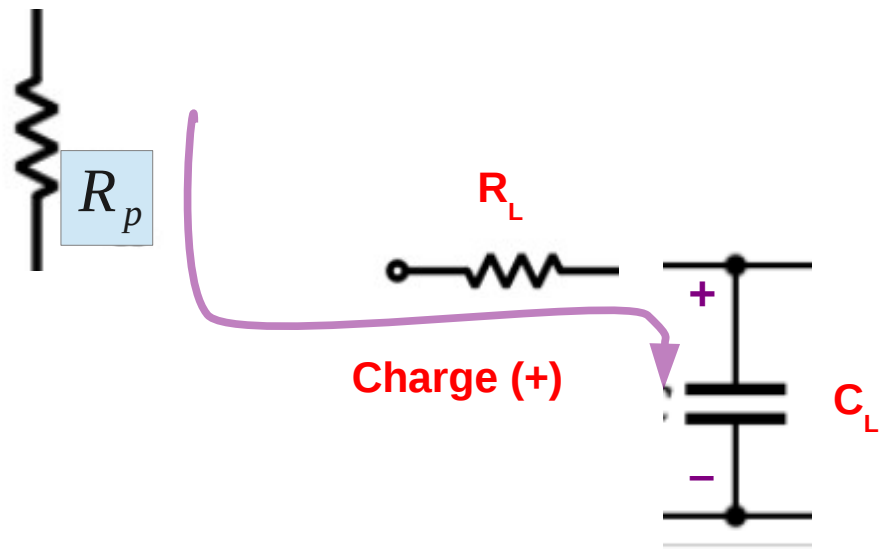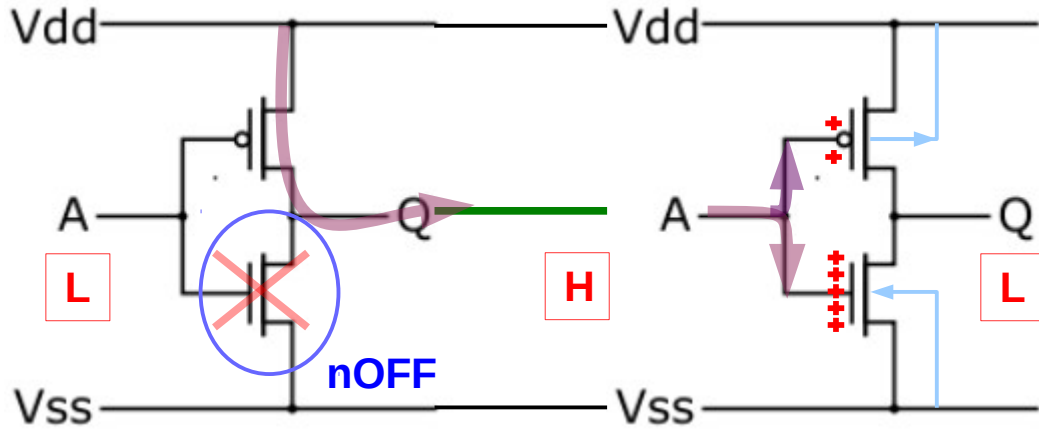


Rising and Falling Time

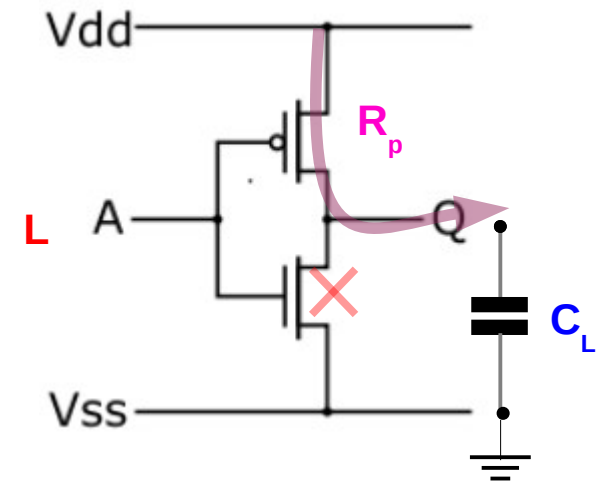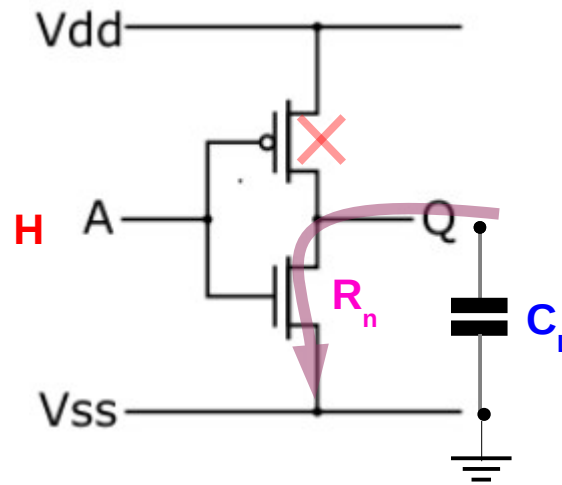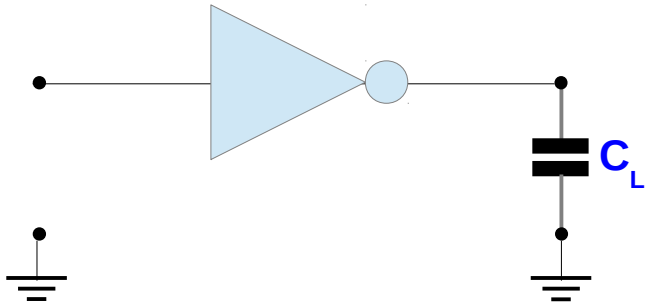



$$t_f \propto R_n C_L$$

$$t_r \propto R_p C_L$$

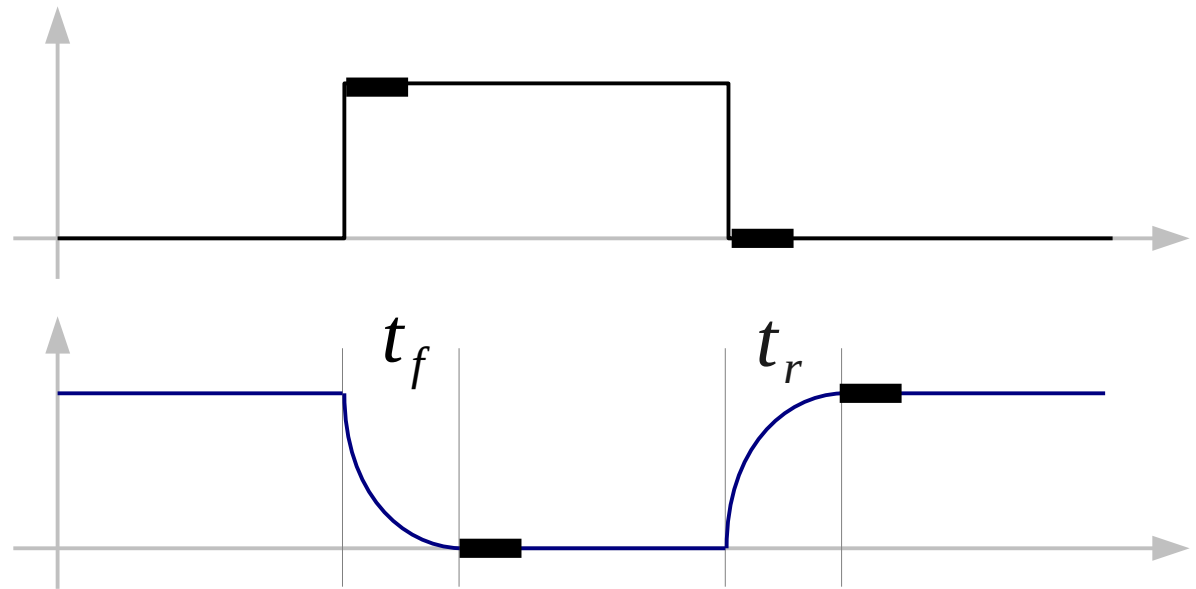


Rising and Falling Time (1)

$$R_n < R_p$$

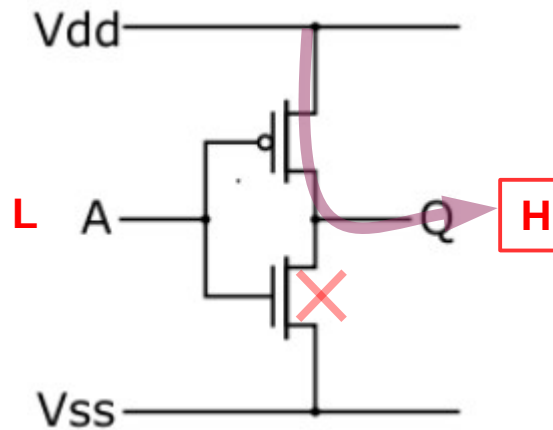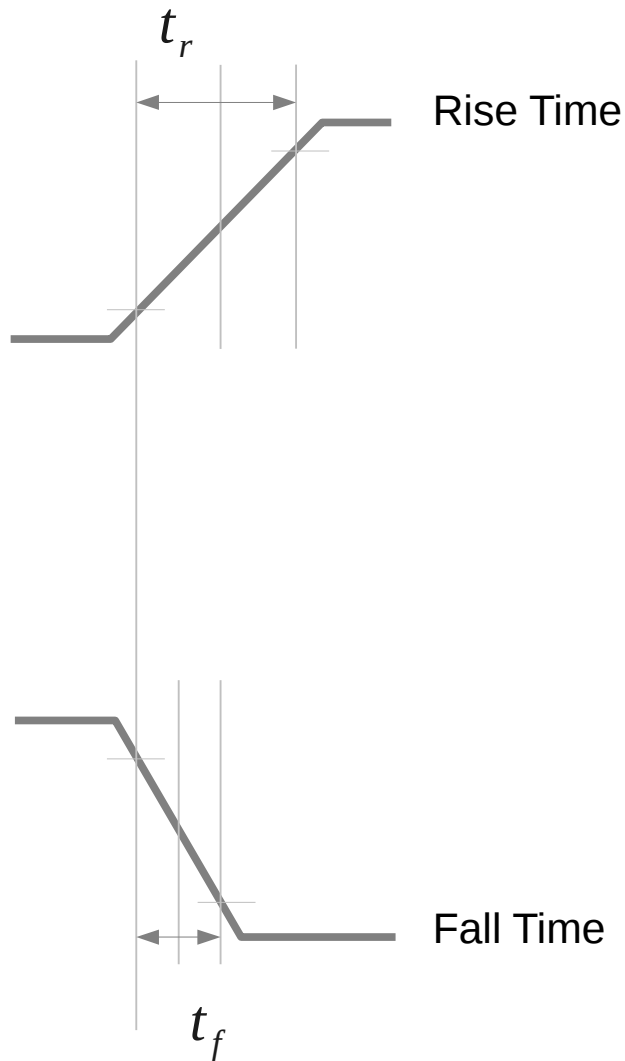


$$\frac{\beta_n}{\beta_p} > 1 \quad \frac{R_n}{R_p} < 1$$
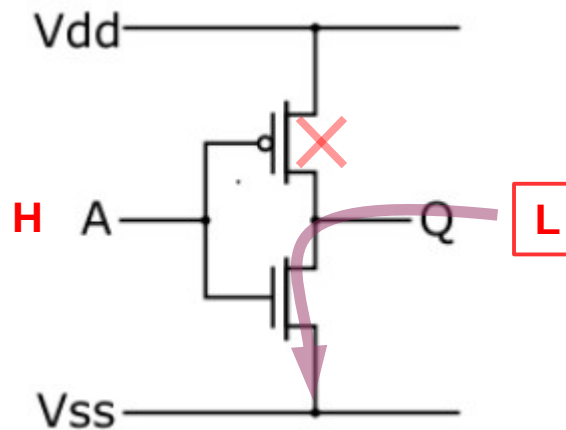
$$\frac{\tau_n}{\tau_p} = \frac{R_n C_{out}}{R_p C_{out}} = \frac{R_n}{R_p} < 1$$




$$\frac{t_f}{t_r} = \frac{2.2\tau_n}{2.2\tau_p} < 1$$


Rising and Falling Time (2)

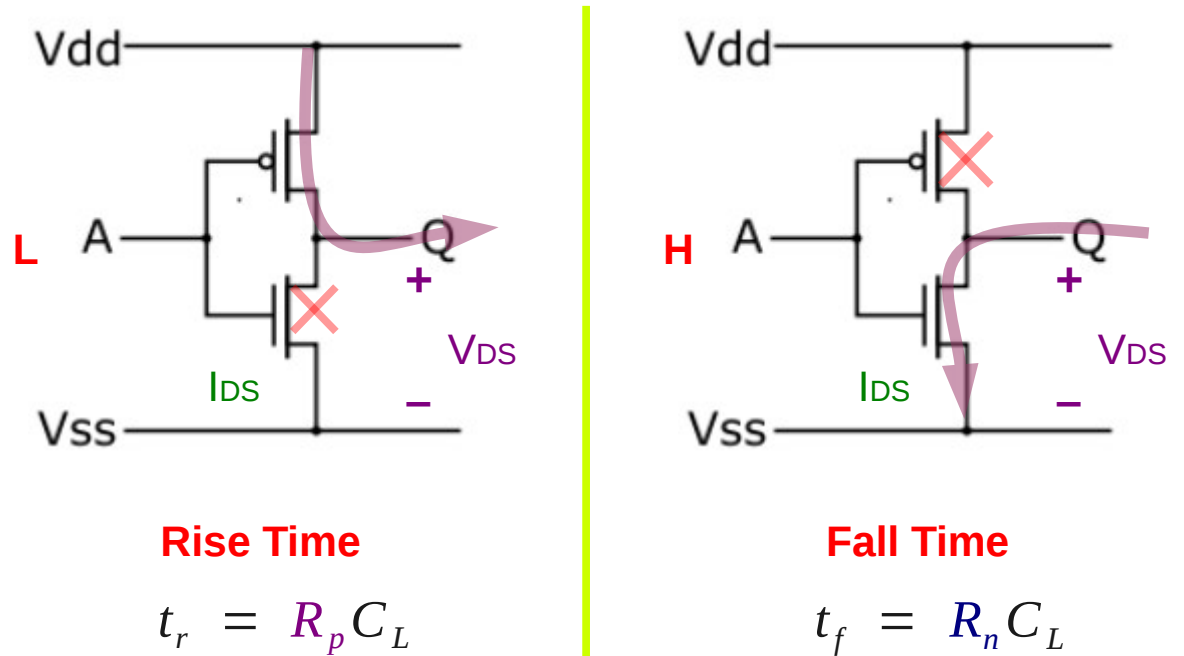




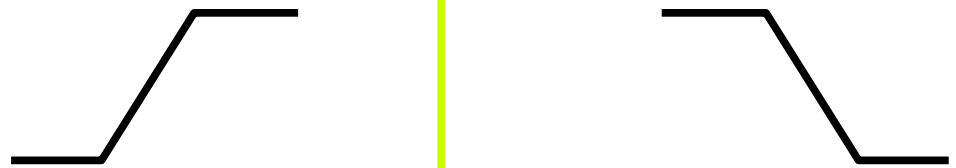
$$\frac{\beta_n}{\beta_p} = 1.0 \quad R_n = R_p$$


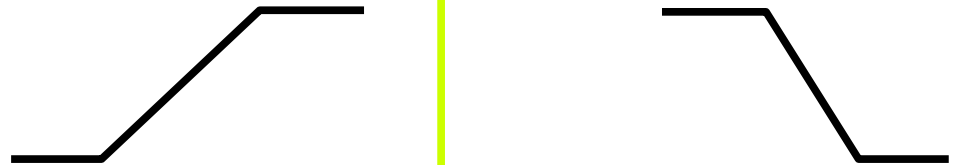
$$\frac{\beta_n}{\beta_p} = 2.0 \quad R_n < R_p$$



Propagation Delay

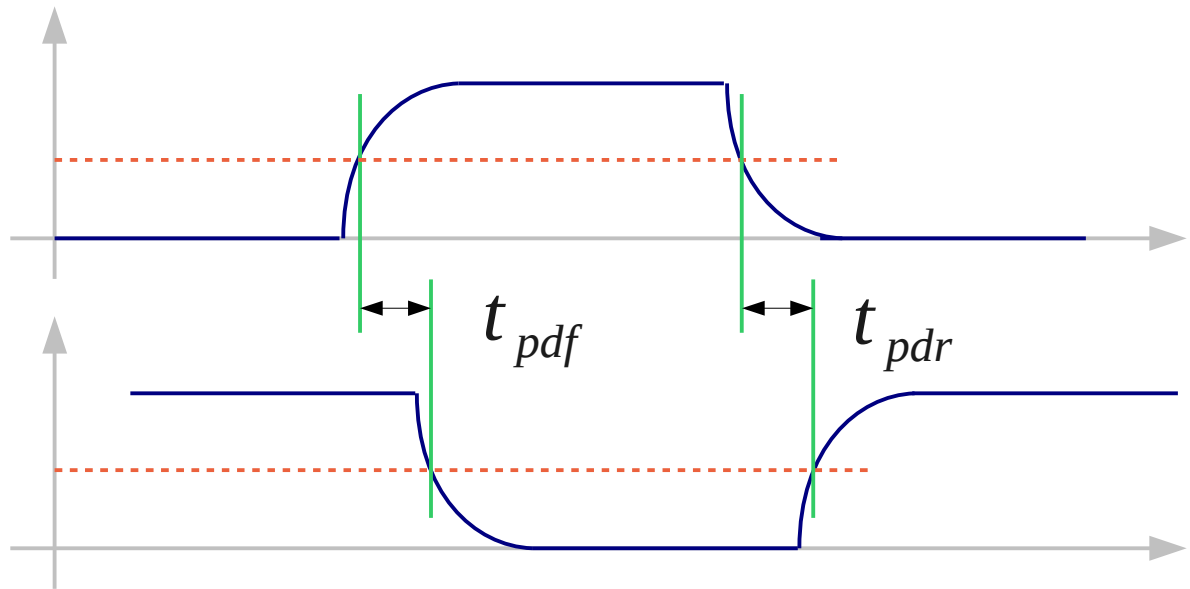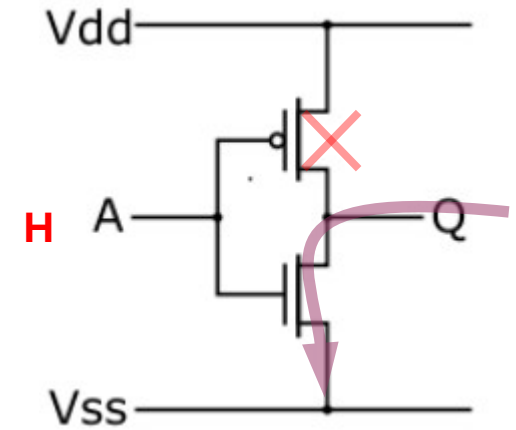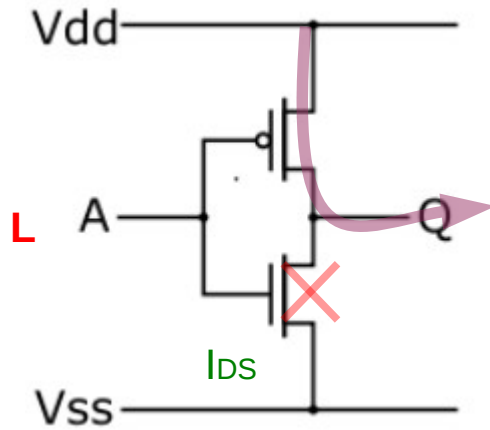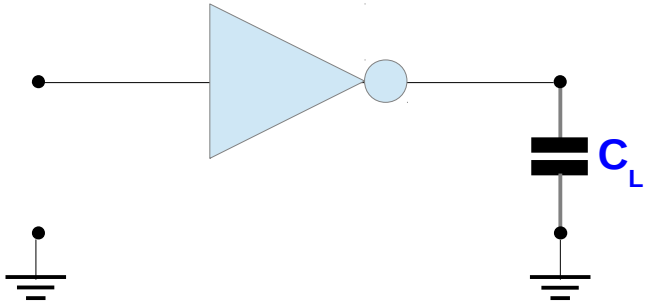

Characteristic Curve

References

- [1] <http://en.wikipedia.org/>
- [2] <http://www.allaboutcircuits.com/>
- [3] W. Wolf, "Modern VLSI Design : Systems on Silicon"
- [4] N. Weste, D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective"
- [5] J. P. Uyemura, "Introduction to VLSI Circuits and Systems"