

BJT Overview

Characteristics (H.2)

20170421-2

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

References

Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org


V_{BE}

V_B measured from E

V_{CB}


V_C measured from B

n p n

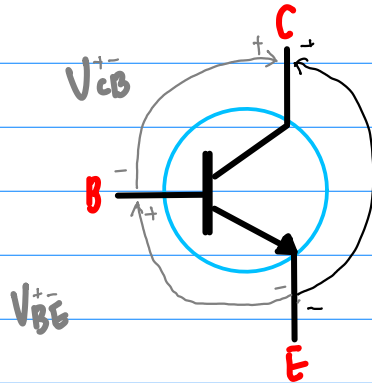


V_{CE}

$$V_{CE} = V_{CB}^{+-} + V_{BE}^{+-}$$

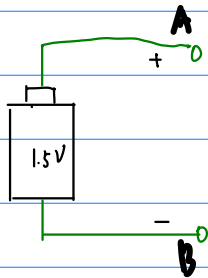


$$V_{AB} = 1.5V$$


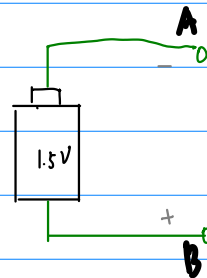




$$V_{BA} = -1.5V$$

$$V_{AB}^{+-} = -V_{BA}^{+-}$$

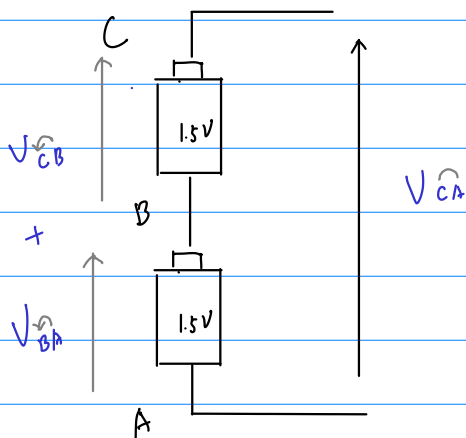

Active Region

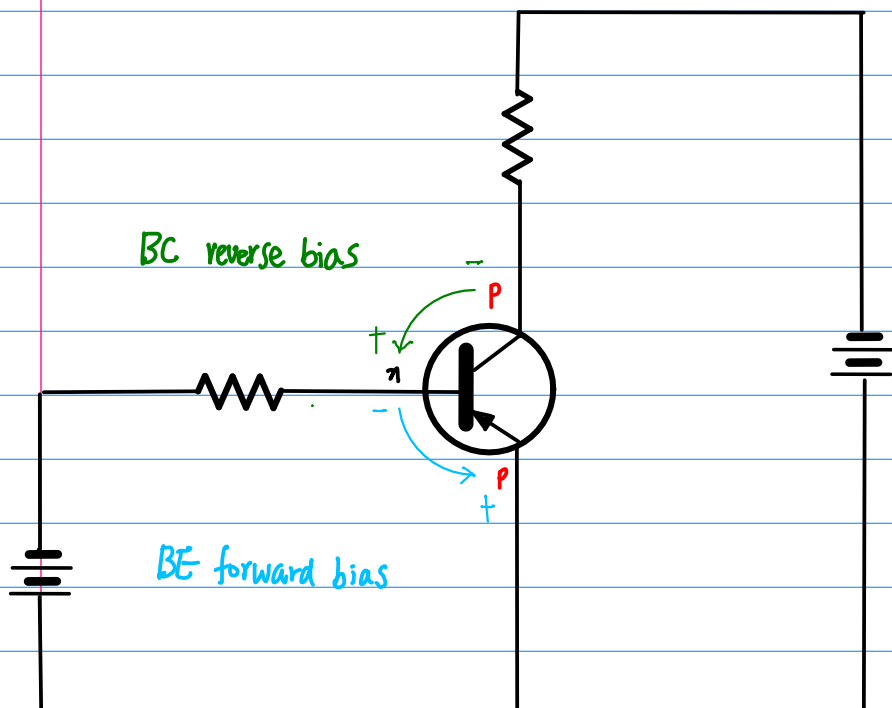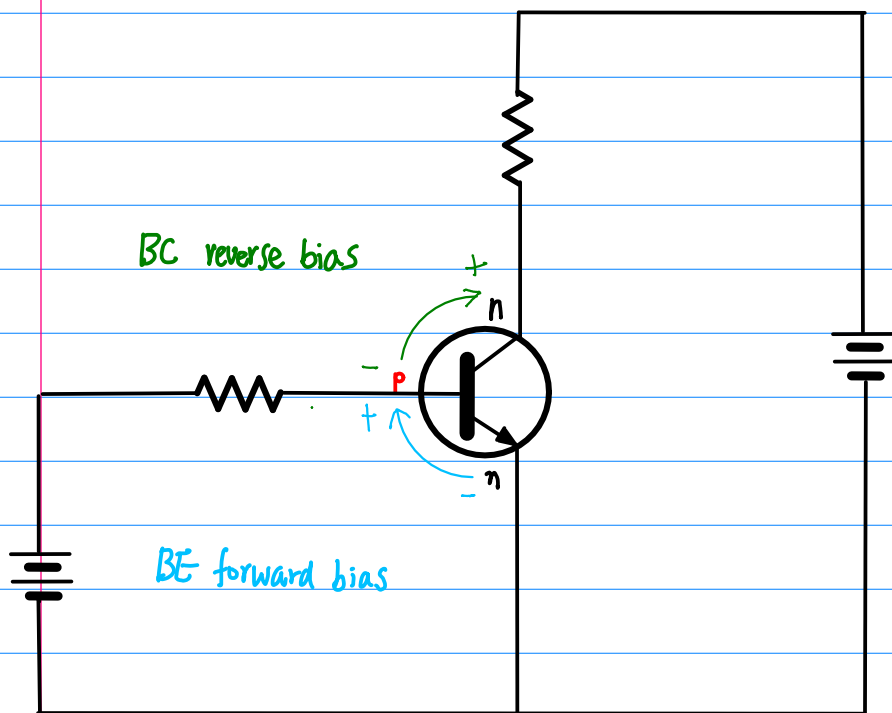

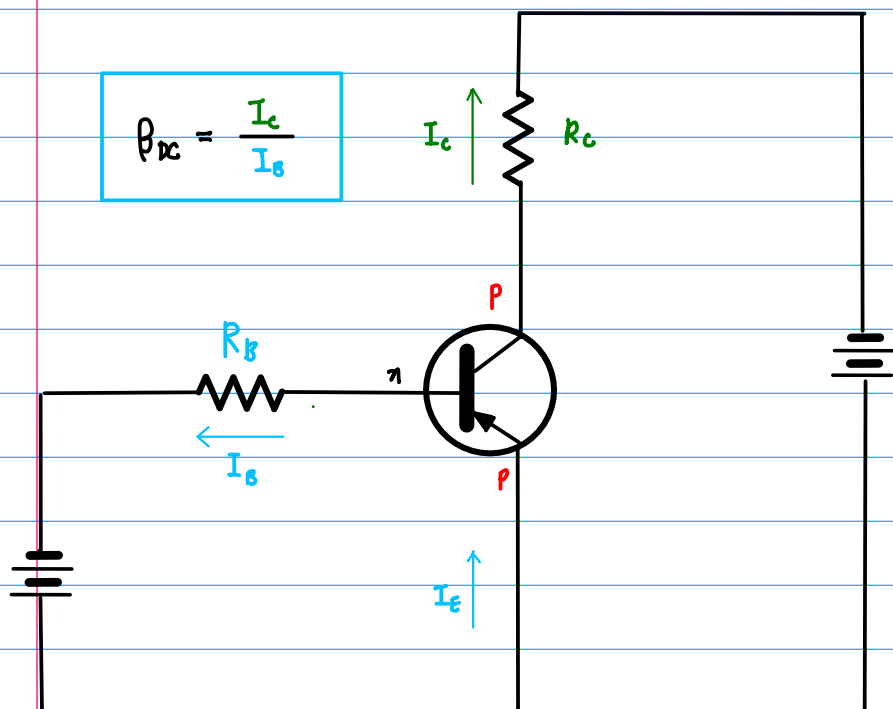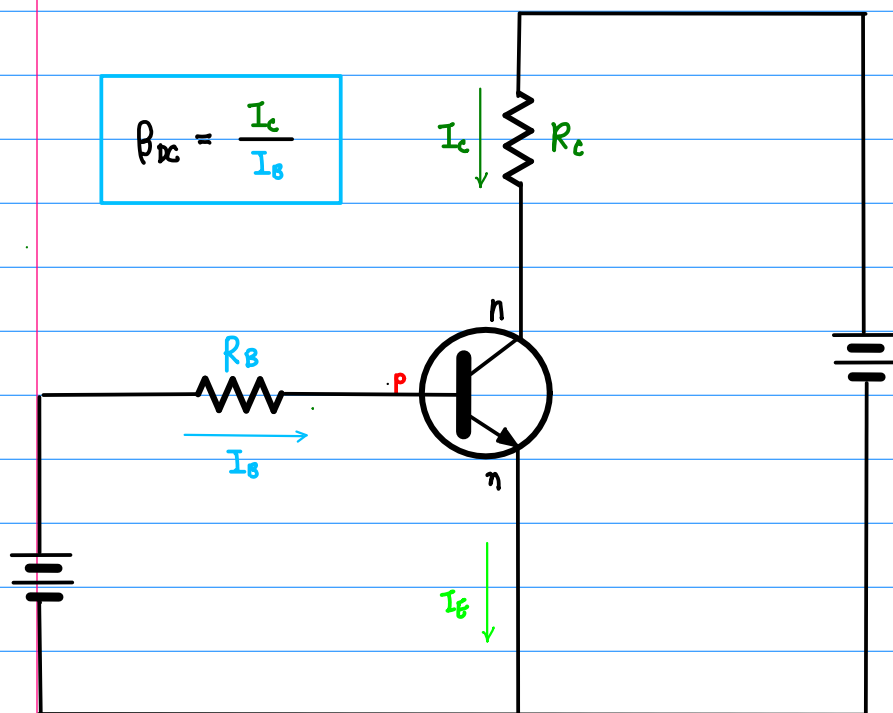



$$\beta_{DC} = \frac{I_c}{I_B}$$


20 ~ 200

$$h_{FE} = \beta_{DC}$$

$$\alpha_{DC} = \frac{I_c}{I_E}$$

0.95 ~ 0.99

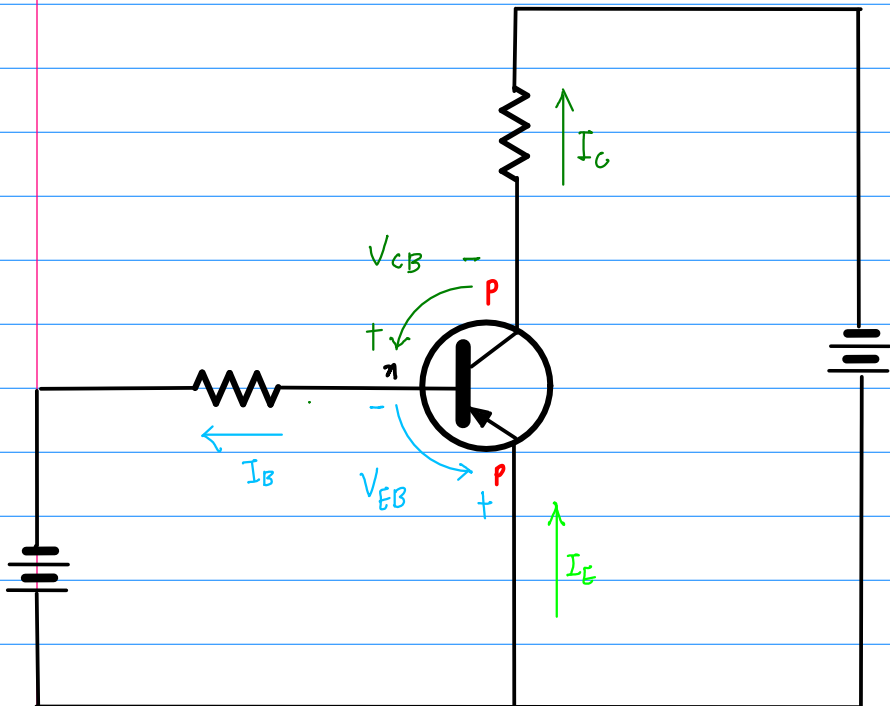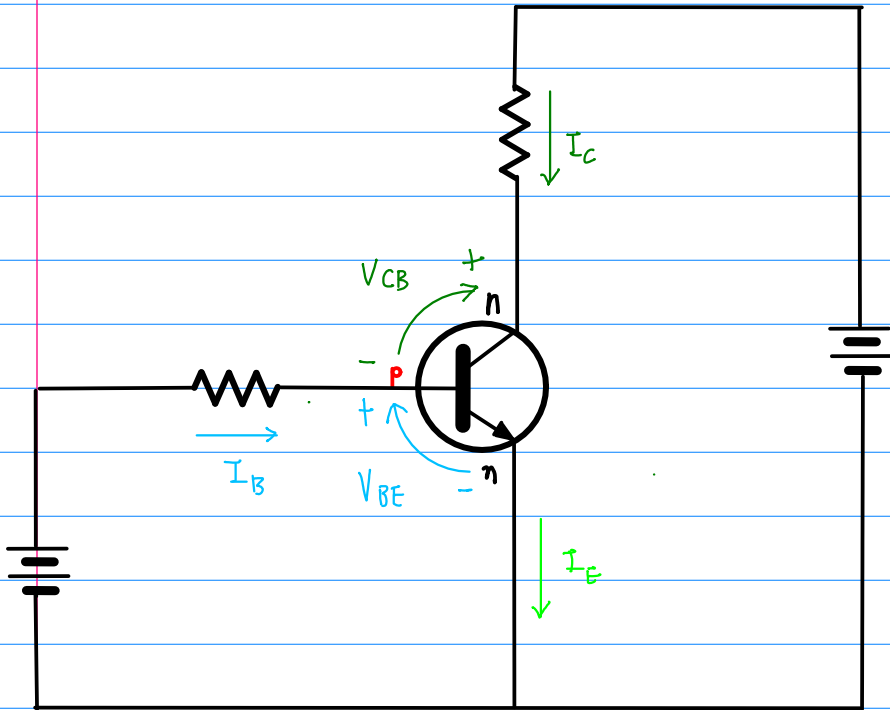

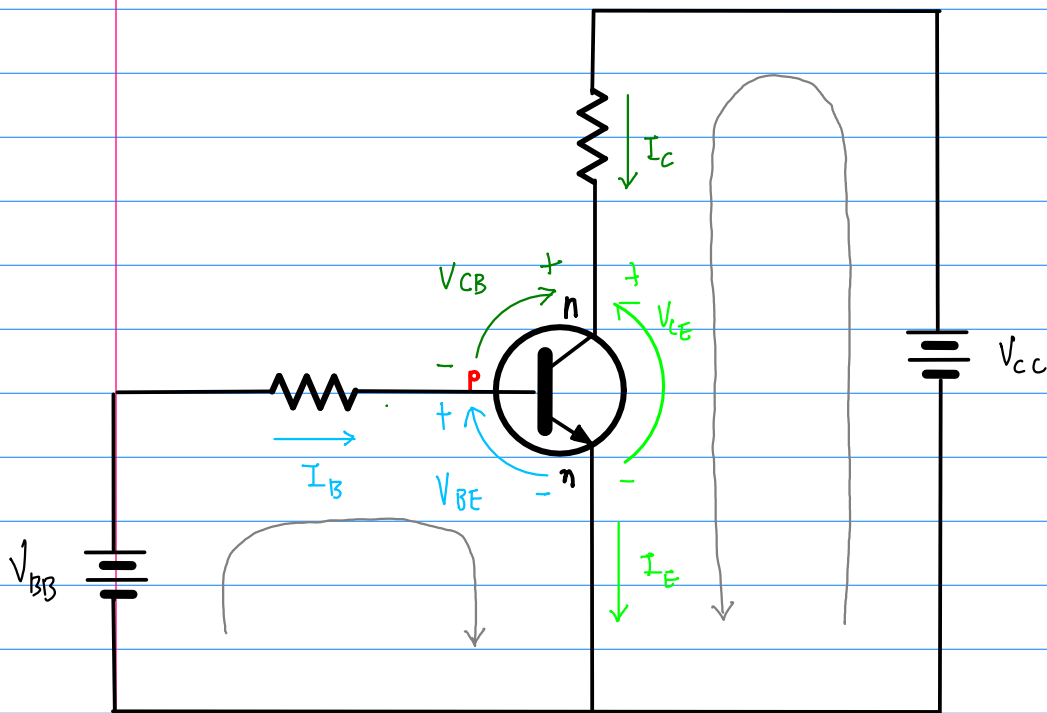

$$V_{BB} = I_B R_B + V_{BE}$$

$$V_{CC} = I_C R_C + V_{CE}$$



$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$


$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C = \beta \cdot I_B$$
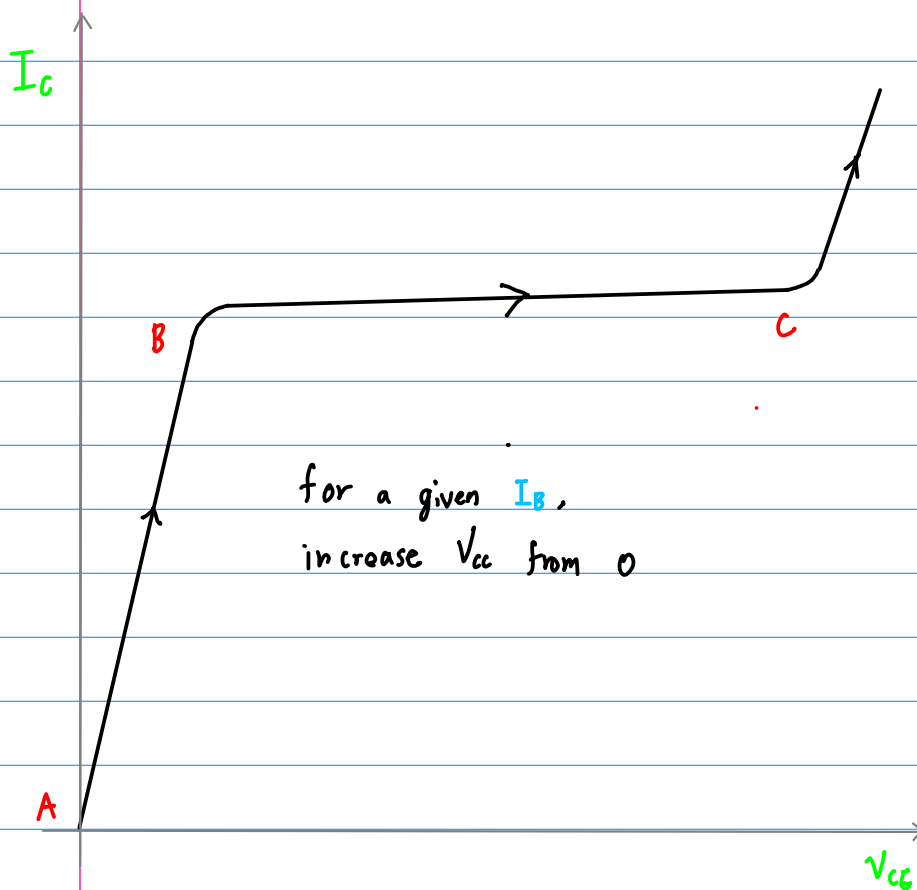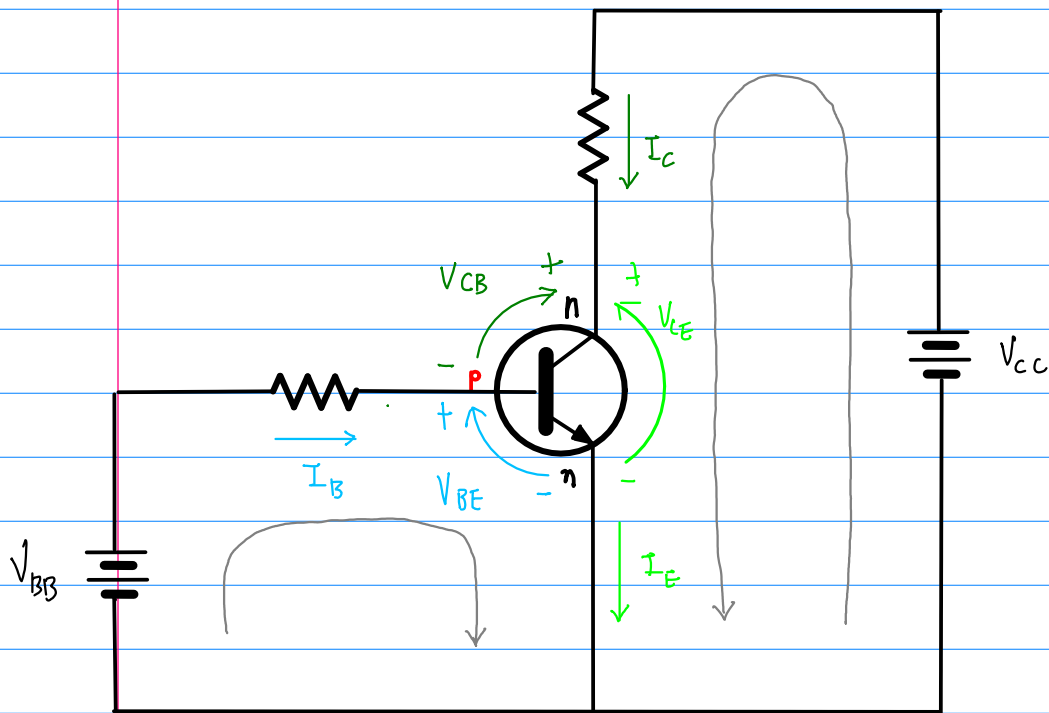
$$V_{CE} = V_{CC} - \beta \cdot I_B \cdot R_C$$



BJT Input Characteristic

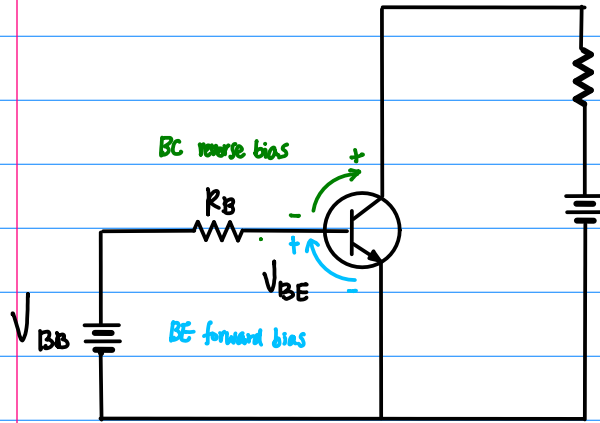


$$V_{BB} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$V_{BE} = 0.7 \text{ V in active region}$$

$$\uparrow I_B = \frac{V_{BB} - 0.7}{R_B} \downarrow$$


BJT Output Characteristics

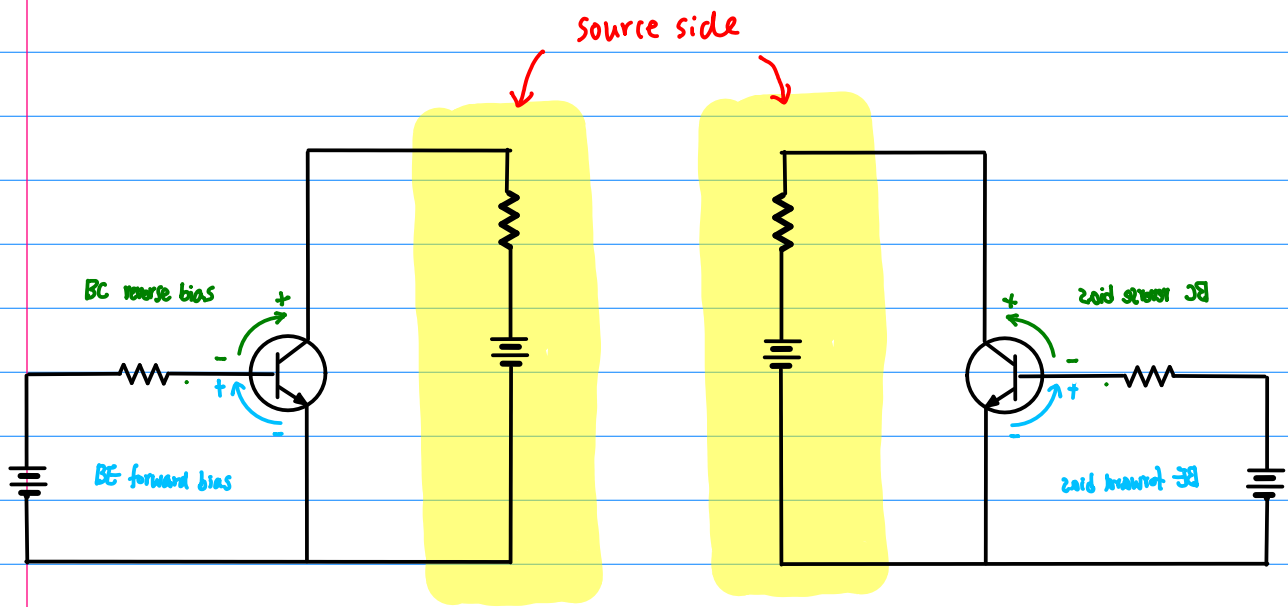


Active Region assumed

Source Side Equation R_T

max v $\leftarrow R_L = \infty$

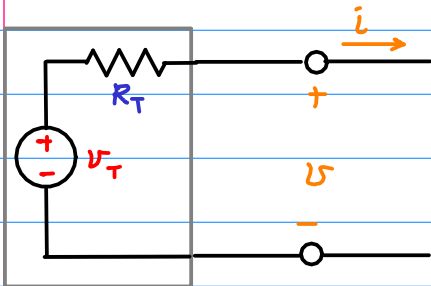


max i $\leftarrow R_L = 0$

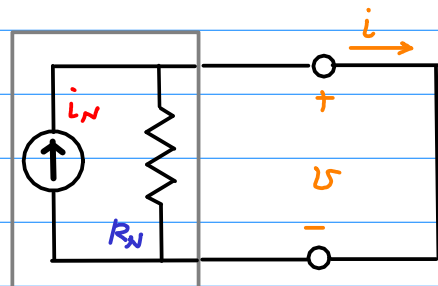




$i < i_N$
 $v < v_T$



$0 < R_L < \infty$


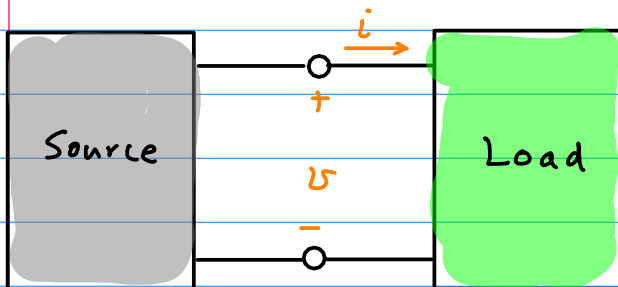


$$i = \frac{1}{R_T} (v_T - v)$$


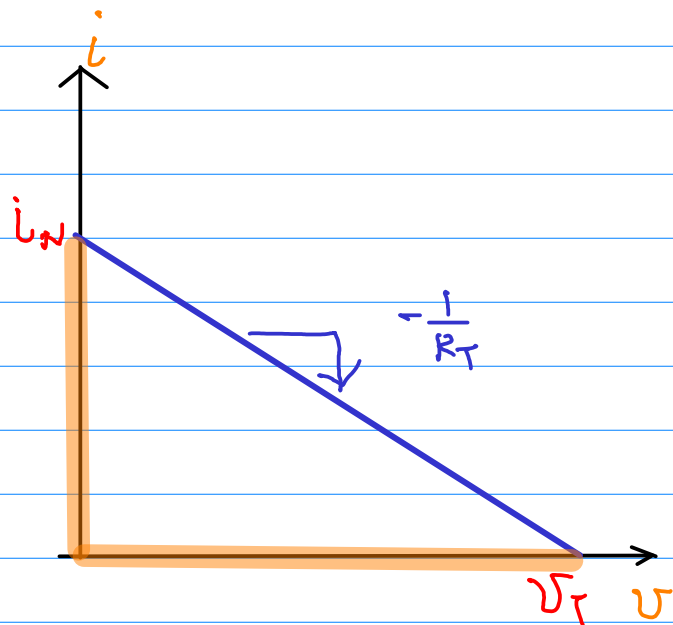


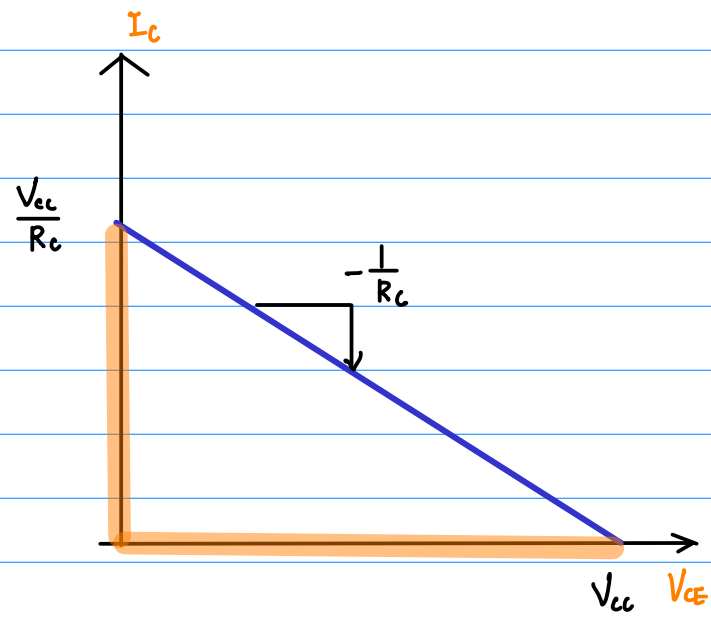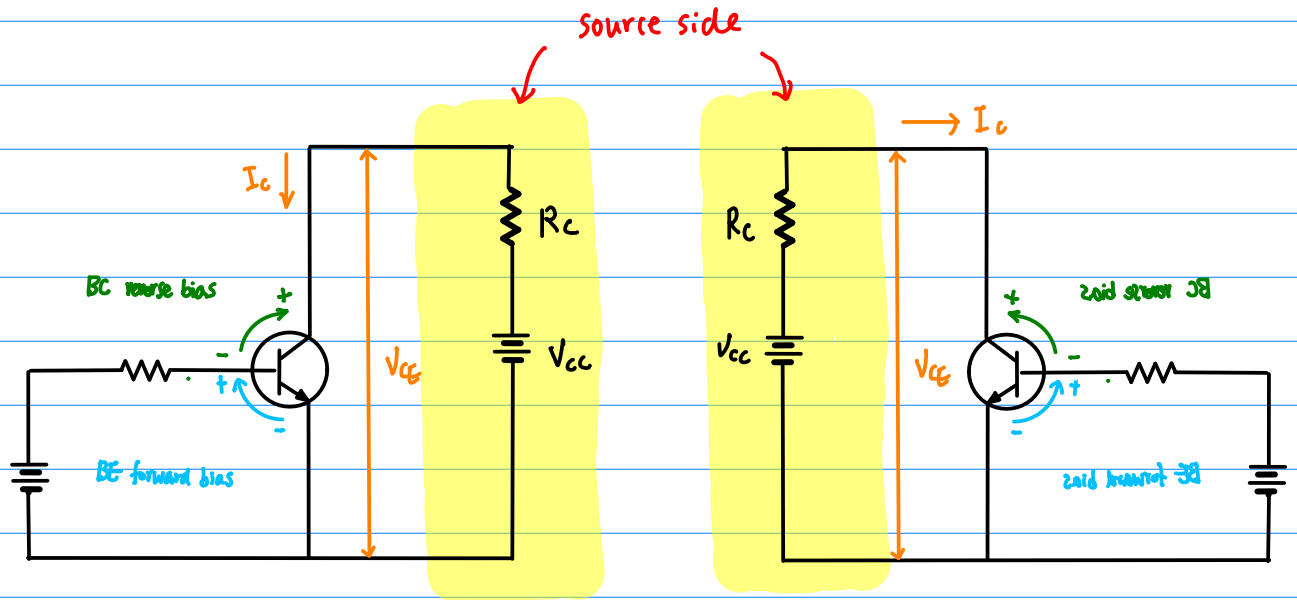

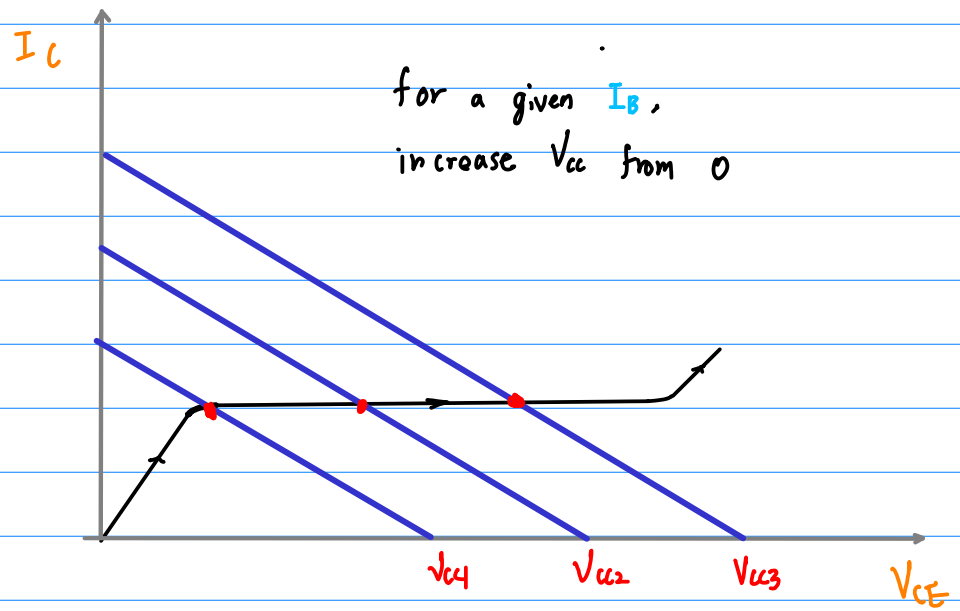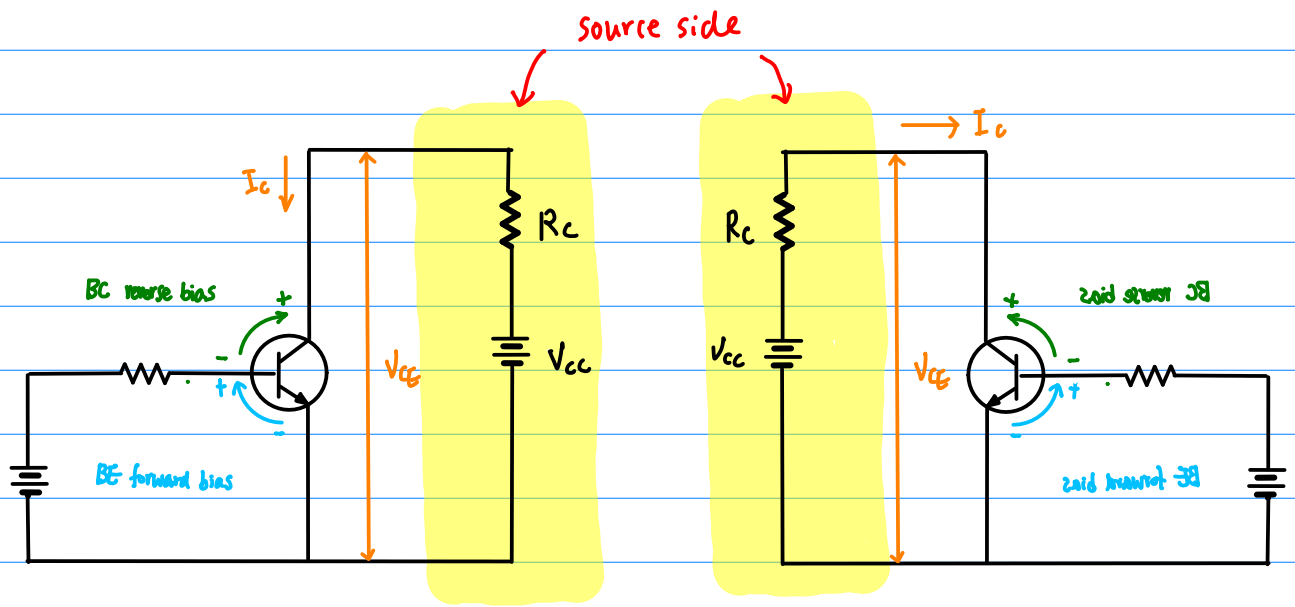


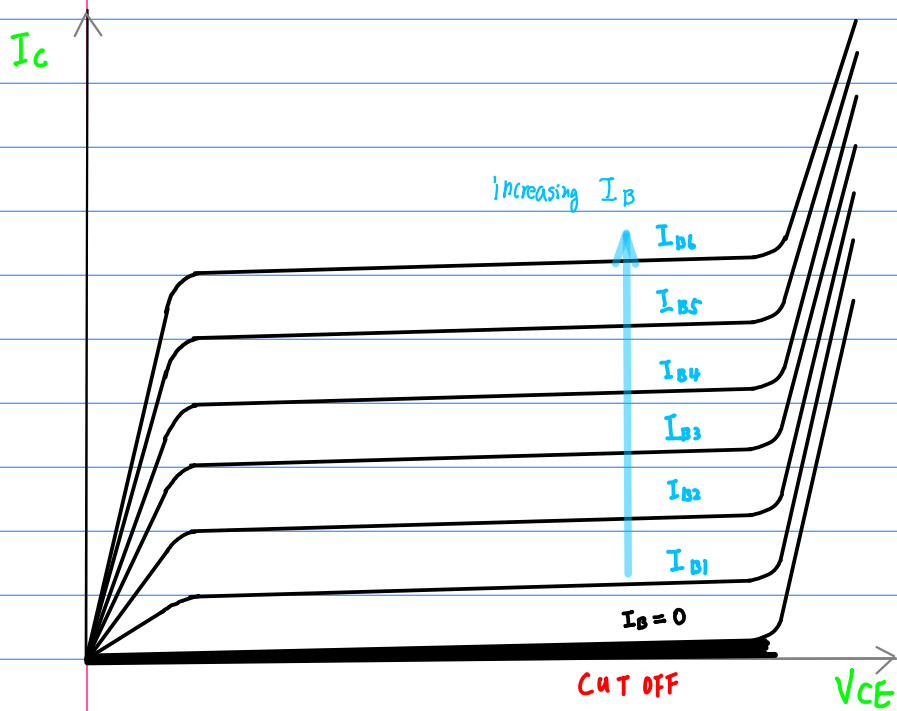
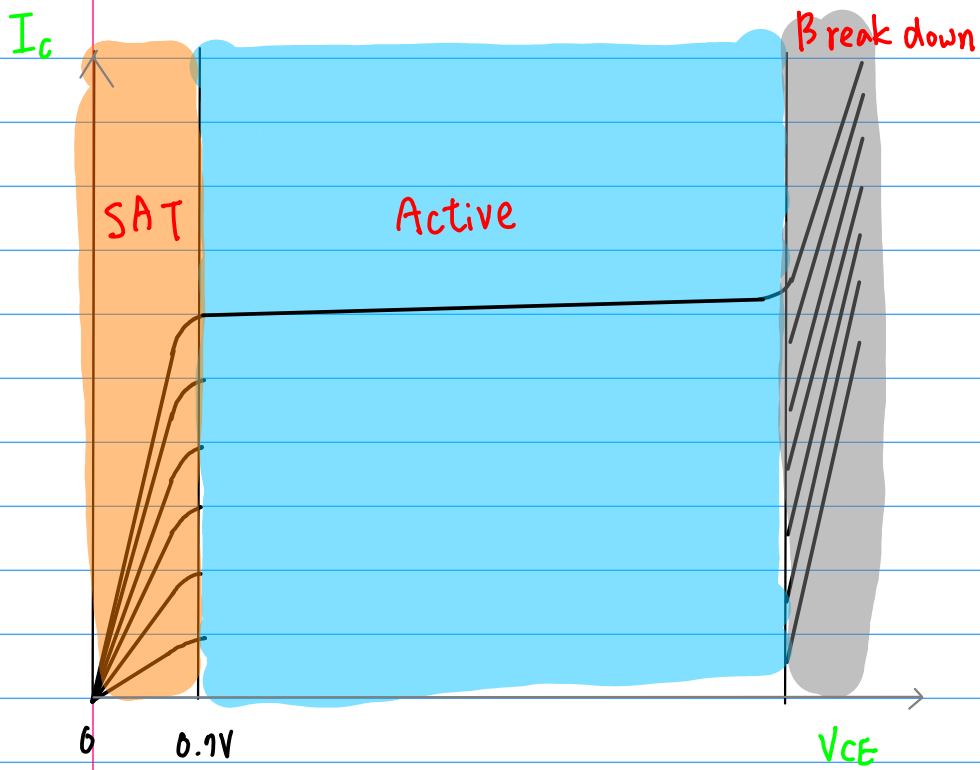


(A) At the origin

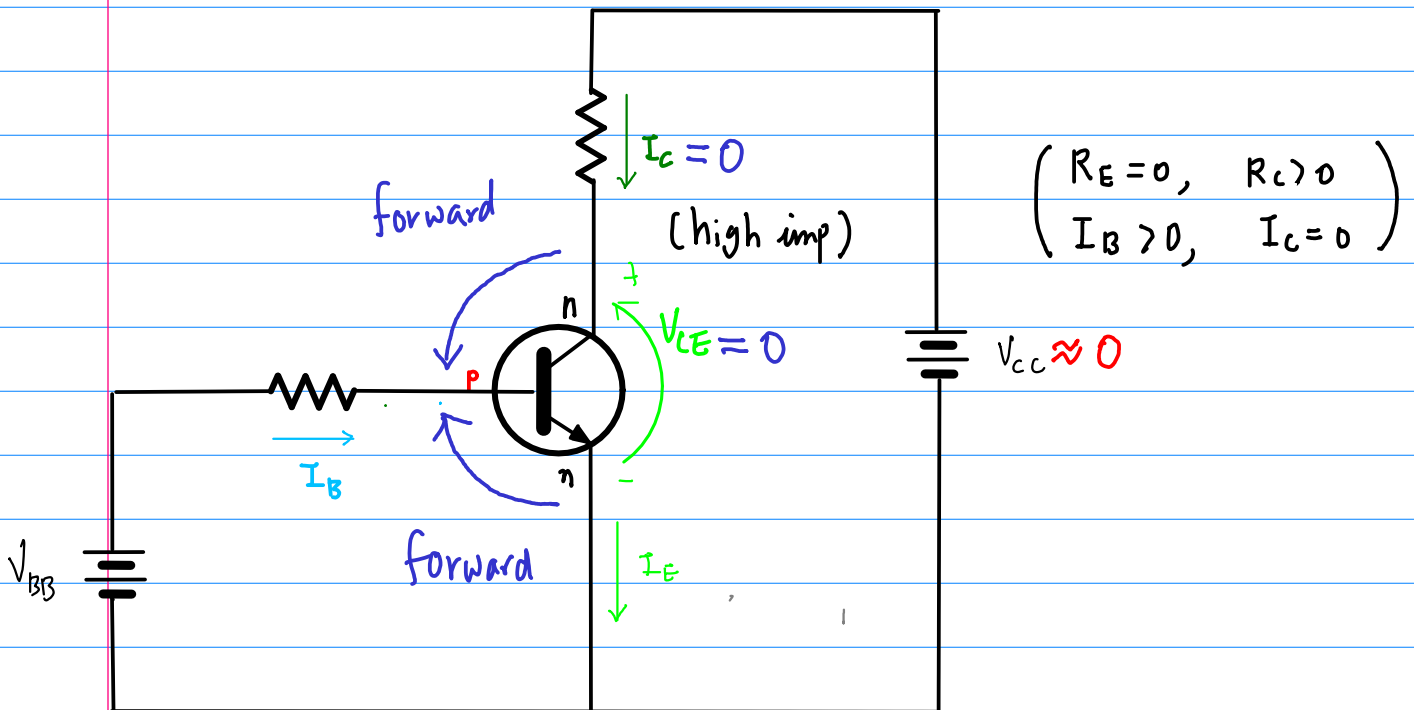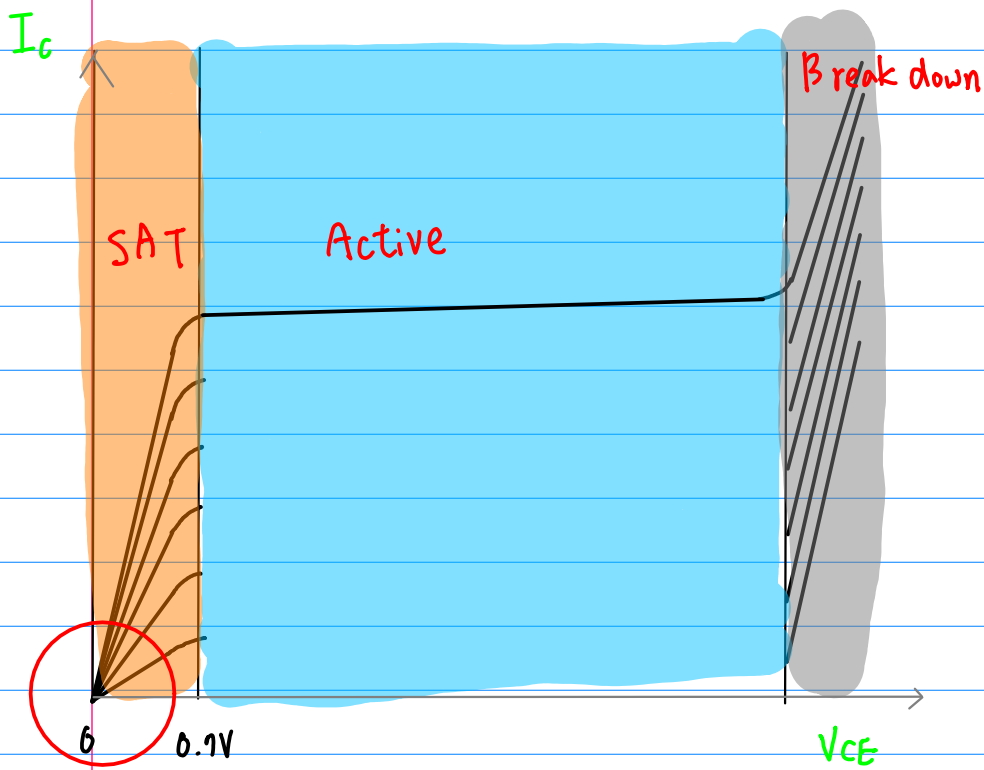


(A) - (B)

Saturation

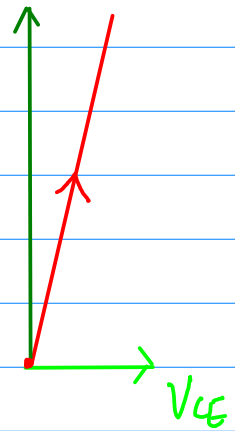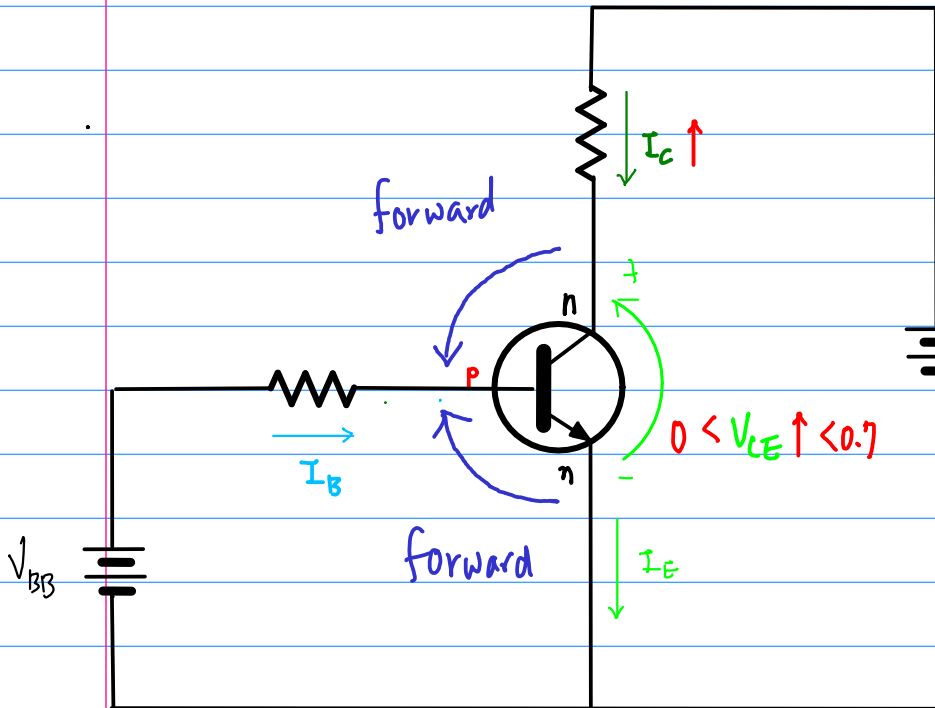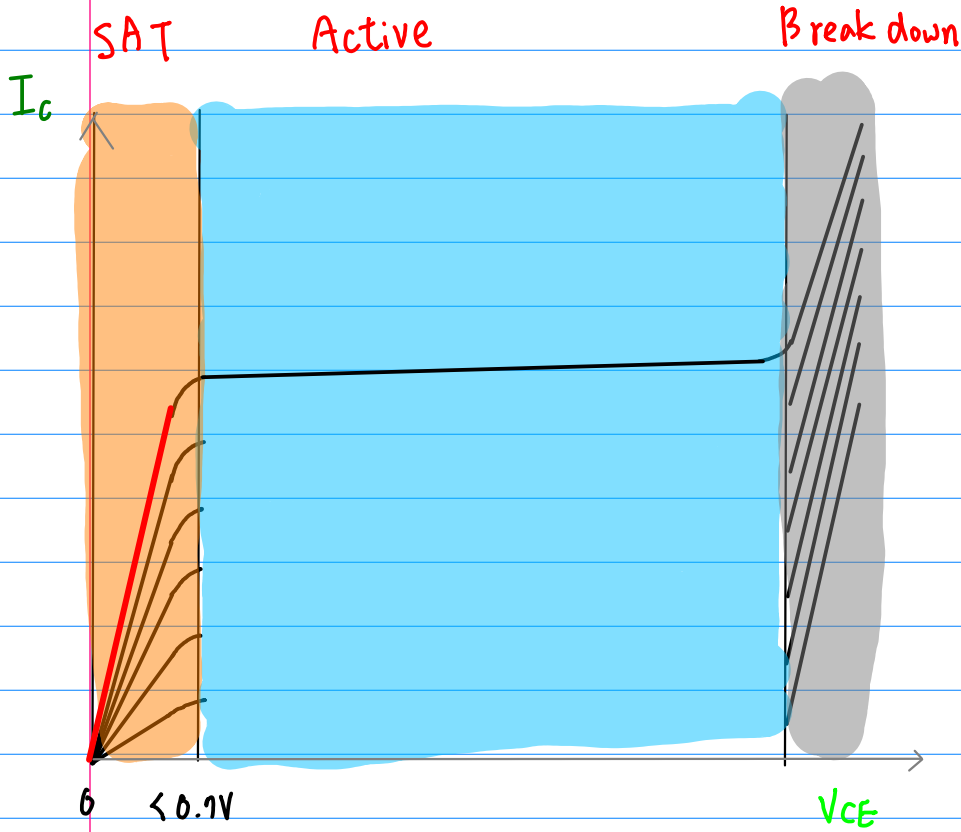



$I_c \uparrow$ large R_c large V_{drop}
 $V_{CE} \uparrow$ slowly small R_{ce} small V_{drop}

$V_{CE} < 0.7V$ for forward bias


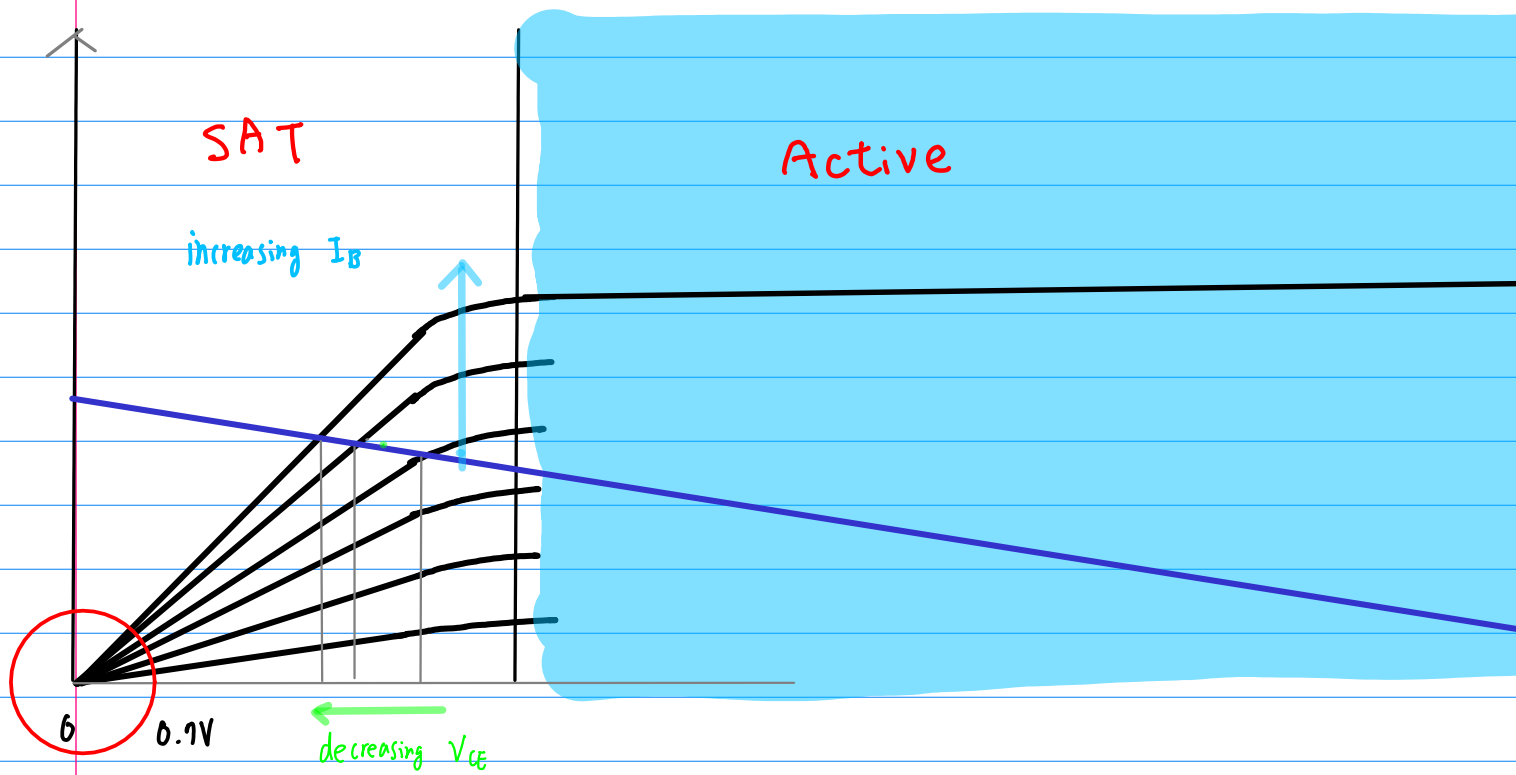


$I_B \uparrow \Rightarrow I_C \uparrow \Rightarrow \text{more } V_{\text{drop across } R_C}$
 $\Rightarrow V_{CE} \downarrow$

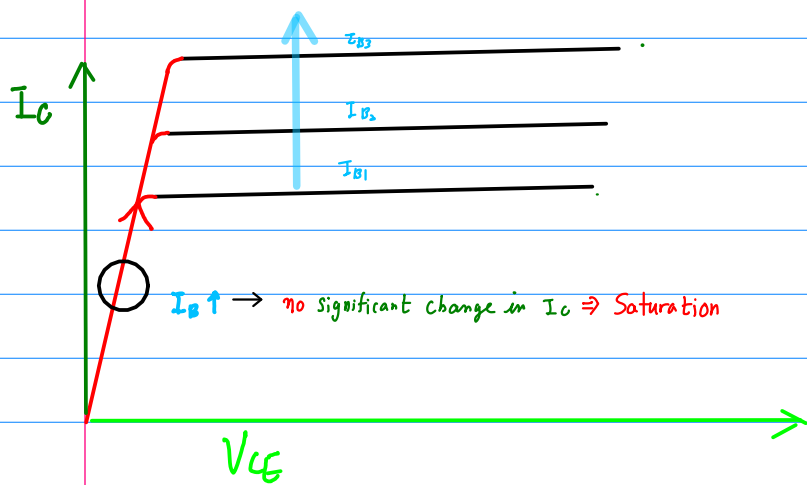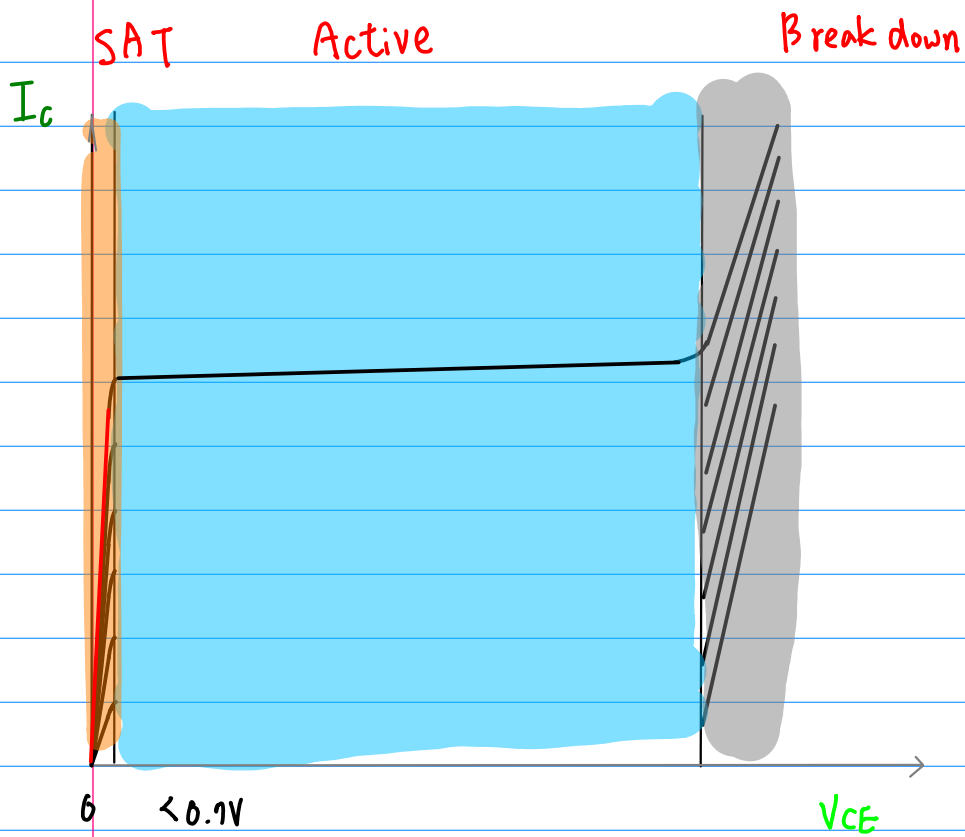
difference not much.. $V_{CE} \cong 0.3 \text{ V}$



(B) - (C) Active

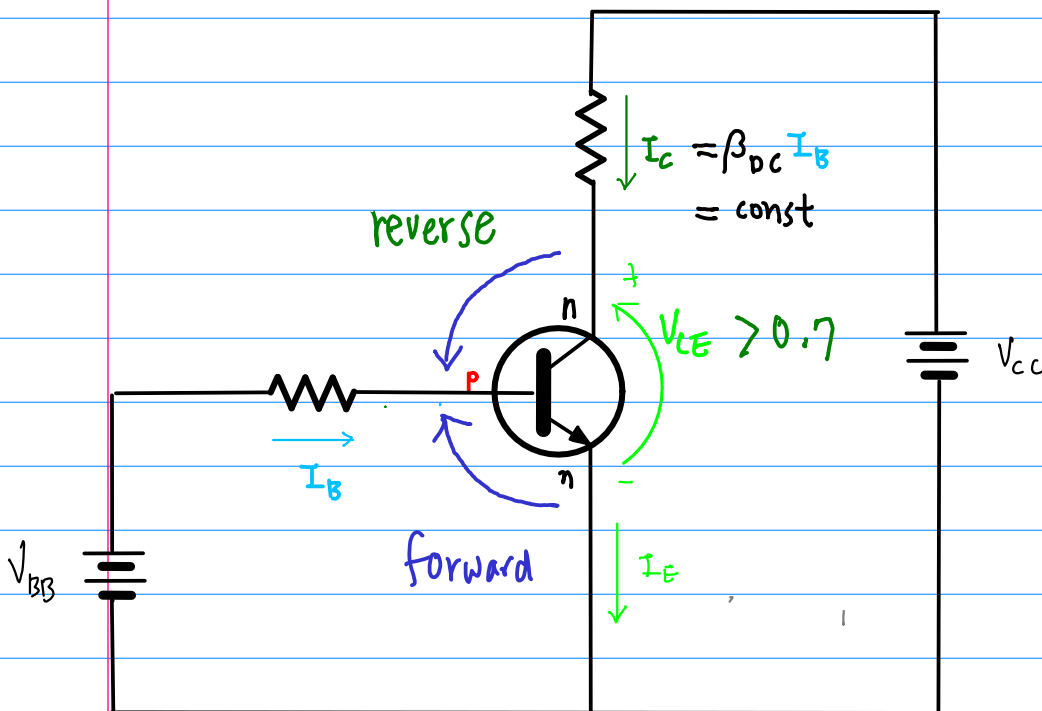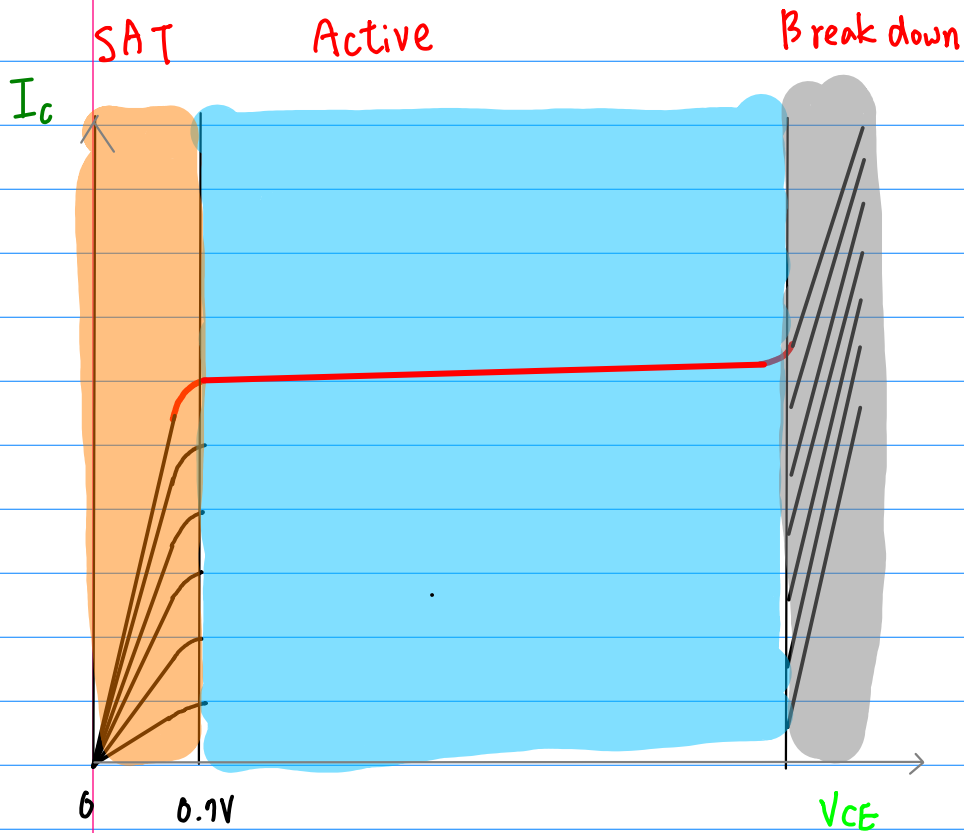


$$V_{CE} + V_{R_C} = V_{CC}$$

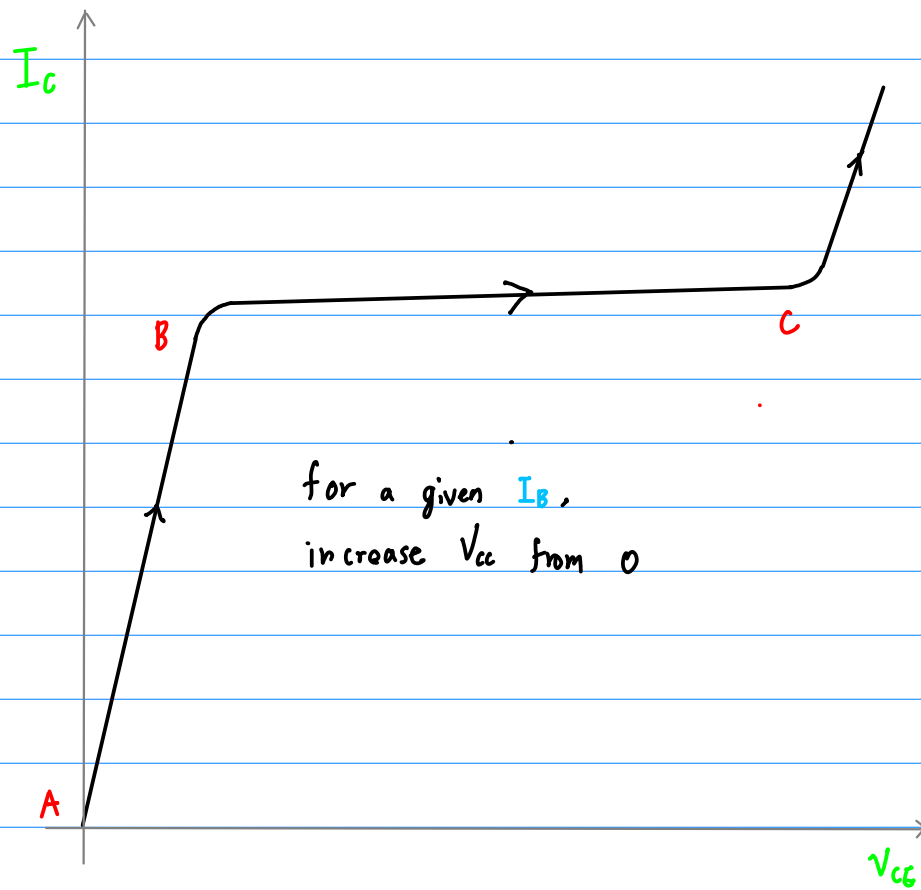

<http://www.physics.csbsju.edu/trace/CC.html>



(A) At the origin

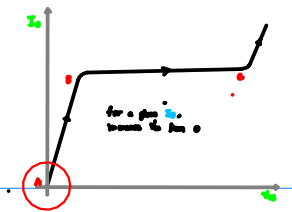

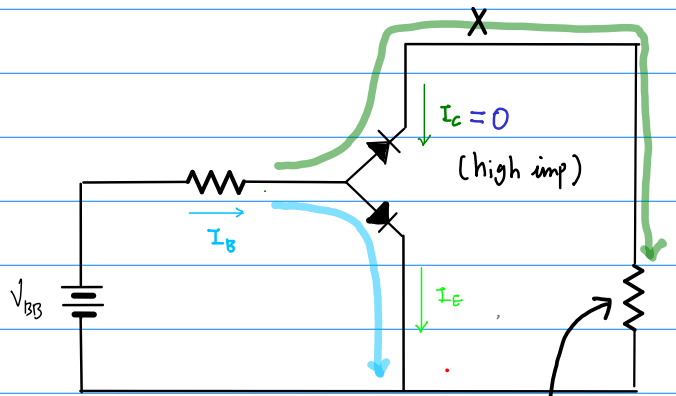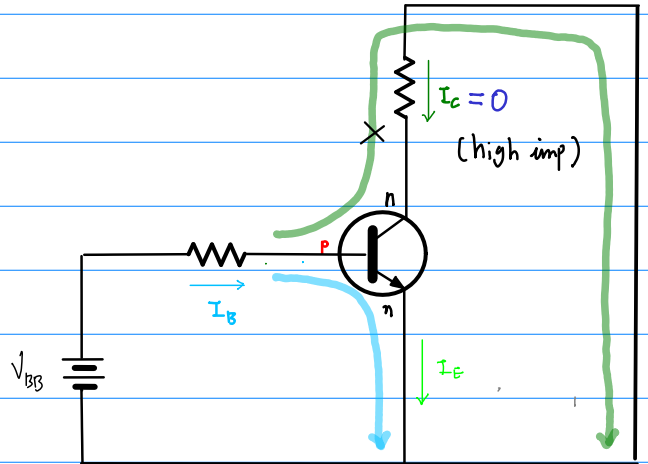(A) $V_{cc} \approx 0$



2 paths

B \rightarrow E very small R
 B \rightarrow C $(R_c) \rightarrow I_c = 0$



no voltage drop if $I_c = 0$
 $V_{BC} = V_{BE}$






$-V_{CB} = V_{BE}$

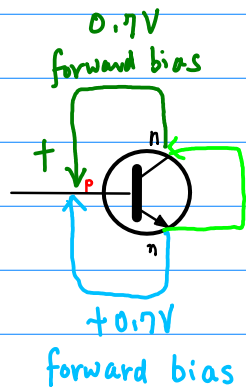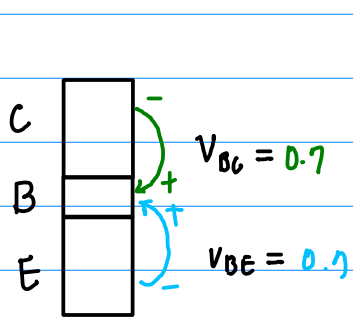

$V_{CE} = 0$ for saturation and $I_c = 0$

$V_{CE} = V_{CB} + V_{BE} = -V_{BC} + V_{BE} = -0.7 + 0.7 = 0$

(A)-(B) Saturation

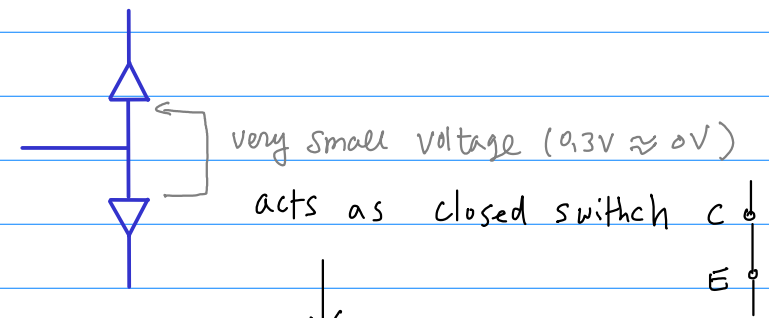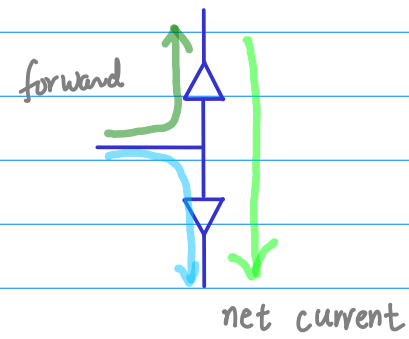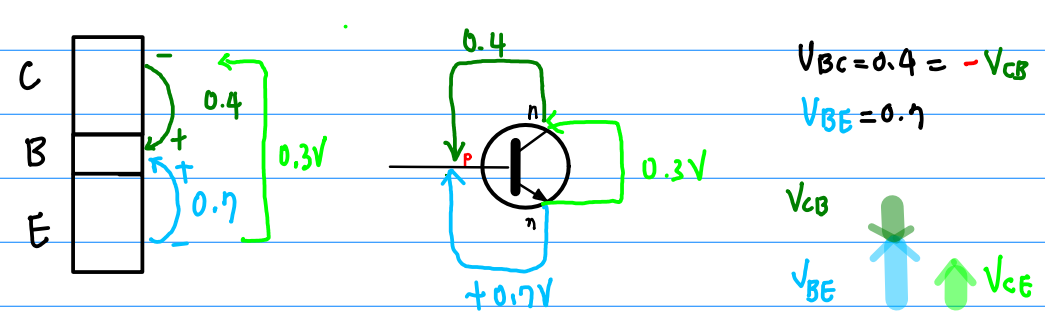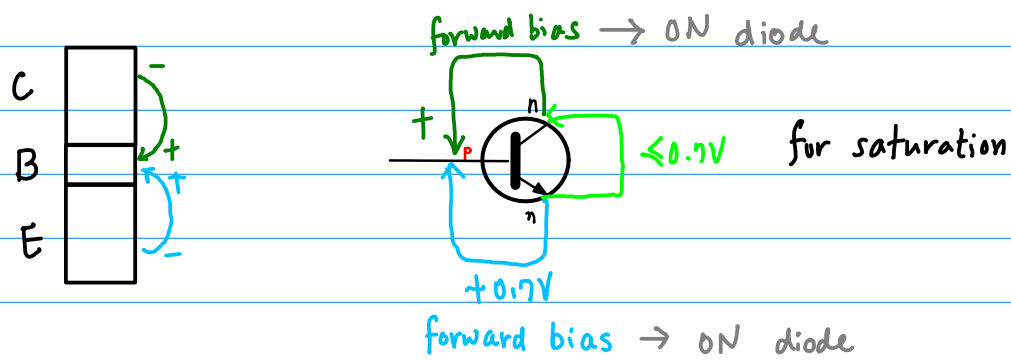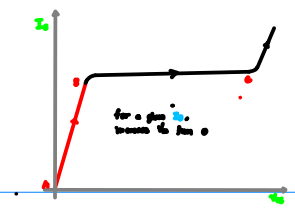

$$I_E = I_B + I_C \quad \text{difference}$$



$$I_E - I_C = I_B$$

most of V_{CC} will be on external R_C or R_E
 $V \uparrow \Rightarrow I \uparrow \rightarrow I_C, I_E$
 $\frac{V}{R} = I$ large


Comparatively large I_B
 difference current I_E small

(B) - (C)



Active (Linear)

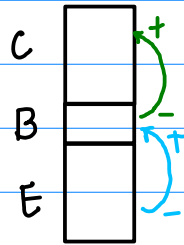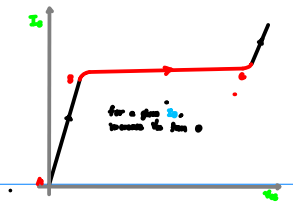

reverse bias

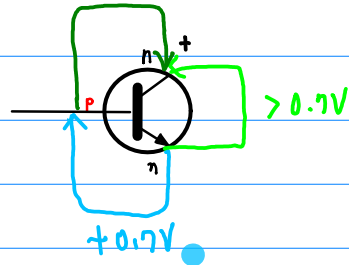

active (linear)

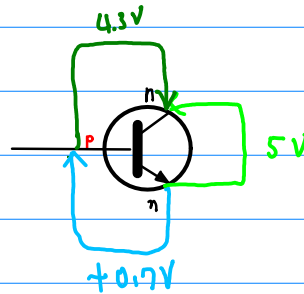
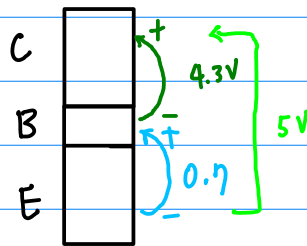



V_{CB}

V_{CE}




V_{BE}



reverse

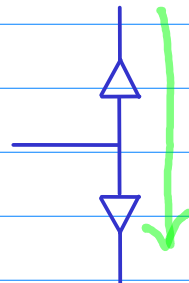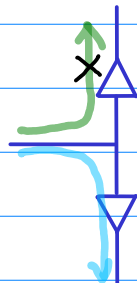

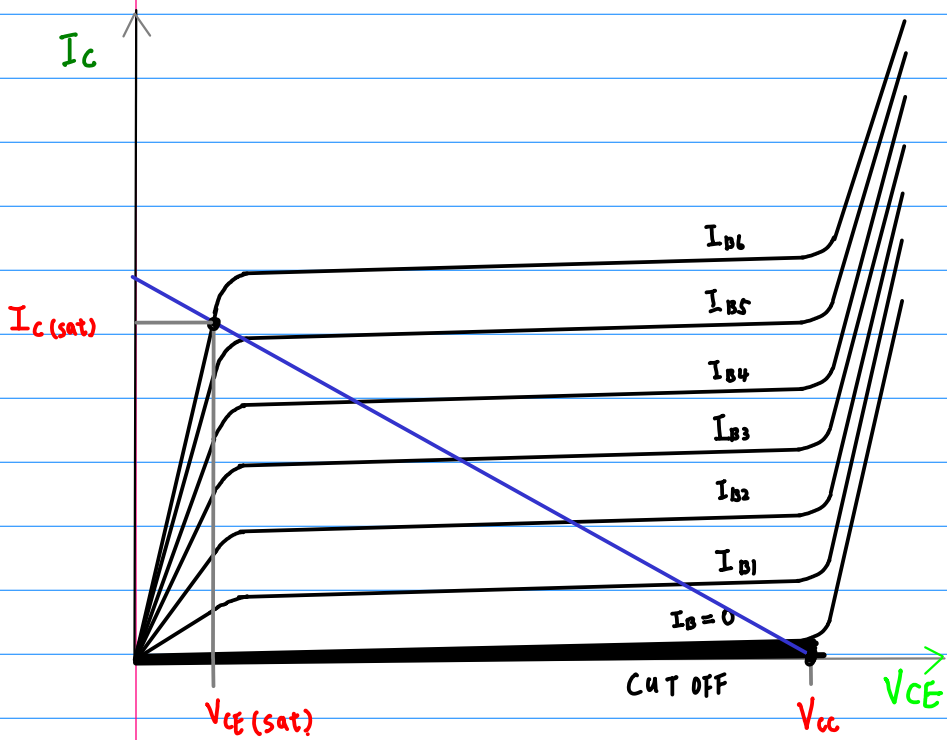

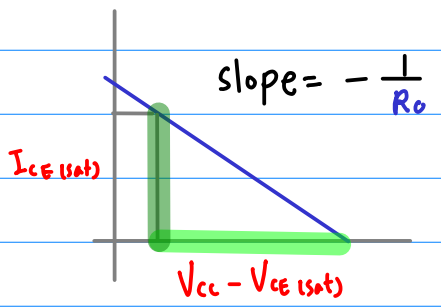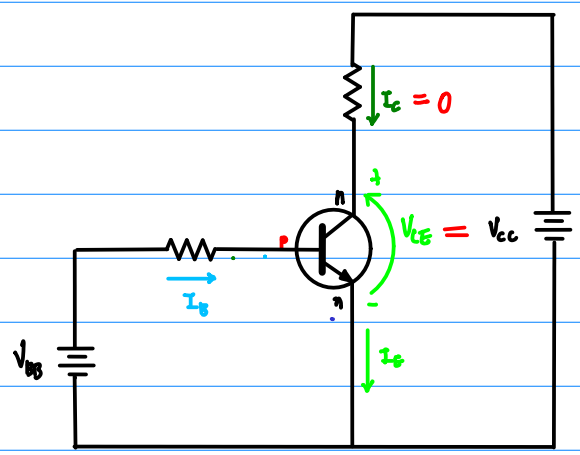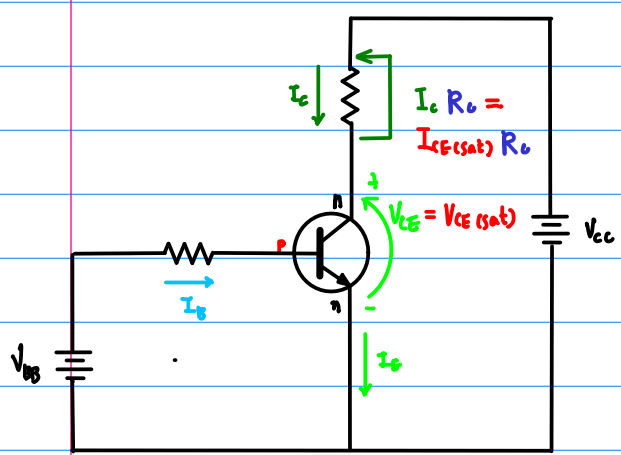
$$V_{cc} - V_{ce(sat)} = I_{c(sat)} R_c$$



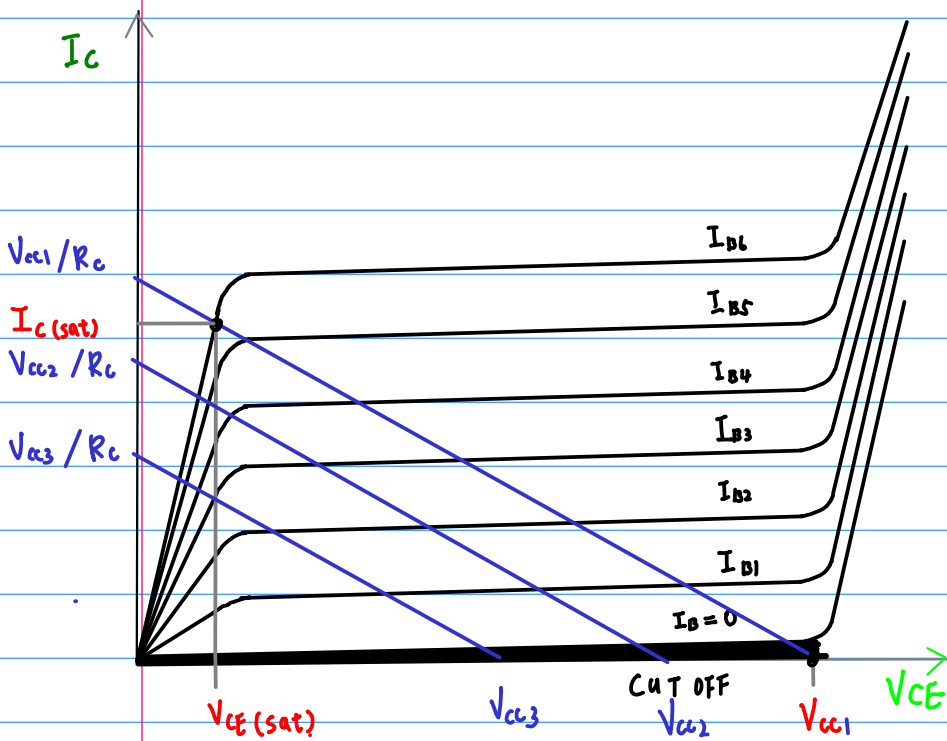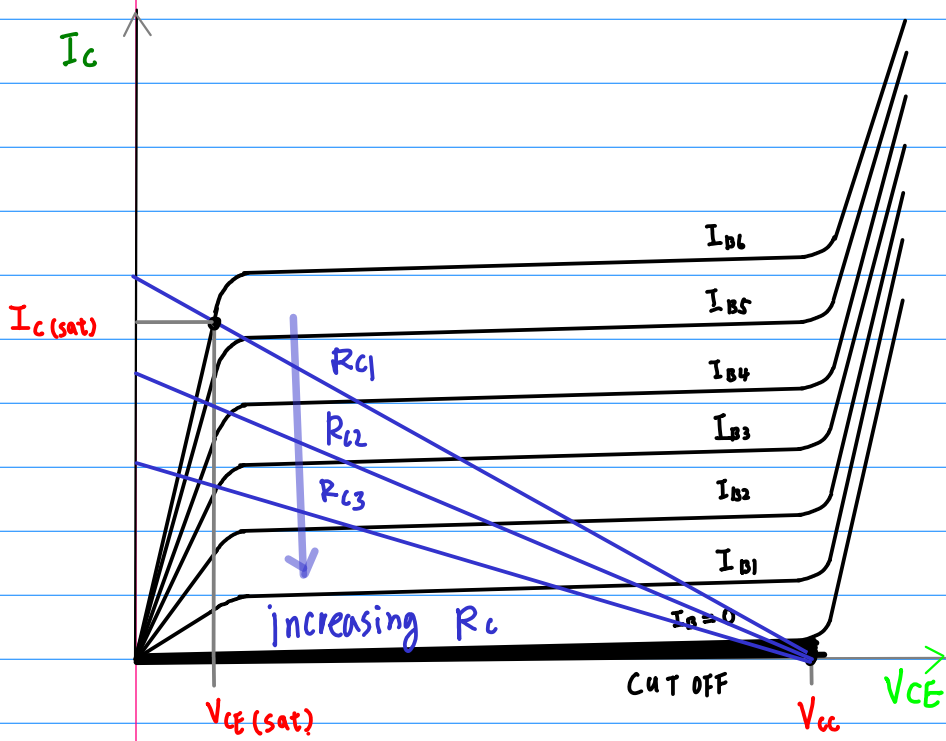

Why saturation

Active Region

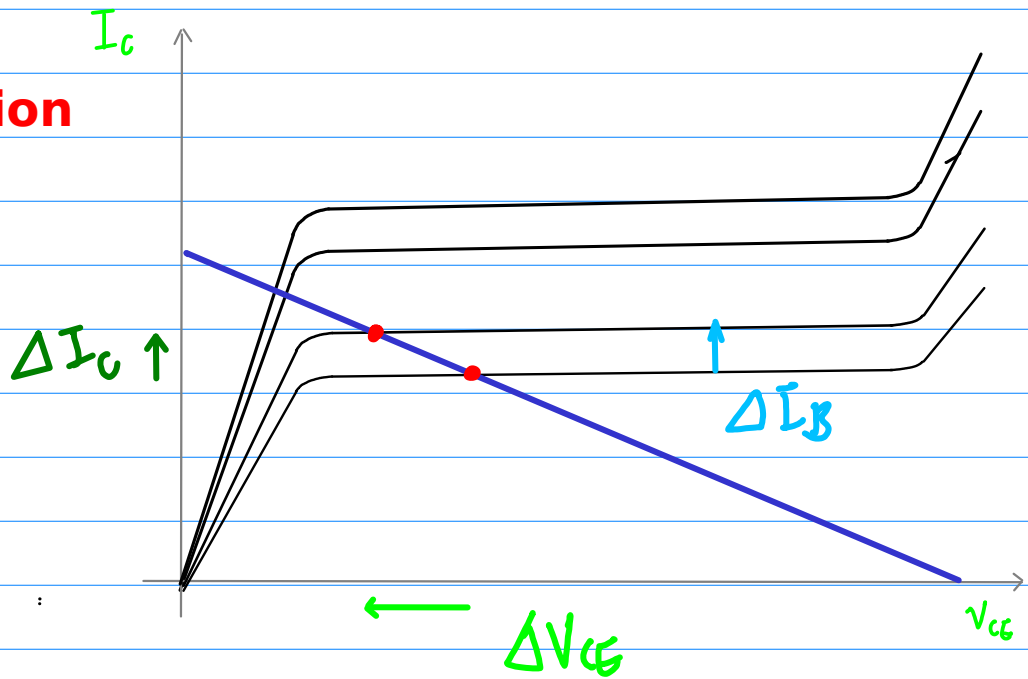

Saturation Region

very small change
no visible change
Saturated

