

FlipFlop Timing (3D)



Copyright (c) 2011-2013 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.


This document was produced by using OpenOffice and Octave.

Register

 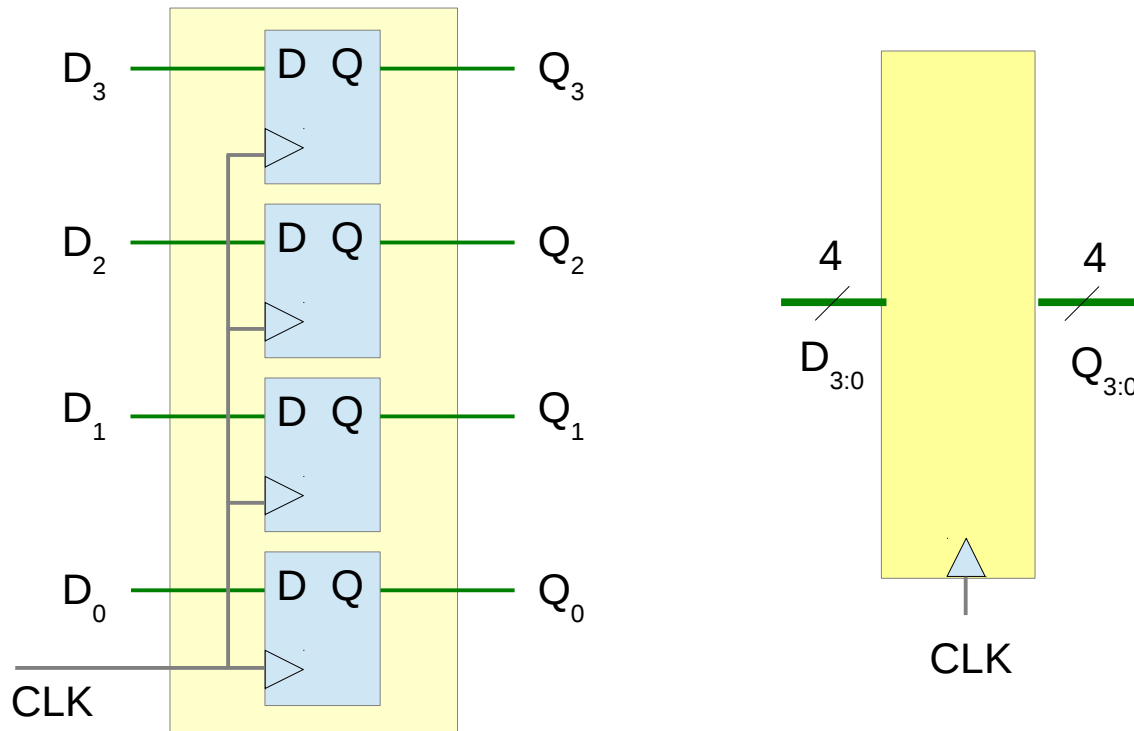


Types of Timing Diagrams

a timing diagram without delays

 

a timing diagram with delays

 

DFF Testbench

```
module dff(d, clk, rst, q, qb);
  input d, clk, rst;
  output q, qb;
  reg q;

  always @(posedge clk)
  begin
    if (~rst) q = 0;
    else q = d;
  end

  assign qb = ~q;
endmodule
```

Nonblocking Assignments <=

Blocking Assignments =

```
initial
begin
  clk =0;
  d =0;
  rst =1;
  rst =0;
  #20 rst = 1;

  #10 d <= 1;
  #10 d <= 0;
  #10 d <= 1;
  #10 d <= 0;
  #10 d <= 1;
  #10 d <= 1;

  $finish;
end
```

```
#10 d = 1;
#10 d = 0;
#10 d = 1;
#10 d = 0;
#10 d = 1;
#10 d = 1;
```

```
`timescale 1ns/100ps

module dff_tb;

reg d, clk, rst;

dff U1 (d, clk, rst, q, qb);

always #10 clk = ~clk;

initial
begin
  $dumpfile("test.vcd");
  $dumpvars(0, dff_tb);
end

endmodule
```

Testbench with Nonblocking Assignments

```
module dff(d, clk, rst, q, qb);
  input d, clk, rst;
  output q, qb;
  reg q;

  always @(posedge clk)
  begin
    if (~rst) q = 0;
    else q = d;
  end

  assign qb = ~q;
endmodule
```

```
initial
begin
    clk =0;
    d =0;

    rst =1;
    rst =0;
    #20 rst = 1;

    #10 d <= 1;
    #10 d <= 0;
    #10 d <= 1;
    #10 d <= 0;
    #10 d <= 1;
    #10 d <= 1;
    $finish;
end
```


```
`timescale 1ns/100ps

module dff_tb;

reg d, clk, rst;

dff U1 (d, clk, rst, q, qb);

always #10 clk = ~clk;




initial
begin
    $dumpfile("test.vcd");
    $dumpvars(0, dff_tb);
end

endmodule
```

DFF Testbench Waveforms

Nonblocking Assignments

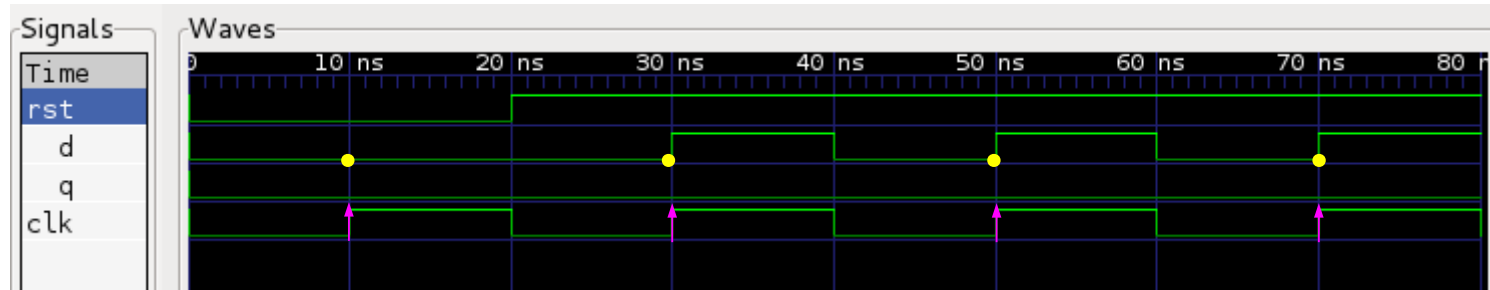
```
#10 d <= 1;  
#10 d <= 0;  
#10 d <= 1;  
#10 d <= 0;  
#10 d <= 1;  
#10 d <= 1;
```



samples the unchanged d input values at the posedge of clk

Blocking Assignments

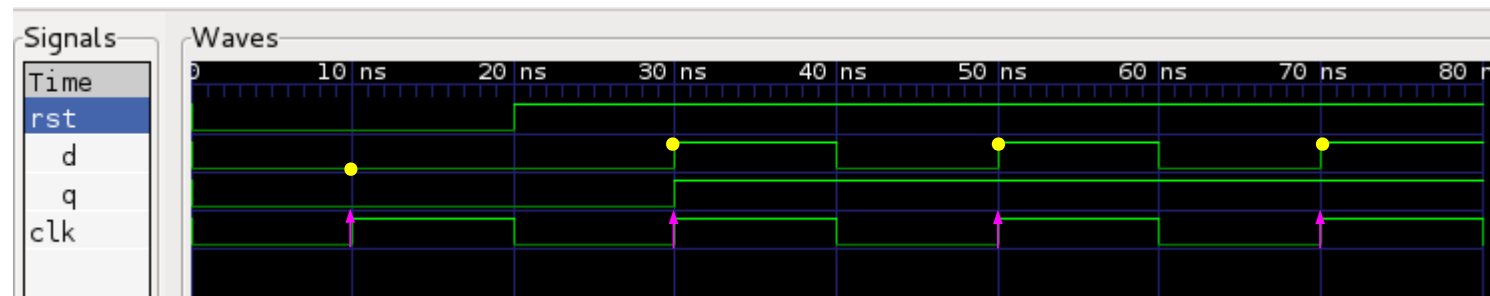
```
#10 d = 1;  
#10 d = 0;  
#10 d = 1;  
#10 d = 0;  
#10 d = 1;  
#10 d = 1;
```




samples the changed d input values at the posedge of clk

Blocking Assignments
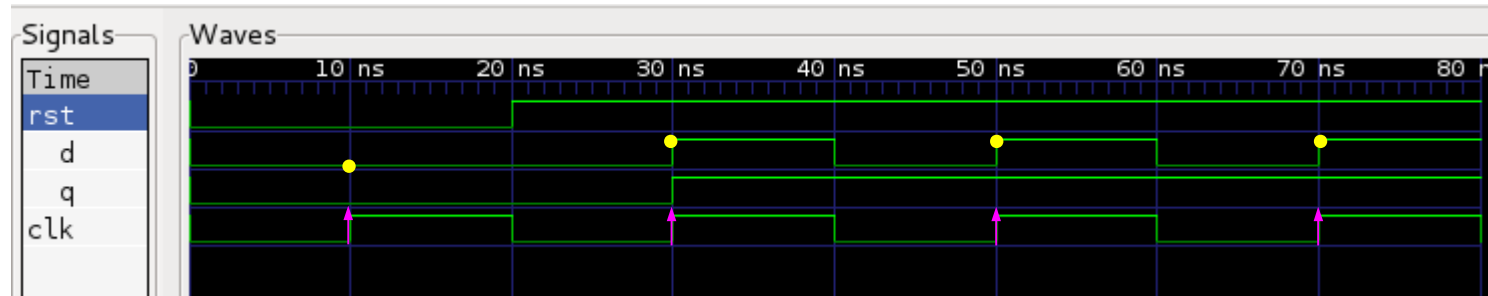
```
#10 d = 1;  
#10 d = 0;  
#10 d = 1;  
#10 d = 0;  
#10 d = 1;  
#10 d = 1;
```



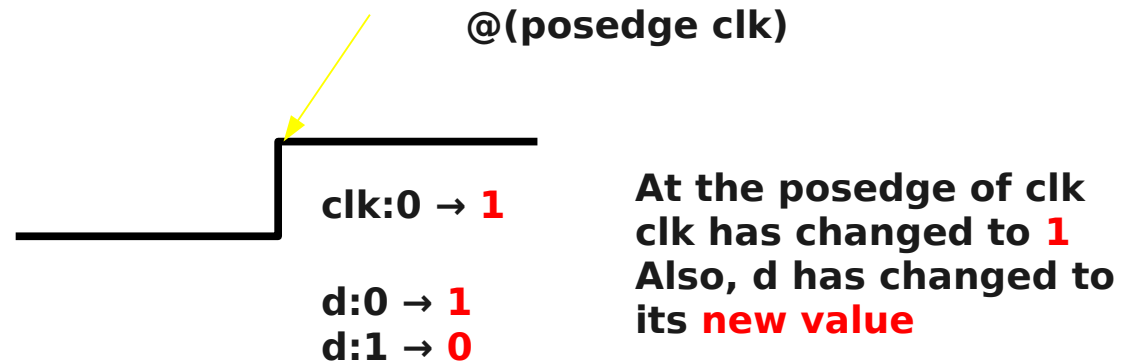
```
always @(posedge clk)  
begin  
  if (~rst) q = 0;  
  else    q = d;  
end
```



Nonblocking Assignments

Nonblocking Assignments
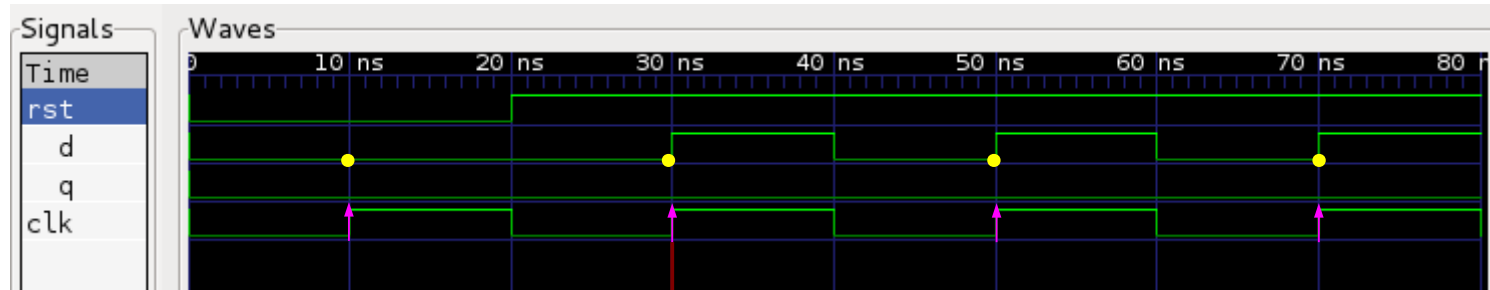
```
#10 d <= 1;  
#10 d <= 0;  
#10 d <= 1;  
#10 d <= 0;  
#10 d <= 1;  
#10 d <= 1;
```



In each of time slot which is delayed by 10 time units, there is only **one** assignment that can be scheduled simultaneously,

samples the unchanged d input values at the posedge of clk


- (1) Allowing scheduling of assignments **without waiting for its completion**
- (2) Executed **last** in the time step in which it is scheduled (after all blocking assignments' execution)

Regular Events	Nonblocking Update Events	Monitor Events
----------------	---------------------------	----------------



- Evaluate
- Update

So, the input d update is done after the posedge clk


FF Timing - Input and Output Delays

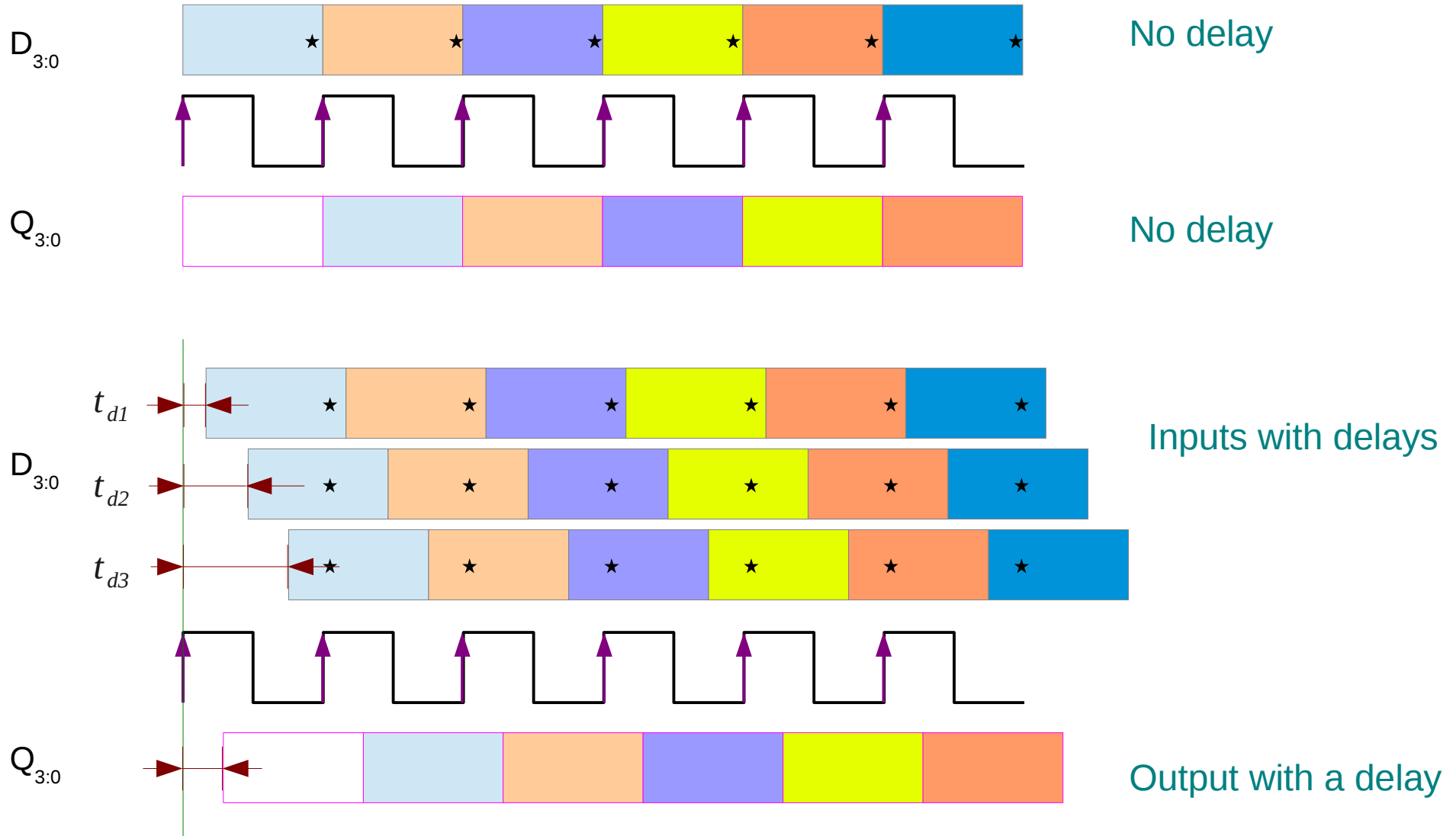



Reg to Reg Timing

  



Clock Skew

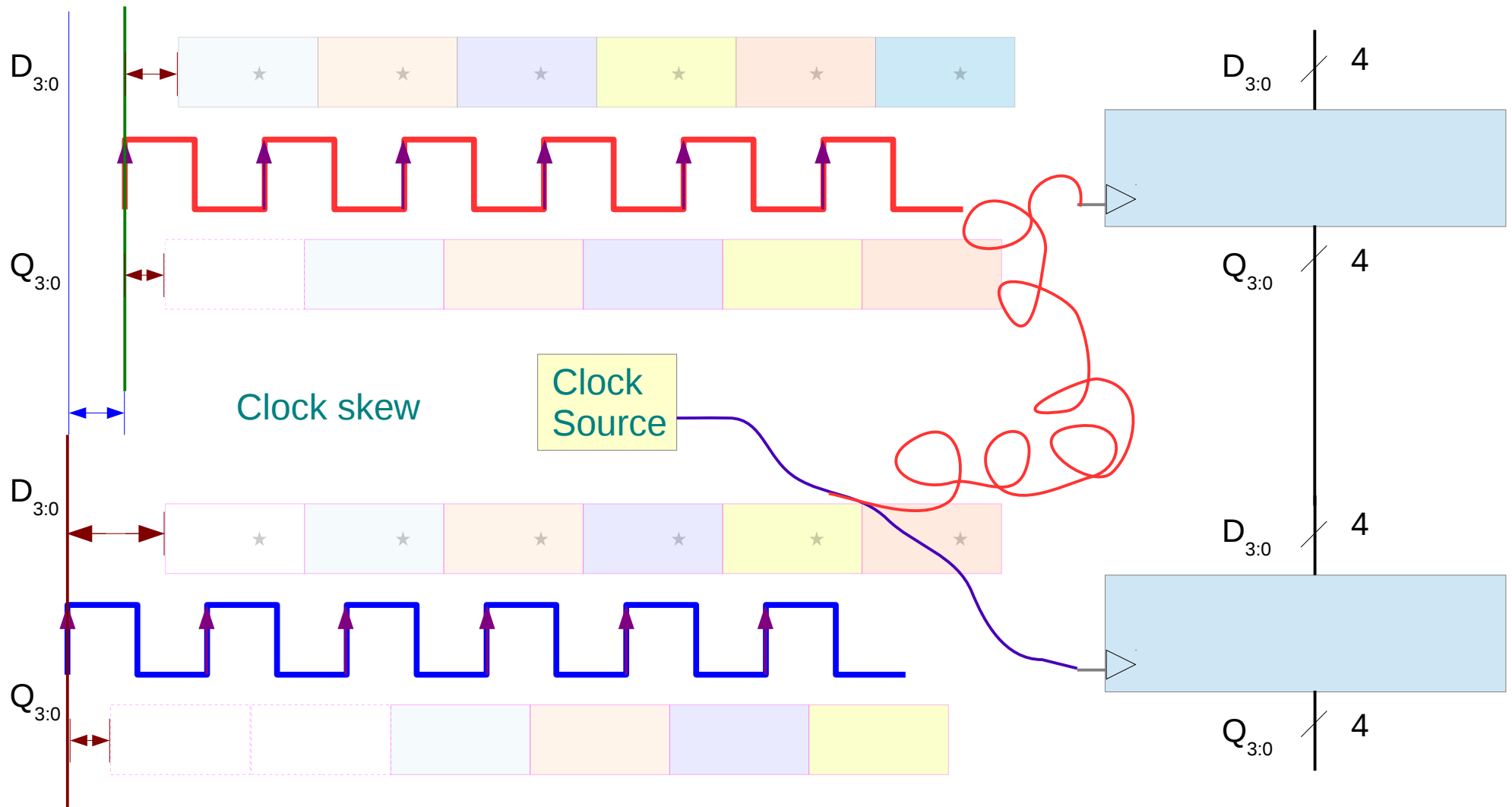



Path Delay

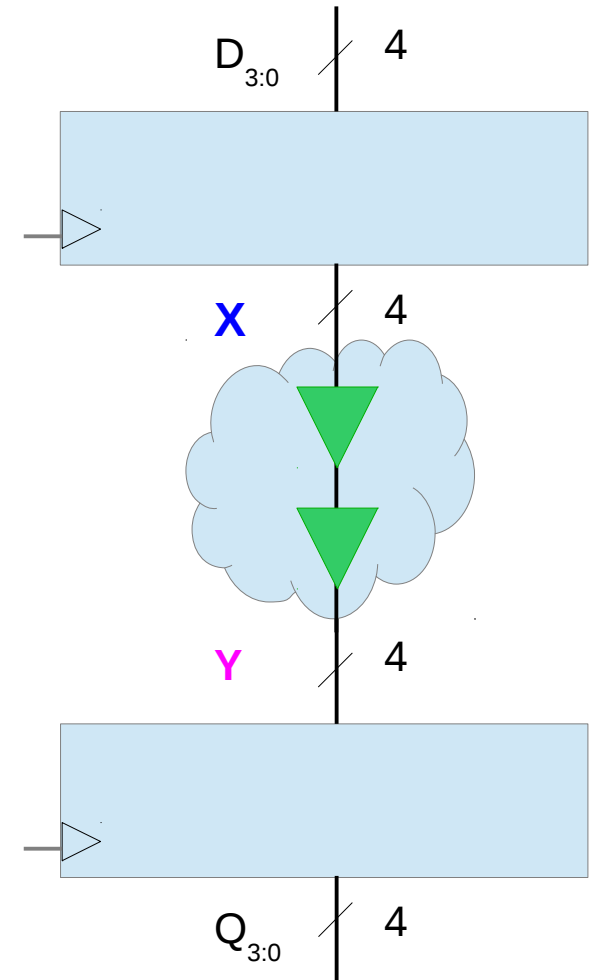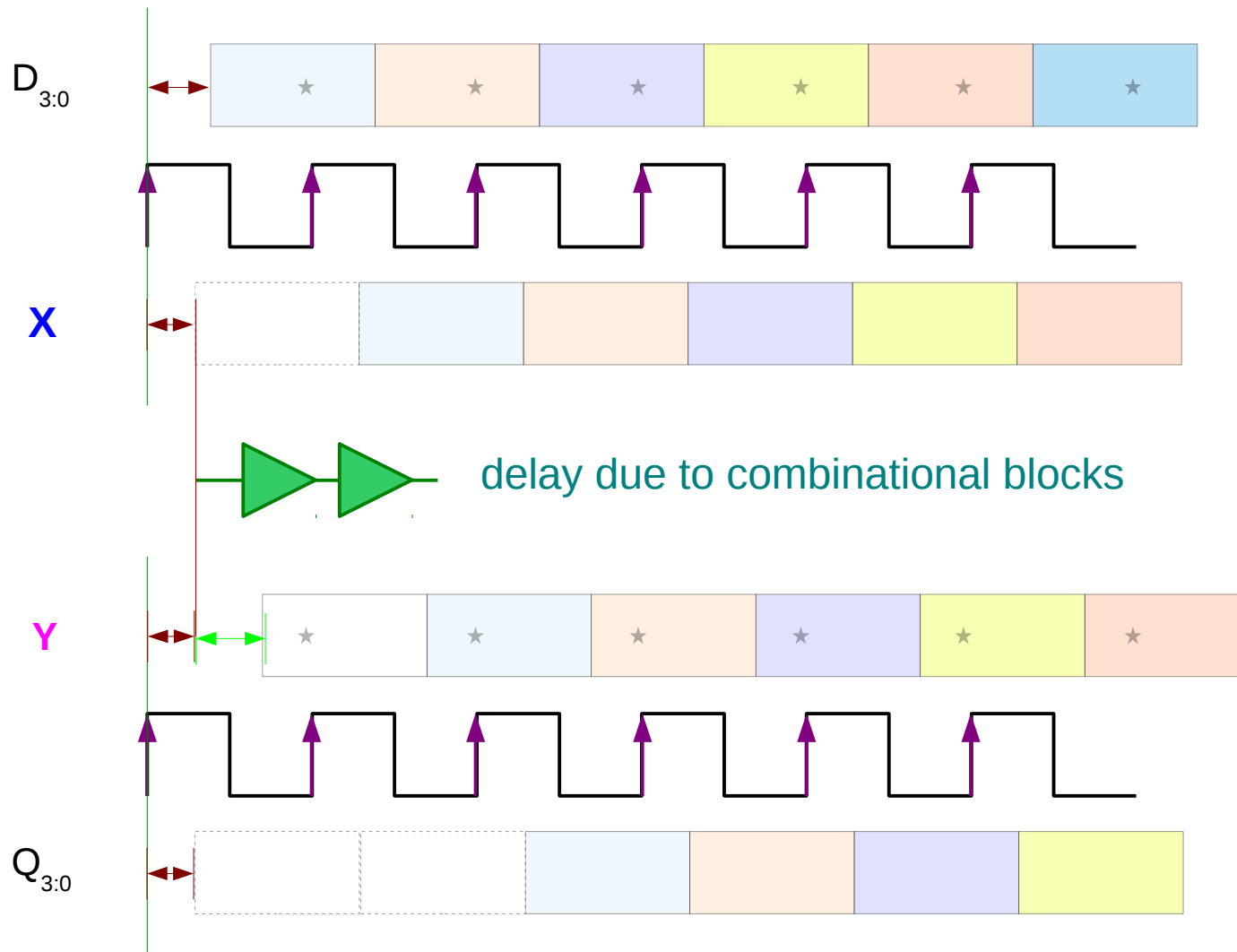



Setup & Hold Time (1)

  

Setup & Hold Time (2)



 
 


Clock Gating

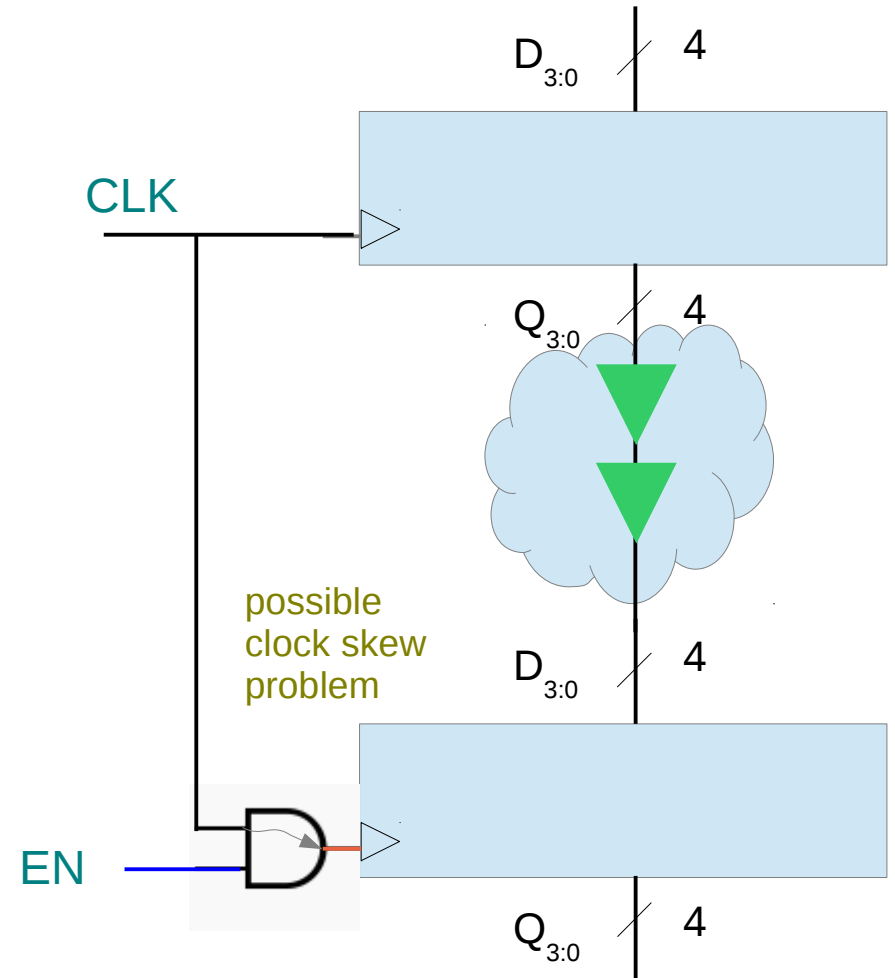 

Register Timing

NOR-based SR Latch

    

References

- [1] <http://en.wikipedia.org/>
- [2] <http://planetmath.org/>
- [3] M.L. Boas, "Mathematical Methods in the Physical Sciences"