

R	Clk	D	Q	Q'
0	X	X	0	1
1	r	0	0	1
1	r	1	1	0


 
 


Fig 6.1

 



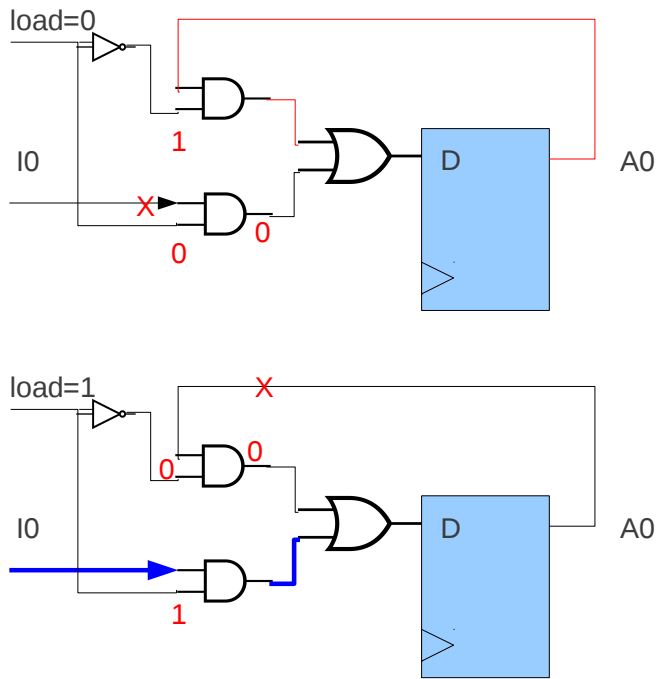
 
 
 
 


Fig 6.2 4-bit register with parallel load

 

Sheet1

 



 
 
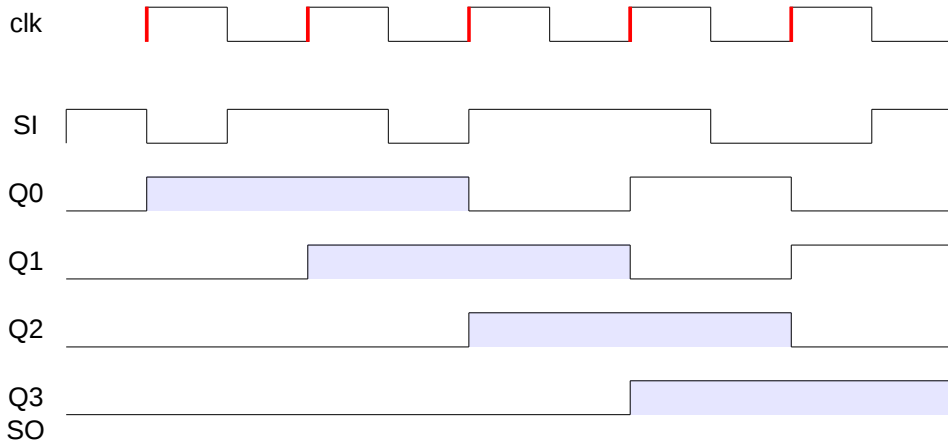
 
 
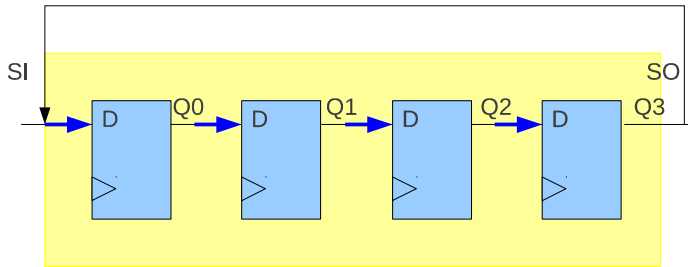


Fig 6.4

 

Sheet1

 

ShiftControl



CLK.ShiftControl

