

# RLC Transient Response (H.1)

## 1st Order Circuit

20150720


The necessities in Electric Circuit  
wikiversity

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".
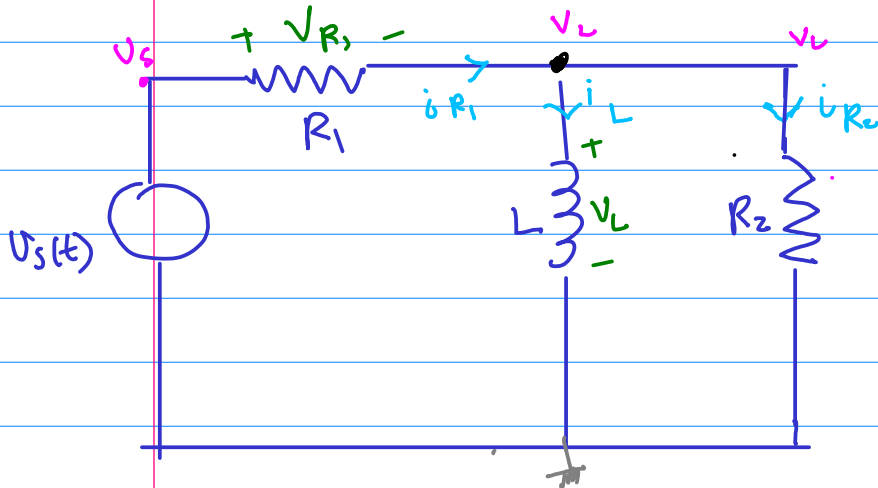
# DC Steady State Solution

변하지 않는 input에 대한 Steady state 출력 값  
Constant input



$$v_L = L \frac{di_L}{dt}$$

KCL  $i_{R_1} - i_L - i_{R_2} = 0$

$$\frac{v_s - v_L}{R_1} - i_L - \frac{v_L}{R_2} = 0$$

$$\frac{v_s}{R_1} - \frac{L}{R_1} \frac{di_L}{dt} - i_L - \frac{L}{R_2} \frac{di_L}{dt} = 0$$

$$-\left(\frac{L}{R_1} + \frac{L}{R_2}\right) \frac{di_L}{dt} - i_L + \frac{v_s}{R_1} = 0$$

$$\boxed{\frac{L(R_1 + R_2)}{R_1 R_2}} \frac{di_L}{dt} + i_L = \boxed{\frac{1}{R_1}} v_s$$


$$\boxed{\tau} \frac{dx}{dt} + x(t) = \boxed{K_s} F$$

$$\boxed{\frac{di_L}{dt} + \frac{R_1 R_2}{L(R_1 + R_2)} i_L = \frac{R_2}{L(R_1 + R_2)} v_s}$$

$$\frac{L(R_1 + R_2)}{R_1 R_2} \frac{di_L}{dt} + i_L = \frac{1}{R_1} v_S$$

$$\tau \frac{dx}{dt} + |x(t)| = K_s \bar{F}$$

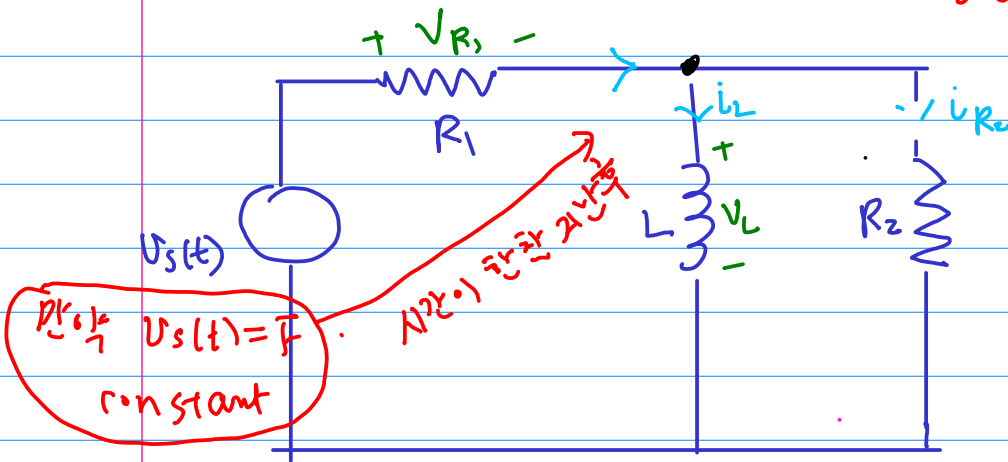흐르는 전류가 일정 (변함 X)  $\rightarrow \frac{di_L}{dt} = 0$






$v_S(t) = \bar{F}$   
 constant

$$\frac{L(R_1 + R_2)}{R_1 R_2} \frac{di_L(\infty)}{dt} + i_L(\infty) = \frac{1}{R_1} \bar{F}$$

$$\tau \frac{dx(\infty)}{dt} + |x(\infty)| = K_s \bar{F}$$

$i_L(\infty) = \frac{1}{R_1} \bar{F}$

$\boxed{DC}$  steady state 2x 6x

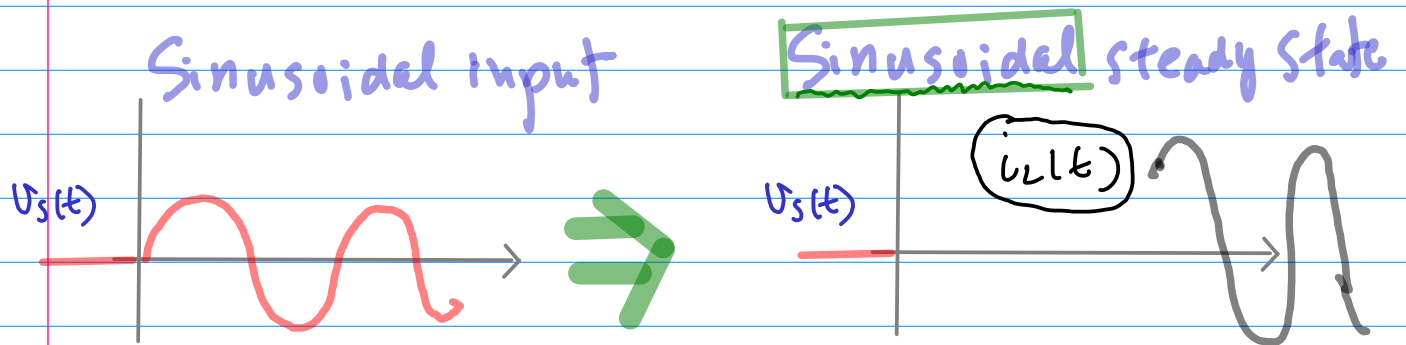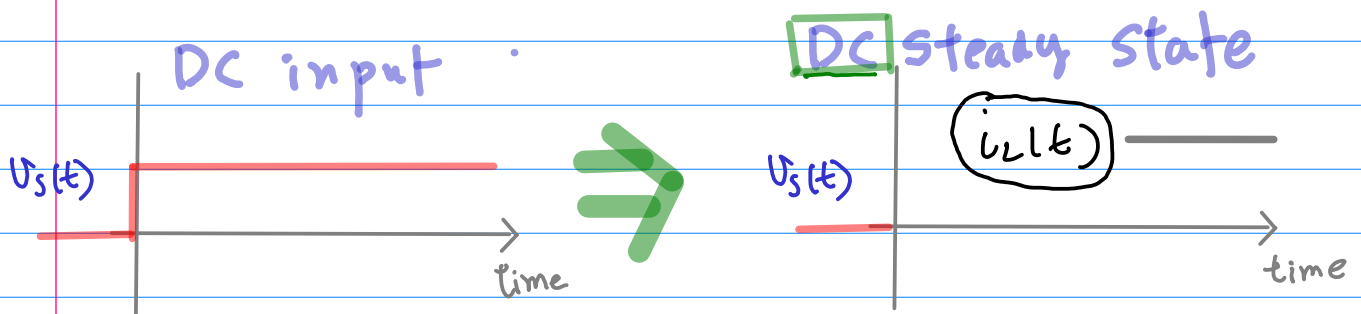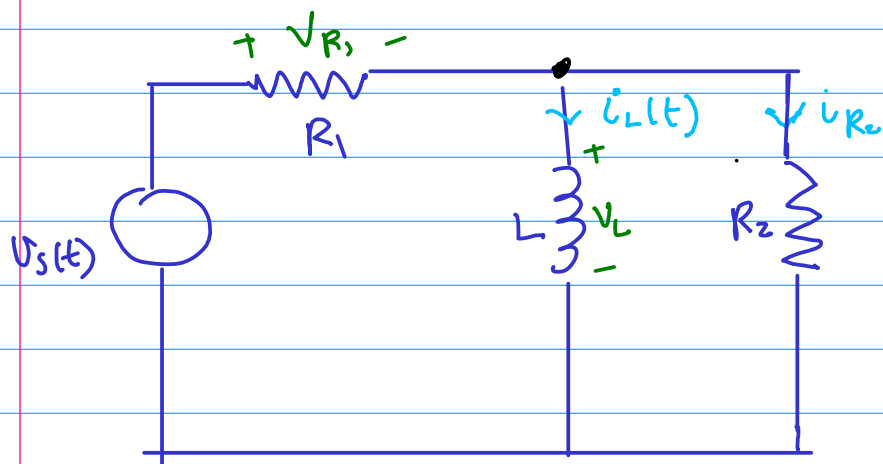

phasor  
+  
Impedance

# DC Steady state



<p>at <math>t = \infty</math> <math>\frac{dV_c(t)}{dt} = 0</math></p> <p><math>\rightarrow i_c(\infty) = 0</math></p>	<p>at <math>t = \infty</math> <math>\frac{dI_L(t)}{dt} = 0</math></p> <p><math>\rightarrow V_L(\infty) = 0</math></p>
<p>at <math>t = \infty</math></p>	<p>at <math>t = \infty</math></p>

$$\tau \left( \frac{dx}{dt} \right) + 1 x(t) = K_s F \quad x(\infty) = \underline{K_s F}$$

$$\frac{1}{\omega_0^2} \left( \frac{d^2x(t)}{dt^2} \right) + 2 \zeta \frac{1}{\omega_n} \left( \frac{dx(t)}{dt} \right) + 1 x(t) = K f(t)$$

$$\underline{x(\infty) = K f(t)}$$

constant input을 가하는 Steady state onky  $x(t)$  는  $t = \infty$  일때의 값이므로

$$\frac{d^2x}{dt^2} = \frac{dx}{dt} = 0$$


# Sinusoidal Steady state

at  $t = \infty$

$$\frac{d v_c(t)}{dt} = 0$$

$$\rightarrow i_c(\infty) = 0$$

at  $t = \infty$

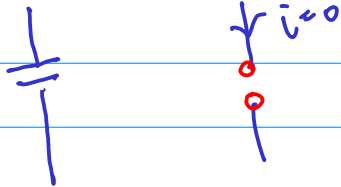


at  $t = \infty$


$$\frac{d i_L(t)}{dt} = 0$$

$$\rightarrow v_L(\infty) = 0$$

at  $t = \infty$

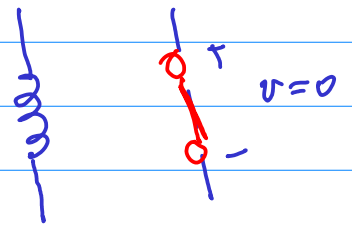

$$v_c(t) = A \cos \omega t$$


$$i_c = C \frac{d v_c}{dt}$$

$$I = \frac{1}{j \omega C} V$$

# Transient Response : 1<sup>st</sup> Order System

$$\tau \frac{dx}{dt} + x(t) = K_s \bar{F}$$

$$x(t) \begin{cases} \rightarrow V_c(t) \\ \rightarrow i_L(t) \end{cases}$$

- ① find  $x(0^-)$  &  $x(\infty)$  2 steady state values
- ② find  $x(0^+)$  &  $\dot{x}(0^+)$  initial conditions
- ③ find 1<sup>st</sup> order diff Eq

$$\tau \frac{dx}{dt} + x(t) = K_s \bar{F}$$

- ④ find  $\tau$

- ⑤ find  $x(t) = \underbrace{x_h(t)} + \underbrace{x_p(t)}_{x(\infty)}$

- ⑥ find  $\alpha = [x(0) - x(\infty)]$


@ this method works for DC input only

$$\tau \frac{dx}{dt} + x(t) = K_s \bar{F}$$

$$x(t) = [x(0) - x(\infty)] e^{-t/\tau} + x(\infty) \quad t \geq 0$$





# DC input


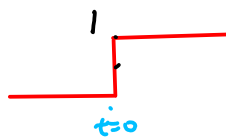


$$u(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$$



step function

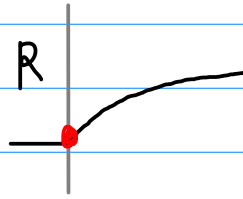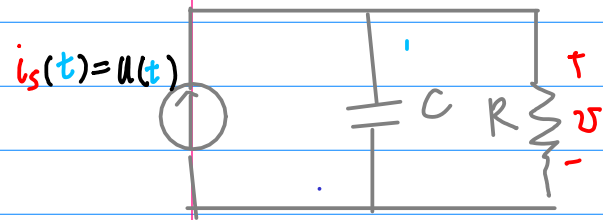



$$v = R(1 - e^{-t/RC})$$

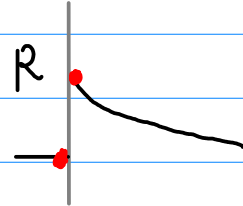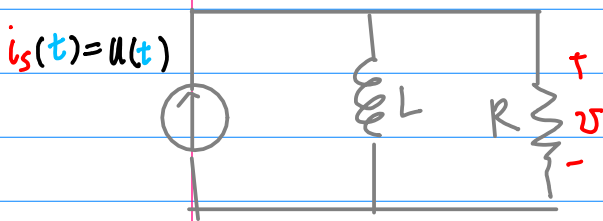

$$v = R e^{-(R/L)t}$$

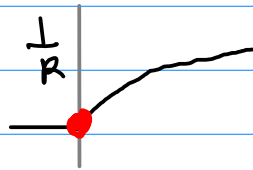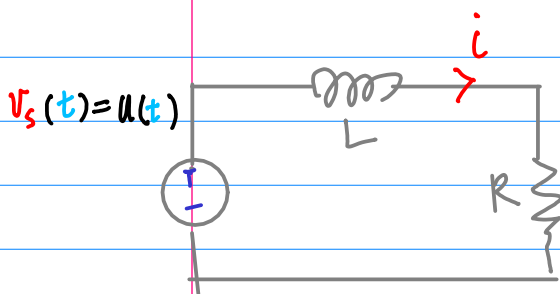


$$i = \frac{1}{R} (1 - e^{-(R/L)t})$$


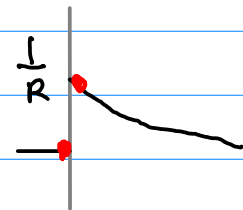
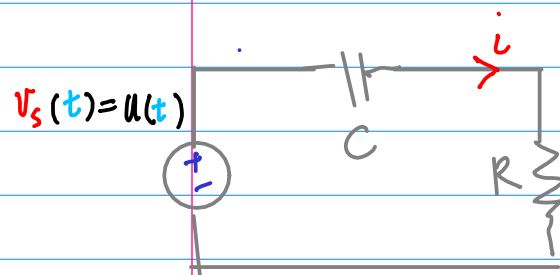


$$i = \frac{1}{R} e^{-t/RC}$$




# Unit step function

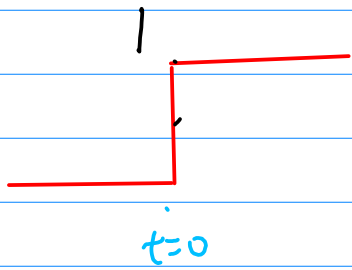
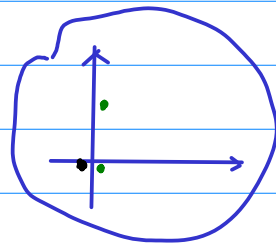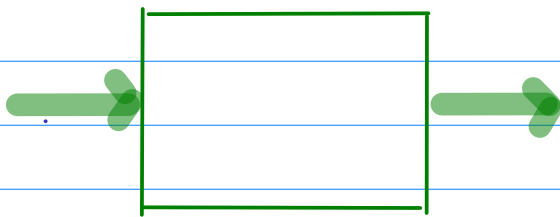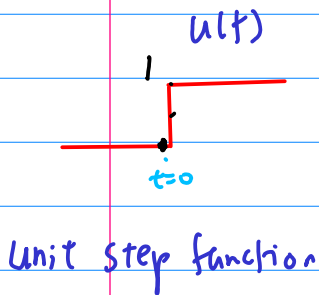
$$u(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$$



Step response

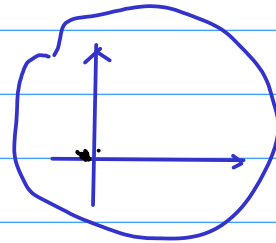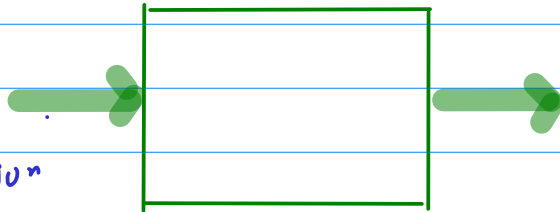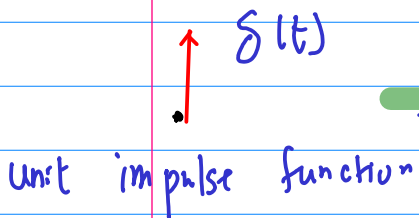


impulse response  $h(t)$

## Zero State Response (ZSR)


$t < 0$

input  $x(t) = 0$

no initial condition.

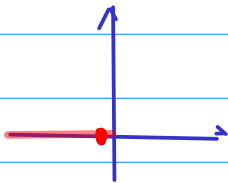

output  $y(t) = 0$

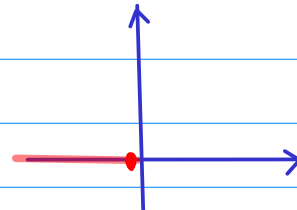

$t > 0$  일 때

non-zero input  $x(t)$ 에 의한  
output response

## Zero Input Response (ZIR)

$t > 0$









input  $x(t) = 0$  no input

non-zero initial condition에 의해









output  $t > 0$  나타남

→ transient response 일 수 있음.


$t=0^+$

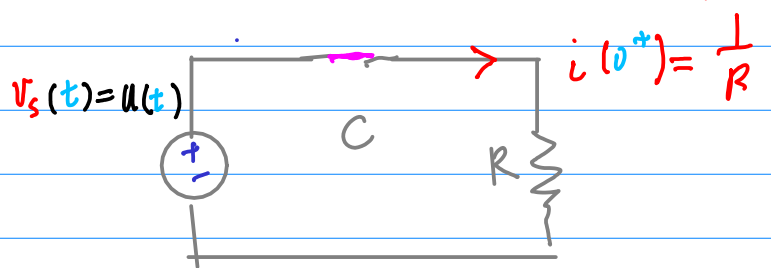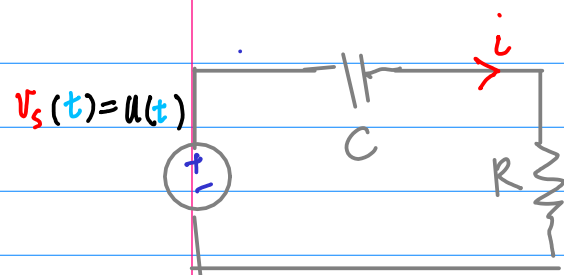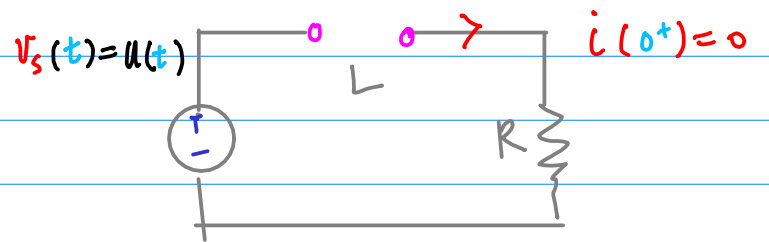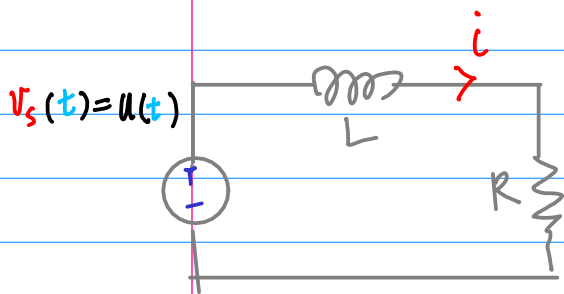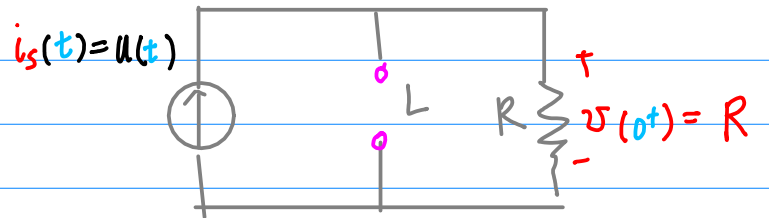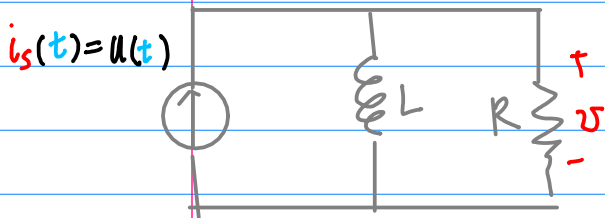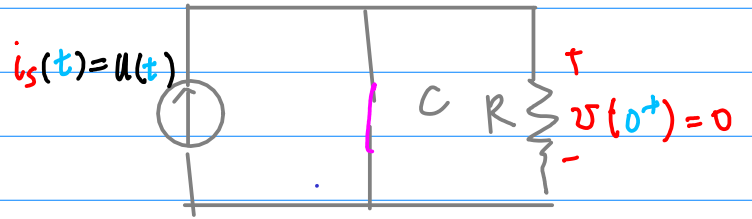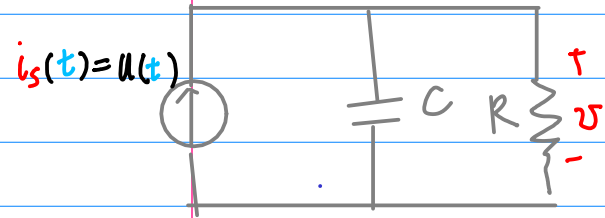



$t = \infty$

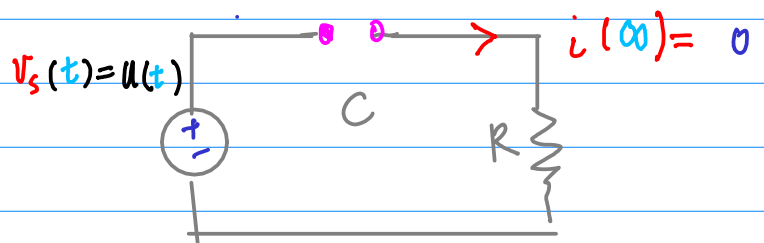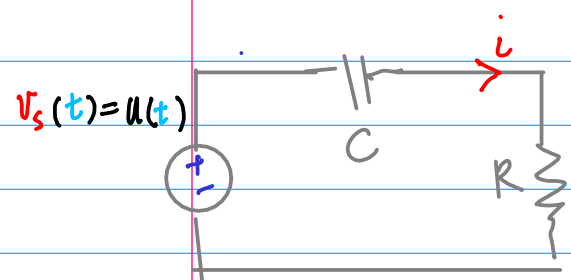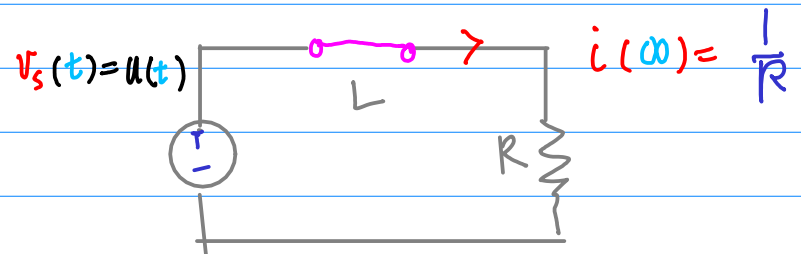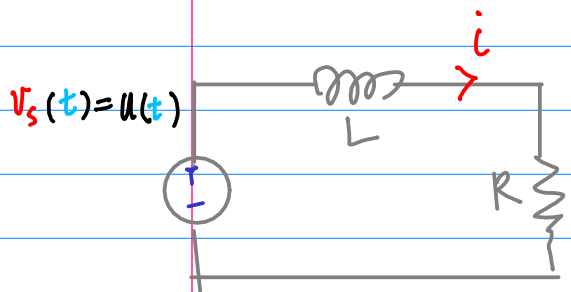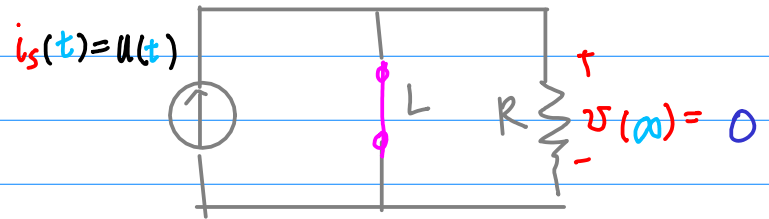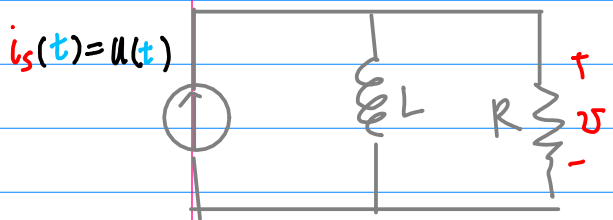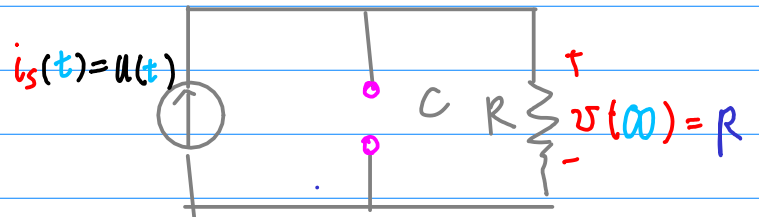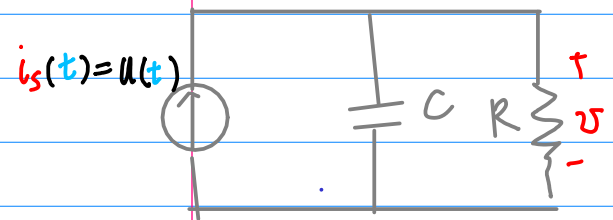



# $v(0^+)$ & $v(\infty)$

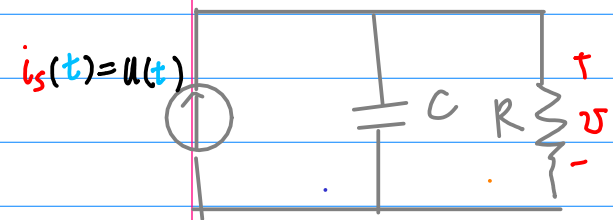



$$v(0^+) = 0 \quad v(\infty) = R$$

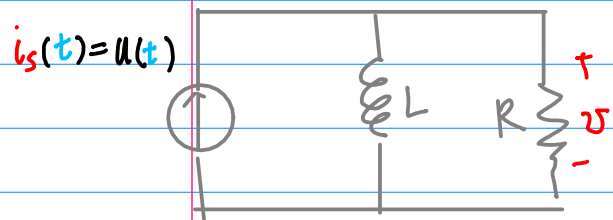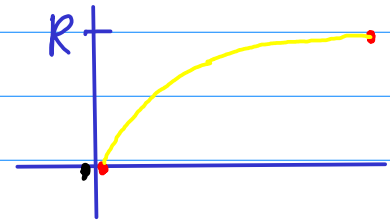


$$v(0^+) = R \quad v(\infty) = 0$$

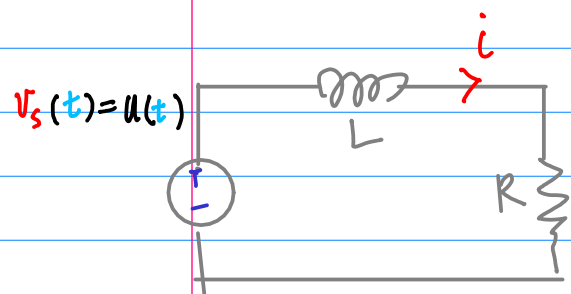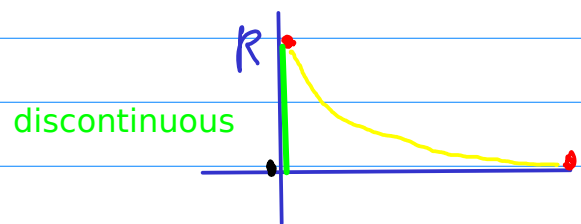
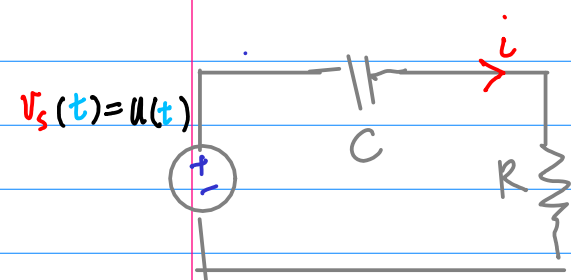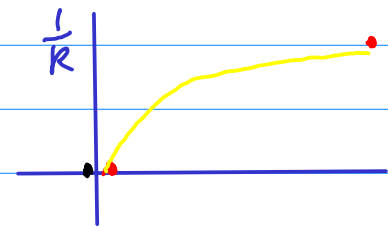
$$i(0^+) = 0 \quad i(\infty) = \frac{1}{R}$$


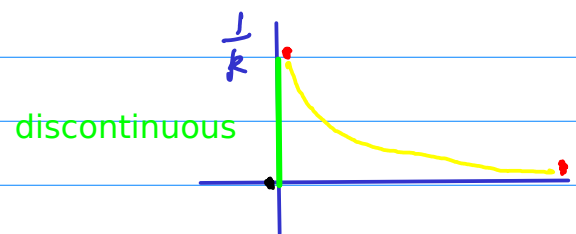
$$i(0^+) = \frac{1}{R} \quad i(\infty) = 0$$




# ODE

## Zero State Response


init cond ( $0^+$ ) = 0

$t > 0$

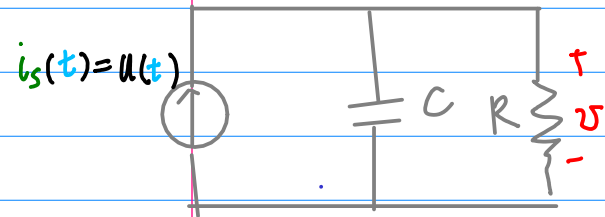

$$C \frac{dv}{dt} + \frac{v}{R} = i_s$$
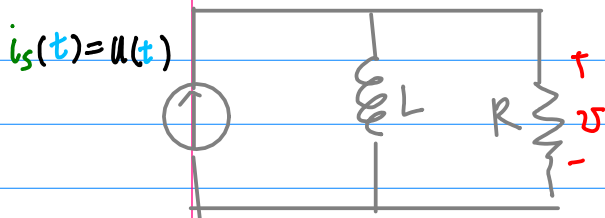
$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C} i_s$$




$$L \frac{di}{dt} = v_L \quad i_L = \frac{1}{L} \int v_L dt$$

$$\frac{1}{L} \int_0^t v dt + \frac{v}{R} = i_s$$


$$\frac{1}{L} v + \frac{1}{R} \frac{dv}{dt} = \frac{di_s}{dt}$$
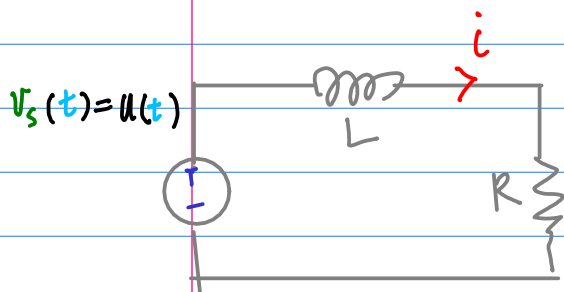
$$\frac{dv}{dt} + \frac{R}{L} v = R \frac{di_s}{dt}$$



$$L \frac{di}{dt} + R i = v_s$$
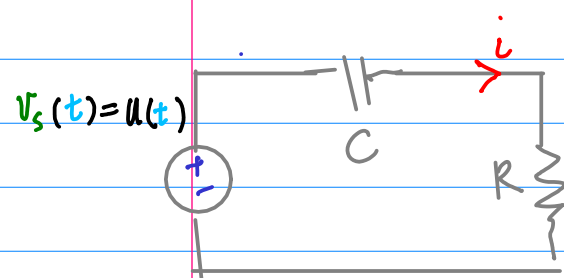
$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L} v_s$$



$$C \frac{dv_c}{dt} = i_c \quad v_c = \frac{1}{C} \int i_c dt$$


$$\frac{1}{C} \int_0^t i dt + R i = v_s$$

$$\frac{1}{C} i + R \frac{di}{dt} = \frac{dv_s}{dt}$$

$$\frac{di}{dt} + \frac{1}{RC} i = \frac{1}{R} \frac{dv_s}{dt}$$


**ODE**

for DC input

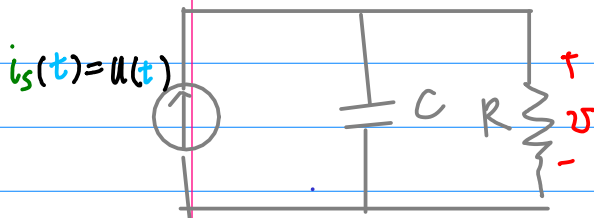


$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C} i_s$$
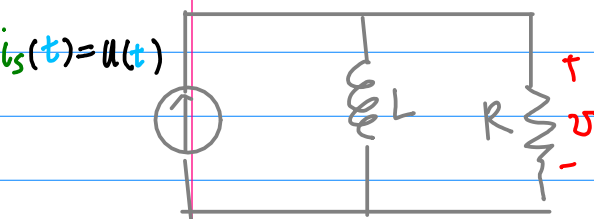
$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C}$$




$$\frac{dv}{dt} + \frac{R}{L} v = R \frac{di_s}{dt}$$

$$\frac{dv}{dt} + \frac{R}{L} v = 0^*$$

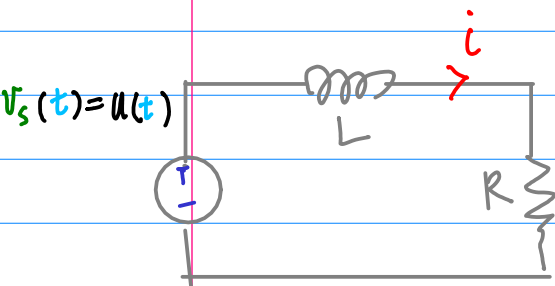

$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L} v_s$$
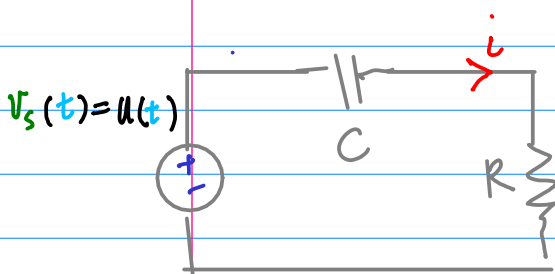
$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L}$$



$$\frac{di}{dt} + \frac{1}{RC} i = \frac{1}{R} \frac{dv_s}{dt}$$


$$\frac{di}{dt} + \frac{1}{RC} i = 0^*$$



①



$$\tau \frac{dx}{dt} + x(t) = K_s \bar{F}$$
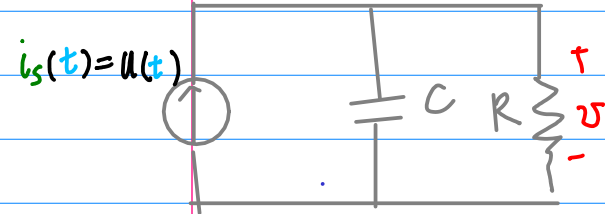
$$x(t) = [x(0) - x(\infty)] e^{-t/\tau} + x(\infty) \quad t \geq 0$$





$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C}$$

$$v(t) = [0 - R] e^{-t/RC} + R$$

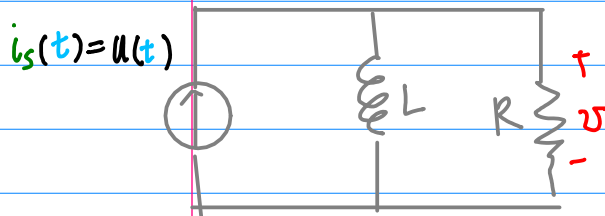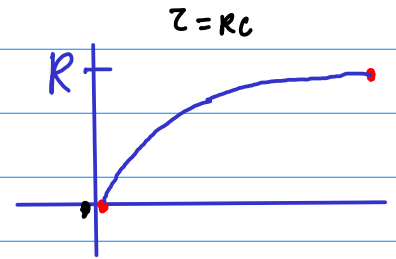



$$\frac{dv}{dt} + \frac{R}{L} v = 0^*$$

$$v(t) = [R - 0] e^{-t/(L/R)} + 0$$

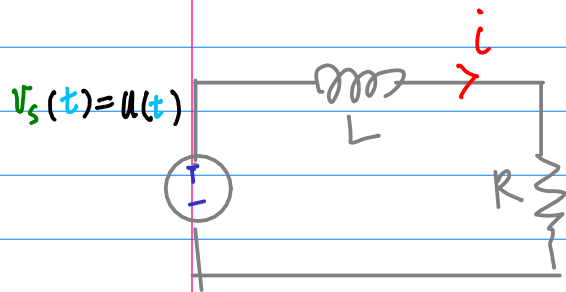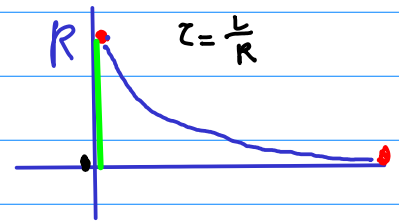


$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L}$$

$$i(t) = [0 - R] e^{-t/(L/R)} + R$$

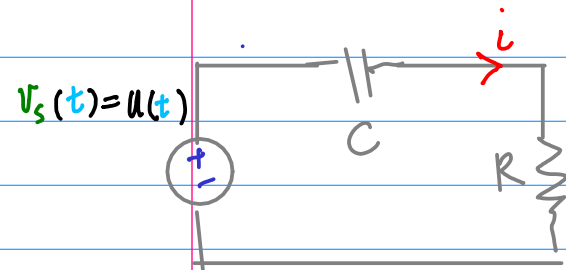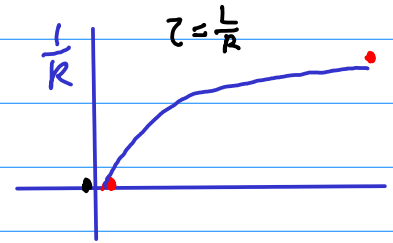

$$\frac{di}{dt} + \frac{1}{RC} i = 0^*$$

$$i(t) = [R - 0] e^{-t/RC} + 0$$

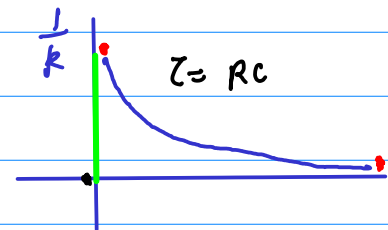

## Classical Approach for solving ODE.

$$y' + a y = g(t) \quad \text{1st order Linear ODE}$$

$$m + a = 0 \quad \text{aux. eq}$$

$$y_h(t) = C_1 e^{-a \cdot t}$$

$t > 0$  step function input  $g(t) \rightarrow \text{Const}$  ①

$$y_p(t) = A$$

$$a \cdot A = 1 \quad A = \frac{1}{a}$$


$$y(t) = y_h(t) + y_p(t)$$

$$y(t) = C_1 e^{-a \cdot t} + \frac{1}{a}$$

$$* \textcircled{y(0^+)} = C_1 e^{-a \cdot 0} + \frac{1}{a} \rightarrow \text{determine } \textcircled{C_1}$$

2

$$y_h + y_p$$

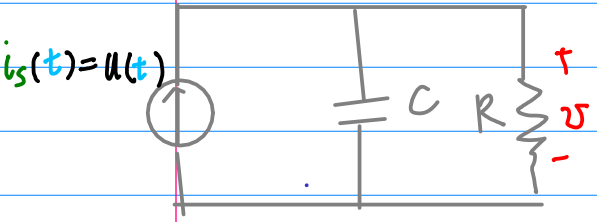

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C}$$

$$v_h(t) = c_1 e^{-t/RC}$$


$$\frac{v_p}{RC} = \frac{1}{C}$$

$$v_p(t) = R$$

$$v(0^+) = 0$$

$$c_1 = -R$$

$$v = R(1 - e^{-t/RC})$$

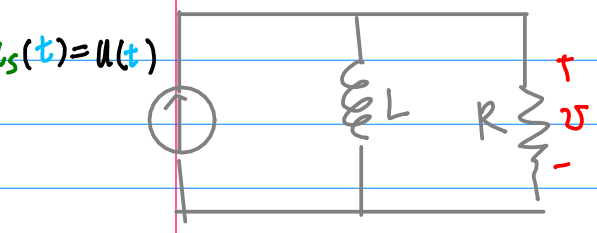

$$\frac{dv}{dt} + \frac{R}{L} v = 0^*$$

$$v_h(t) = c_1 e^{-t(L/R)}$$


$$\frac{R}{L} v_p = 0$$

$$v_p(t) = 0$$

$$v(0^+) = R$$

$$c_1 = R$$

$$v = R e^{-(R/L)t}$$

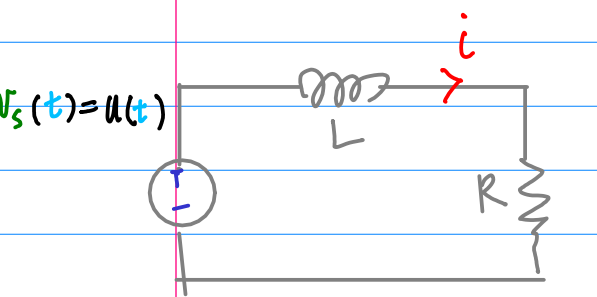

$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L}$$

$$i_h(t) = c_1 e^{-t(L/R)}$$


$$\frac{R}{L} i_p = \frac{1}{L}$$

$$i_p(t) = \frac{1}{R}$$

$$i(0^+) = 0$$

$$c_1 = -\frac{1}{R}$$

$$i = \frac{1}{R}(1 - e^{-(R/L)t})$$

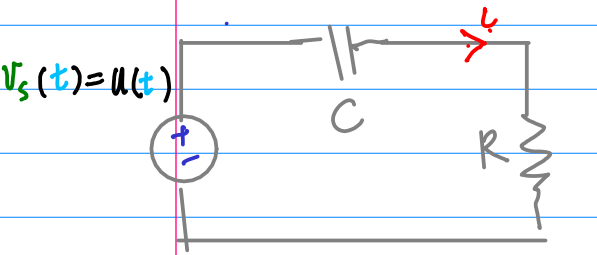

$$\frac{di}{dt} + \frac{1}{RC} i = 0^*$$

$$i_h(t) = c_1 e^{-t/RC}$$

$$\frac{1}{RC} i_p = 0$$

$$i_p(t) = 0$$

$$i(0^+) = \frac{1}{R}$$

$$c_1 = \frac{1}{R}$$

$$i = \frac{1}{R} e^{-t/RC}$$

# Solving IVPs with Laplace Transform

$$y' + a y = g(t)$$

1st order Linear ODE

$$y(0^-)$$

initial condition

$$0^-$$

Laplace Transform

$$sY(s) - y(0^-) + aY(s) = G(s)$$

$$(s+a)Y(s) = y(0^-) + G(s)$$

$$Y(s) = \frac{y(0^-)}{(s+a)} + \frac{G(s)}{(s+a)}$$

ZIR

ZSR

step function input  $g(t) = u(t)$   $G(s) = \frac{1}{s}$


Zero state Response to the unit step input (ZSR)

$$y(0^-) = 0$$

$$Y(s) = \frac{1}{s(s+a)} = \frac{1}{a} \left( \frac{1}{s} - \frac{1}{s+a} \right)$$

$$y(t) = \frac{1}{a} (1 - e^{-at})$$

# ③ ZSK using Laplace Transform

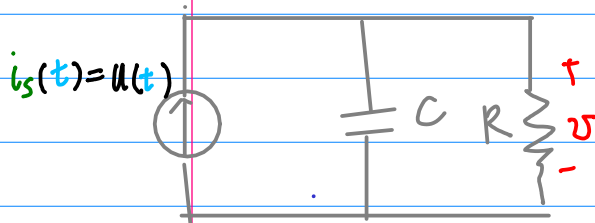


$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C} u(t)$$

$$v(0^-) = 0$$

$$V(s) = \frac{1}{C} \frac{1}{s(s + \frac{1}{RC})}$$

$$= R \left( \frac{1}{s} - \frac{1}{s + \frac{1}{RC}} \right)$$

$$v = R(1 - e^{-t/RC})$$

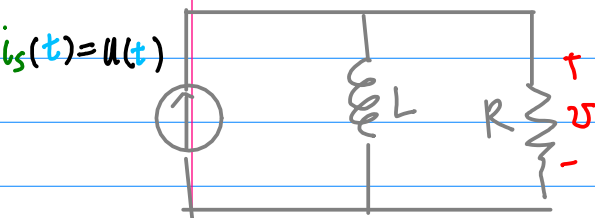


$$\frac{dv}{dt} + \frac{R}{L} v = R \delta(t)$$

$$v(0^-) = 0$$

$$V(s) = R \frac{1}{s + \frac{R}{L}}$$

$$v = R e^{-(R/L)t}$$

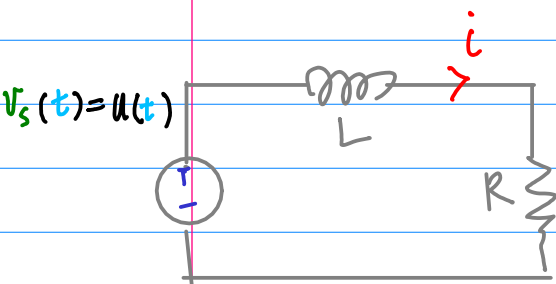


$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L} u(t)$$

$$i(0^-) = 0$$

$$I(s) = \frac{1}{L} \frac{1}{s(s + \frac{R}{L})}$$

$$= \frac{1}{R} \left( \frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right)$$

$$i = \frac{1}{R} (1 - e^{-(R/L)t})$$

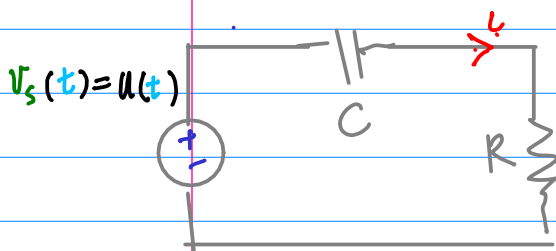

$$\frac{di}{dt} + \frac{1}{RC} i = \frac{1}{R} \delta(t)$$

$$i(0^-) = 0$$

$$I(s) = \frac{1}{R} \frac{1}{s + \frac{1}{RC}}$$

$$i = \frac{1}{R} e^{-t/RC}$$

# S-domain Impedance

Time Domain	s-Domain	


wikipedia.org

non-zero initial conditions

ZSR using s-domain impedance

Element	Impedance expression
Resistor	$R$
Inductor	$sL$
Capacitor	$\frac{1}{sC}$

④ ZSR using s-domain impedance

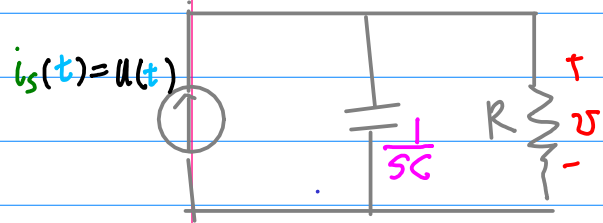

$$\frac{1}{sC} \parallel R$$


$$= \frac{1}{sC + \frac{1}{R}}$$

$$Z = \frac{1}{C \left( s + \frac{1}{RC} \right)}$$

$$V(s) = \frac{1}{C} \frac{1}{s \left( s + \frac{1}{RC} \right)}$$

$$= R \left( \frac{1}{s} - \frac{1}{s + \frac{1}{RC}} \right)$$

$$v = R(1 - e^{-t/RC})$$

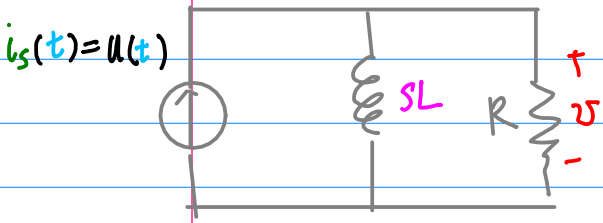


$$sL \parallel R = \frac{1}{\frac{1}{sL} + \frac{1}{R}}$$

$$= \frac{sLR}{sL + R}$$

$$Z = R \frac{s}{s + \frac{R}{L}}$$

$$V(s) = R \frac{1}{s + \frac{R}{L}}$$

$$v = R e^{-(R/L)t}$$

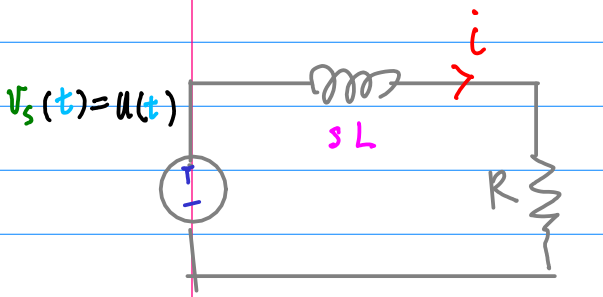

$$sL + R$$


$$= L \left( s + \frac{R}{L} \right)$$

$$Y = \frac{1}{L} \frac{1}{\left( s + \frac{R}{L} \right)}$$

$$I(s) = \frac{1}{L} \frac{1}{s \left( s + \frac{R}{L} \right)}$$

$$= \frac{1}{R} \left( \frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right)$$

$$i = \frac{1}{R} (1 - e^{-(R/L)t})$$

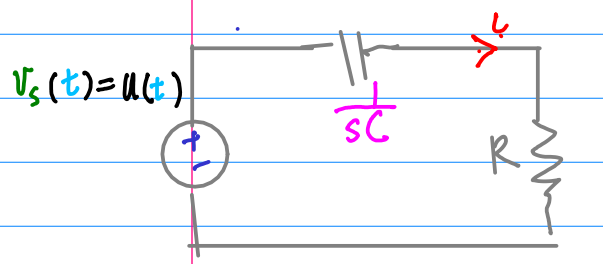

$$\frac{1}{sC} + R = \frac{1}{sC} (1 + sRC)$$

$$= \frac{R}{s} \left( \frac{1}{RC} + s \right)$$




$$Y = \frac{1}{R} \frac{s}{s + \frac{1}{RC}}$$

$$I(s) = \frac{1}{R} \frac{1}{s + \frac{1}{RC}}$$

$$i = \frac{1}{R} e^{-t/RC}$$

(4)

$$v_s(t) = u(t)$$

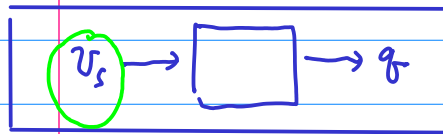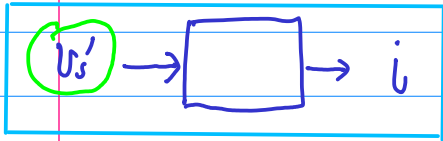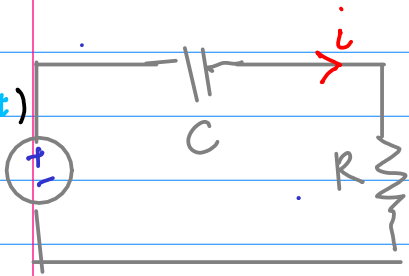

$$C \frac{dv_c}{dt} = i_c \quad v_c = \frac{1}{C} \int i_c dt$$

$$\frac{1}{C} \int_0^t i dt + Ri = v_s$$

$$\frac{1}{C} i + R \frac{di}{dt} = \frac{dv_s}{dt}$$

$$\frac{di}{dt} + \frac{1}{RC} i = \frac{1}{R} \frac{dv_s}{dt}$$

$$\frac{dq}{dt} + \frac{1}{RC} q = \frac{1}{R} v_s$$

$$q_h(t) = c_1 e^{-\frac{t}{RC}}$$

$$q_p(t) = A \quad 0 + \frac{1}{RC} A = \frac{1}{R}$$

$$= C$$

$$q(t) = c_1 e^{-\frac{t}{RC}} + C$$


$$q(0^+) = c_1 e^{-\frac{0^+}{RC}} + C = 0 \quad c_1 = -C$$

$$q(t) = C(1 - e^{-\frac{t}{RC}})$$

$$i(t) = q'(t) = \frac{1}{R} e^{-\frac{t}{RC}}$$



$$V_s(t) = u(t)$$

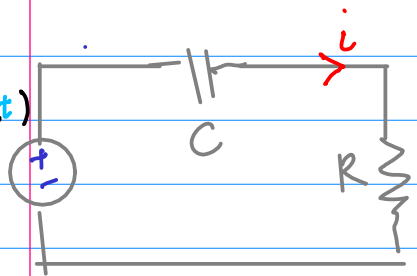

$$C \frac{dv_c}{dt} = i_c \quad v_c = \frac{1}{C} \int i_c dt$$

$$\frac{1}{C} \int_0^t i dt + Ri = v_s$$

$$\frac{1}{C} i + R \frac{di}{dt} = \frac{dv_s}{dt}$$

$$\frac{di}{dt} + \frac{1}{RC} i = \frac{1}{R} \frac{dv_s}{dt}$$


$$s \bar{I}(s) - i(0^-) + \frac{1}{RC} \bar{I}(s) = \frac{1}{R} (s V(s) - v(0^-))$$

$$(s + \frac{1}{RC}) \bar{I}(s) = \frac{1}{R} s \frac{1}{s}$$

$$\bar{I}(s) = \frac{1}{R} \frac{1}{(s + \frac{1}{RC})}$$

$$i(t) = \frac{1}{R} e^{-\frac{t}{RC}}$$

$$\frac{1}{sC} \quad sL$$

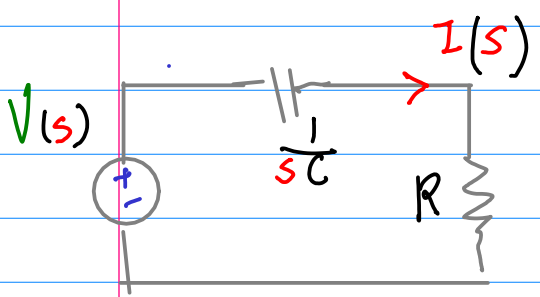


$$I(s) = \frac{V(s)}{(\frac{1}{sC} + R)} = \frac{\frac{1}{s}}{(\frac{1}{sC} + R)}$$

$$\frac{1/R}{\frac{1}{RC} + s}$$




$$\frac{1}{R} e^{-\frac{t}{RC}}$$

$$y^{(N)} + a_1 y^{(N-1)} + \dots + a_{N-1} y^{(1)} + a_N y = x$$

base system

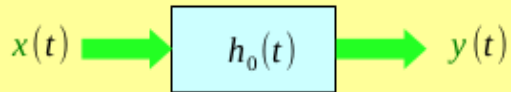

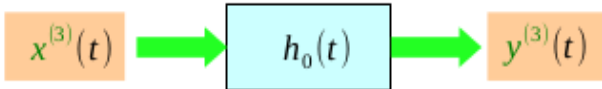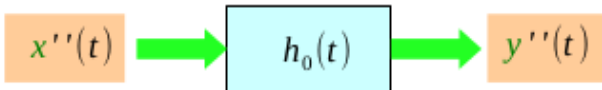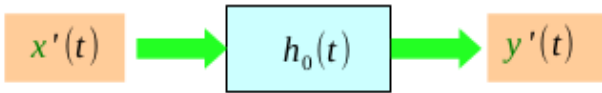notation:  $y^{(N)} = \frac{d^N y}{dt^N} = \frac{d^N}{dt^N} y(t)$



$$y'' + a y' + b y(t) = x(t)$$

$$y''' + a y'' + b y'(t) = x'(t)$$

$$\frac{d^2}{dt^2} \left( \frac{dy}{dt} \right) + a \frac{d}{dt} \left( \frac{dy}{dt} \right) + b \left( \frac{dy}{dt} \right) = \left( \frac{dx}{dt} \right)$$

$$y'' + a y' + b y(t) = x(t)$$







