

RLC Transient Response (H.1)

2nd Order Circuit

20150720

The necessities in Electric Circuit
wikiversity

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Transient Response : 2nd Order System

$$\frac{1}{\omega_0^2} \frac{d^2 x(t)}{dt^2} + 2 \zeta \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$

$$x(t) \begin{cases} \rightarrow V_c(t) \\ \rightarrow i_L(t) \end{cases}$$

① find $x(0^-)$ & $x(\infty)$ 2 steady state values

② find $x(0^+)$ & $\dot{x}(0^+)$ initial conditions

③ find 2nd order diff eq.

$$\frac{1}{\omega_0^2} \frac{d^2 x(t)}{dt^2} + 2 \zeta \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$

④ find ω_n & ζ

⑤ find $x(t) = \underbrace{x_h(t)} + \underbrace{x_p(t)} = x(\infty)$

⑥ find α_1 & α_2

Constant input : DC

$$\frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + 2 \zeta \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$

a) $\zeta > 1$	b) $\zeta = 1$	c) $\zeta < 1$
$\alpha_1 e^{(-\zeta\omega_n + \sqrt{\zeta^2 - 1}\omega_n)t}$ + $\alpha_2 e^{(-\zeta\omega_n - \sqrt{\zeta^2 - 1}\omega_n)t}$ + $x(\infty)$	$\alpha_1 e^{(-\zeta\omega_n)t}$ + $\alpha_2 t e^{(-\zeta\omega_n)t}$ + $x(\infty)$	$\alpha_1 e^{(-\zeta\omega_n + j\sqrt{1-\zeta^2}\omega_n)t}$ + $\alpha_2 e^{(-\zeta\omega_n - j\sqrt{1-\zeta^2}\omega_n)t}$ + $x(\infty)$

$x(\infty)$... particular for ced

Homogeneous sol \rightarrow natural response $\rightarrow 0$ vanishes

$$\begin{aligned} & \alpha_1 e^{(-\zeta\omega_n + \sqrt{\zeta^2 - 1}\omega_n)t} + \alpha_2 e^{(-\zeta\omega_n - \sqrt{\zeta^2 - 1}\omega_n)t} \\ & \alpha_1 e^{(-\zeta\omega_n)t} + \alpha_2 t e^{(-\zeta\omega_n)t} \\ & \alpha_1 e^{(-\zeta\omega_n + j\sqrt{1-\zeta^2}\omega_n)t} + \alpha_2 e^{(-\zeta\omega_n - j\sqrt{1-\zeta^2}\omega_n)t} \end{aligned}$$

$$e^{-\zeta\omega_n t}$$

$$e^{-\zeta\omega_n t} \rightarrow 0$$

$$\boxed{\zeta > 0}$$

$$\omega_n > 0$$

$$t > 0$$



$$\begin{aligned} & c_1 e^{-\zeta\omega_n t} \cos(\sqrt{1-\zeta^2}\omega_n t) \\ & + c_2 e^{-\zeta\omega_n t} \sin(\sqrt{1-\zeta^2}\omega_n t) \end{aligned}$$

① find $x(0^-)$ & $x(\infty)$



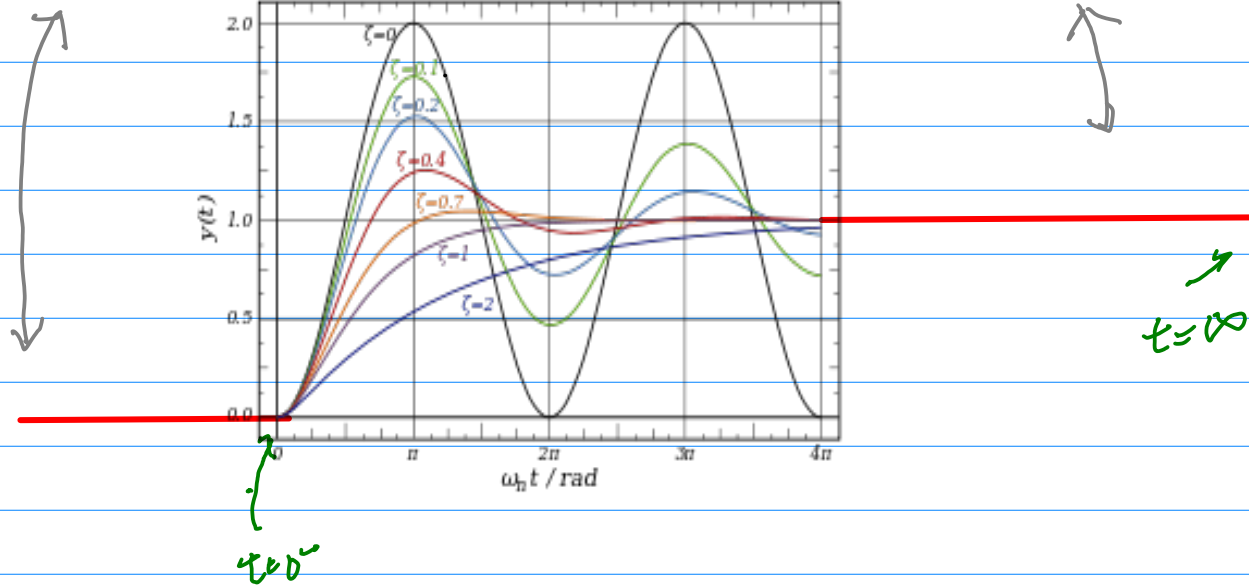
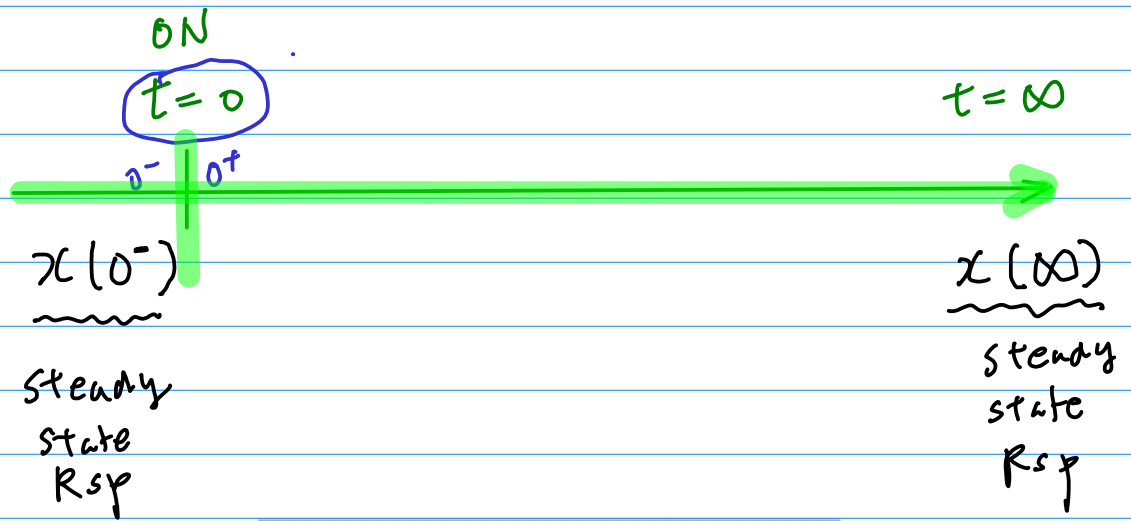


Fig 5.80 $t = 0^-$

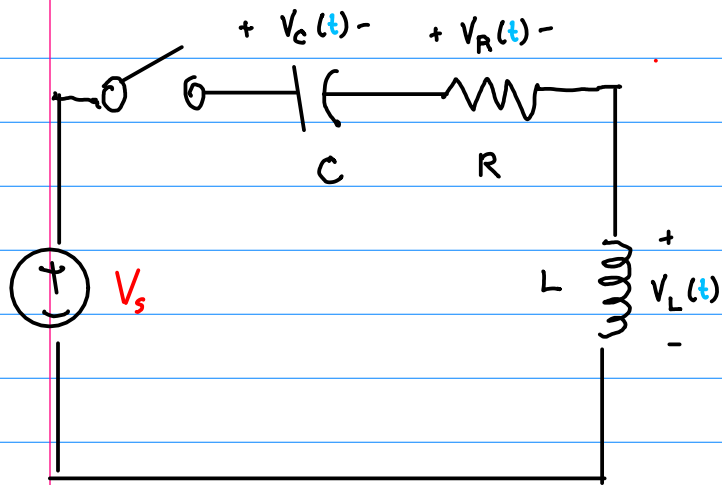


$\frac{25}{2} \text{ mV}$
 \downarrow
 $\begin{cases} V_C(0^-) = 5 \\ i_L(0^-) = 0 \end{cases}$

$t = 0^+$

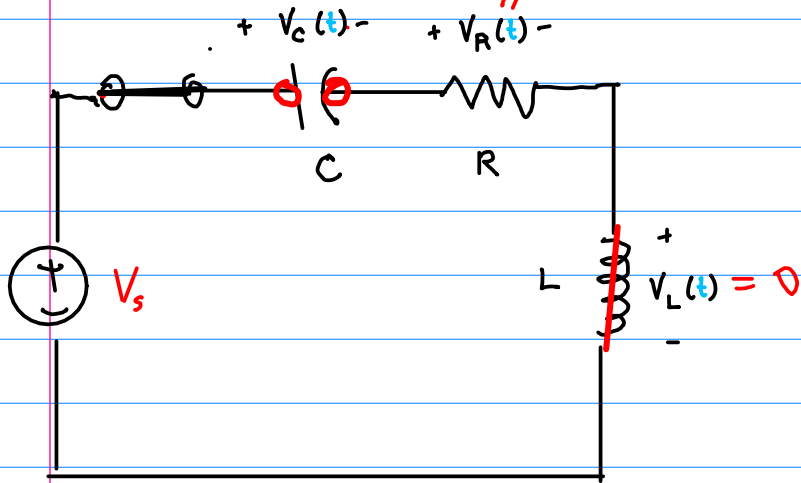


$\begin{cases} V_C(\infty) = 25 \\ i_L(\infty) = 0 \end{cases}$

$t = 0^-$

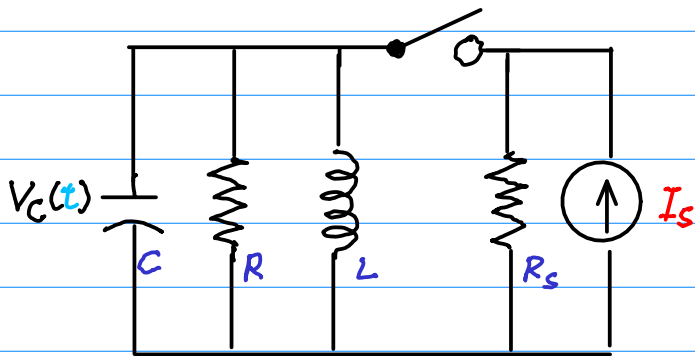


$$i_L(0^-) = 0$$
$$V_C(0^-) = 0$$

$t = \infty$


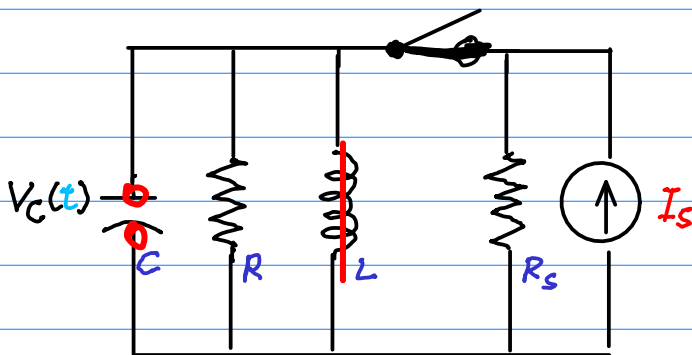


$$i_L(\infty) = I_s$$
$$V_C(\infty) = 0$$

② find $x(0^+)$, $\dot{x}(0^+)$

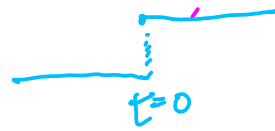


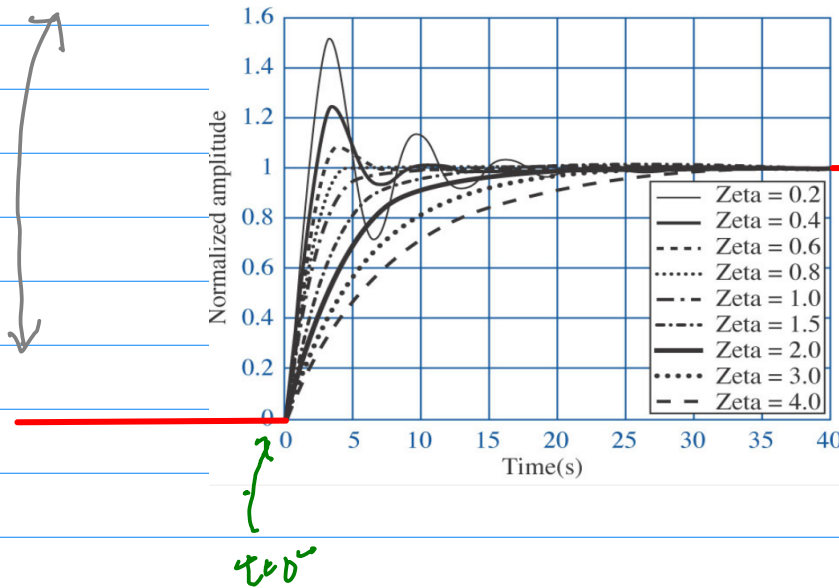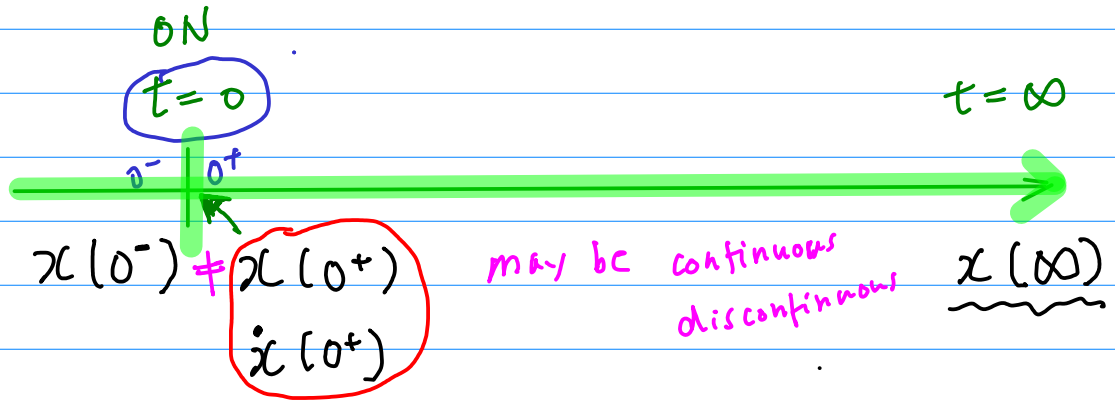continuous v_C : $v_C(0^-) = v_C(0^+)$
 continuous i_L : $i_L(0^-) = i_L(0^+)$



Step 2

$t = 0^+$

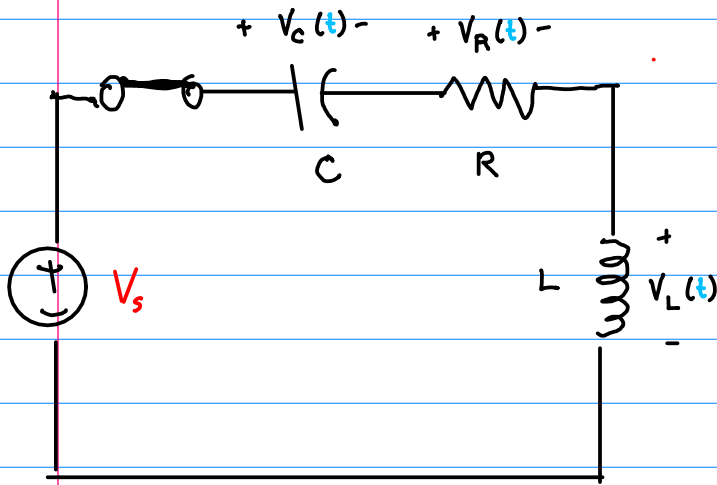

$\frac{2}{21} \text{ mV}$
 \downarrow

$$\begin{cases} V_c(0^-) = 5 = V_c(0^+) \\ i_L(0^-) = 0 = i_L(0^+) \end{cases}$$

continue

$$i_L'(0^+) = ?$$

$t = 0^+$ KVL


$$V_s - V_c(0^+) - R i_L(0^+) - V_L(0^+) = 0$$

$$V_s - V_c(0^+) - R i_L(0^+) - L \frac{di_L(0^+)}{dt} = 0$$

$$\frac{di_L(0^+)}{dt} = \frac{1}{L} \left(\underbrace{V_s}_{4V} - \underbrace{V_c(0^+)}_{5} - \underbrace{R i_L(0^+)}_{0} \right)$$

sleep

$t=0^+$

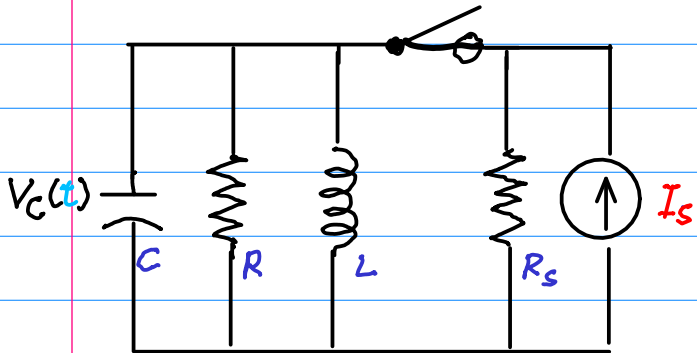

$$i_L(0^-) = 0 = i_L(0^+)$$
$$V_C(0^-) = 0 = V_C(0^+)$$

$$V_C'(0^+) = ?$$

$$I_s - \frac{V_C(t)}{R_s} - i_L(t) - \frac{V_C(t)}{R} - C \frac{dV_C(t)}{dt} = 0$$

$$I_s - \frac{V_C(0^+)}{R_s} - i_L(0^+) - \frac{V_C(0^+)}{R} - C \frac{dV_C(0^+)}{dt} = 0$$

$$\frac{dV_C(0^+)}{dt} = \frac{1}{C} I_s$$

③ find 2nd order diff eq

$$\frac{1}{\omega_0^2} \frac{d^2 x(t)}{dt^2} + 2 \zeta \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$


$t > 0$ \Rightarrow switch "ON"

$$x(t) = \begin{cases} v_c(t) & \leftarrow \text{parallel same volt.} \\ \underline{i_L(t)} & \leftarrow \text{series same current} \end{cases}$$

$$LC \frac{d^2 i_L}{dt^2} + RL \frac{di_L}{dt} + 1 i_L(t) = 0$$

$$LC \frac{d^2 v_c}{dt^2} + L \left(\frac{R_s + R}{R_s R} \right) \frac{dv_c}{dt} + 1 v_c(t) = 0$$

$t > 0$

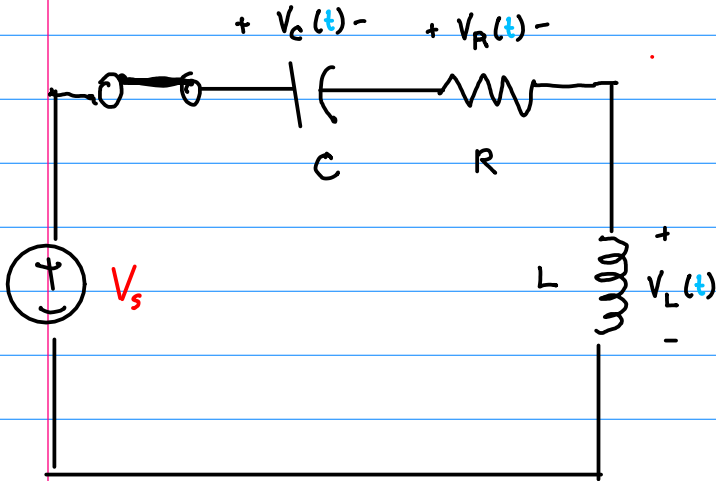

$$V_s - V_c(t) - R \cdot i_L(t) - L \frac{di_L}{dt} = 0$$

$$V_c(t) = \frac{1}{C} \int_{-\infty}^t i_L(t) dt$$

$$\frac{d}{dt} \left\{ V_s - \frac{1}{C} \int_{-\infty}^t i_L(t) dt - R \cdot i_L(t) - L \frac{di_L}{dt} = 0 \right\}$$


↓
KVL

$$-\frac{1}{C} i_L(t) - R \cdot \frac{di_L}{dt} - L \frac{d^2 i_L}{dt^2} = 0$$

$$L \frac{d^2 i_L}{dt^2} + R \frac{di_L}{dt} + 1 i_L(t) = 0$$

$$LC \frac{d^2 i_L}{dt^2} + R \frac{di_L}{dt} + 1 i_L(t) = 0$$

$t > 0$

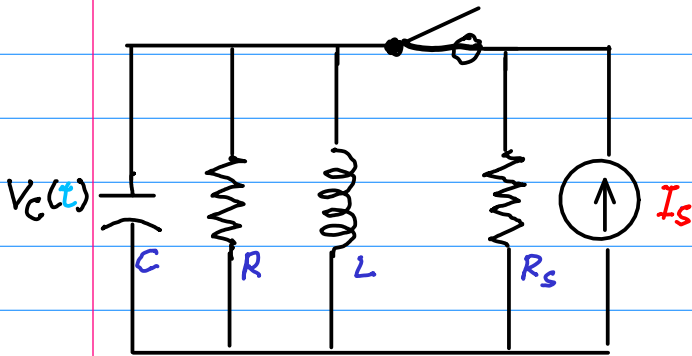

$$L \frac{di_L}{dt} = v_L$$

$$i_L = \frac{1}{L} \int v_L dt$$

KCL

$$I_s - \frac{v_C(t)}{R_s} - i_L(t) - \frac{v_C(t)}{R} - C \frac{dv_C(t)}{dt} = 0$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^{\infty} v_C(t) dt$$

$$\left\{ \frac{d}{dt} \left[I_s - \frac{v_C(t)}{R_s} - \frac{1}{L} \int_{-\infty}^{\infty} v_C(t) dt - \frac{v_C(t)}{R} - C \frac{dv_C(t)}{dt} \right] = 0 \right\}$$

$$\left(\frac{1}{R_s} + \frac{1}{R} \right) \frac{dv_C}{dt} + \frac{1}{L} v_C(t) + C \frac{d^2 v_C}{dt^2} = 0$$

$$L C \frac{d^2 v_C}{dt^2} + L \left(\frac{R_s + R}{R_s R} \right) \frac{dv_C}{dt} + v_C(t) = 0$$

④


Find

ω_n

&

ζ

↑ natural freq ↑ damping ratio

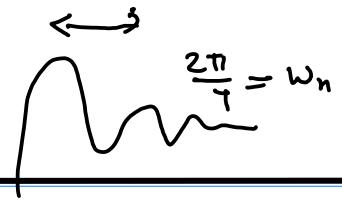

$$\frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + 2 \frac{\zeta}{\omega_n} \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$

$$LC \frac{d^2 i_L}{dt^2} + RC \frac{di_L}{dt} + 1 i_L(t) = 0$$

$$\omega_n = \sqrt{\frac{1}{LC}} = 1000$$

$$\zeta = RC \frac{\omega_n}{2} = 2.5 \quad \text{overdamping}$$

$$LC \frac{d^2 v_C}{dt^2} + L \left(\frac{R_s + R}{R_s R} \right) \frac{dv_C}{dt} + 1 v_C(t) = 0$$

$$\omega_n = \sqrt{\frac{1}{LC}} = 560$$

$$\zeta = L \left(\right) \frac{\omega_n}{2} = 1 \quad \text{critical damping}$$

5) find $x(t) = \underline{x_h(t)} + x_p(t)$ $x(\infty)$

§ out circuit

5 > 1

$$D > 0$$

2 distinct real roots m_1, m_2

$$x_h(t) \Leftarrow x_h(t) = C_1 e^{m_1 t} + C_2 e^{m_2 t}$$

5 = 1

$$D = 0$$

repeated real root m_1

$$x_h(t) \Leftarrow x_h(t) = C_1 e^{m_1 t} + C_2 t e^{m_2 t}$$

5 < 1

$$D < 0$$

2 complex conjugate root $m_1 = \alpha + j\beta, m_2 = \alpha - j\beta$

$$x_h(t) \Leftarrow x_h(t) = C_1 e^{(\alpha + j\beta)t} + C_2 e^{(\alpha - j\beta)t}$$
$$= e^{\alpha t} (C_3 \cos(\beta t) + C_4 \sin(\beta t))$$

(a) $\zeta > 1$

$$x(t) = x_N(t) + x_F(t)$$

$$\begin{aligned} &= \alpha_1 e^{(-\zeta\omega_n + \sqrt{\zeta^2 - 1}\omega_n)t} \\ &+ \alpha_2 e^{(-\zeta\omega_n - \sqrt{\zeta^2 - 1}\omega_n)t} \\ &+ x(\infty) \end{aligned}$$

$t \geq 0$

(b) $\zeta = 1$


$$x(t) = x_N(t) + x_F(t)$$

$$\begin{aligned} &= \alpha_1 e^{(-\zeta\omega_n)t} \\ &+ \alpha_2 t e^{(-\zeta\omega_n)t} \\ &+ x(\infty) \end{aligned}$$

 (c) $\zeta < 1$

$$x(t) = x_N(t) + x_F(t)$$

$$\begin{aligned} &= \alpha_1 e^{(-\zeta\omega_n + j\sqrt{1-\zeta^2}\omega_n)t} \\ &+ \alpha_2 e^{(-\zeta\omega_n - j\sqrt{1-\zeta^2}\omega_n)t} \\ &+ x(\infty) \end{aligned}$$



① find α_1 & α_2

initial condition

$$\begin{cases} i_L(0^+) \\ \dot{i}_L(0^+) \end{cases}$$

$$\begin{cases} v_C(0^+) \\ \dot{v}_C(0^+) \end{cases}$$

Step 2

② $\zeta > 1$

$$x(t) = \alpha_1 e^{(-\zeta\omega_n + \sqrt{\zeta^2 - 1}\omega_n)t} + \alpha_2 e^{(-\zeta\omega_n - \sqrt{\zeta^2 - 1}\omega_n)t} + x(\infty)$$

$x'(t) \Big|_{t=0^+}$
 $t \geq 0$

③ $\zeta = 1$

$$x(t) = \alpha_1 e^{(-\zeta\omega_n)t} + \alpha_2 t e^{(-\zeta\omega_n)t} + x(\infty)$$

$x'(t) \Big|_{t=0^+}$

④ $\zeta < 1$

$$x(t) = \alpha_1 e^{(-\zeta\omega_n + j\sqrt{1-\zeta^2}\omega_n)t} + \alpha_2 e^{(-\zeta\omega_n - j\sqrt{1-\zeta^2}\omega_n)t} + x(\infty)$$





